



**Am29000™ Microprocessor
Memory Design**

Handbook

Advanced
Micro
Devices



Am29000™
Memory Design
Handbook



© 1992 Advanced Micro Devices, Inc.

Advanced Micro Devices reserves the right to make changes in its products without notice in order to improve design or performance characteristics.

This publication neither states nor implies any warranty of any kind, including but not limited to implied warrants of merchantability or fitness for a particular application. AMD assumes no responsibility for the use of any circuitry other than the circuitry in an AMD product.

The information in this publication is believed to be accurate in all respects at the time of publication, but is subject to change without notice. AMD assumes no responsibility for any errors or omissions, and disclaims responsibility for any consequences resulting from the use of the information included herein. Additionally, AMD assumes no responsibility for the functioning of undescribed features or parameters.

Trademarks

AMD, PAL, and PALASM are registered trademarks of Advanced Micro Devices, Inc.

Am29000, Am29005, Am29030, Am29035, Am29050, 29K, Branch Target Cache, LabPro, and MACH are trademarks of Advanced Micro Devices, Inc.

Fusion29K is a service mark of Advanced Micro Devices, Inc.

Product names used in this publication are for identification purposes only and may be trademarks of their respective companies.

TABLE OF CONTENTS

	Preface	P-1
Chapter 1	Overview	1-1
	Performance/Cost Options	1-1
	Memory Latency And Performance	1-2
	How To Use This Handbook	1-3
Chapter 2	Basic Issues For Am29000 Processor Memory Designs	2-1
	Key Memory System Factors	2-1
	Trade-offs	2-5
	Memory Implementation Issues	2-8
	Address And Control Driver Issues	2-17
	Speed Limit	2-18
	Bank Interleaving	2-20
	Instruction vs. Data Access Speeds	2-20
	Test Hardware Interface	2-20
	Memory Design Documentation	2-22
Chapter 3	The Design Process—SRAM Example	3-1
	Interface Decisions	3-1
	Instruction Memory Design	3-4
	Instruction Memory: Single-Bank Burst Access	3-7
	Instruction Memory: Dual-Bank Burst Access	3-14
	Data Memory Design	3-19
	Conclusion	3-26
	Example SRAM Designs — Details	3-27
Chapter 4	The Design Process—Simple EPROM Example	4-1
	Background	4-1
	EPROM Memory Design Assumptions	4-1
	Design Description	4-1
	Detailed Description	4-3
	Conclusions	4-3
	References	4-3
	PAL Device Equations	4-5
Chapter 5	Connecting the Instruction/Data Buses	5-1
	Instruction RAM Design	5-1
	Instruction EPROM Summary	5-5
	Addition Of Read/Write Memory	5-6
	Read/Write Memory Summary	5-7
	DRAM Support	5-8
	Further Increases In Performance	5-9
Chapter 6	16-Bit Memory Architecture	6-1
	Overview Of The 16-Bit Design	6-1
	Theory Of Operation	6-2
	Critical Timing Paths	6-6

	Benchmark Figures	6-8
	Summary	6-8
	Timing Diagrams	6-24
	Parts List	6-26
Chapter 7	Interleaved SCDRAM	7-1
	Memory Structure	7-1
	Instruction Memory	7-1
	Memory Interface Logic Equations	7-5
	Logic Details Signal By Signal	7-8
	Data Memory	7-35
Chapter 8	Single-Bank SCDRAM	8-1
	System Block Diagram	8-1
	Chip Count And Power Consumption	8-1
	Types Of Memory Access	8-2
	Control PAL Device Description	8-6
	Conclusion	8-8
Chapter 9	Interleaved VDRAM	9-1
	Video DRAM Advantages	9-1
	Memory Features	9-2
	Interface Logic Block Diagram	9-3
	Memory Interface Logic Equations	9-6
	Intra-cycle Timing	9-25
	Inter-cycle Timing	9-29
	Parts List	9-35
	Final Discussion	9-35
Chapter 10	Single-Bank VDRAM	10-1
	Overview	10-1
	Memory Features	10-1
	Interface Logic Block Diagram	10-1
	Memory Interface Logic Equations	10-5
	Intra-Cycle Timing	10-20
	Inter-Cycle Timing	10-24
	Parts List	10-29
	Final Discussion	10-29
Chapter 11	Integrated Memory Interface Controllers	11-1
	V29BMC Burst Mode Memory Controller	11-1
	Score Peripheral Access Controller	11-4
	Score VME Interface Controller	11-4
	VLSI Technology ASIC Devices	11-5

LIST OF FIGURES

Figure 2-1	Three-Bus Architecture	2-4
Figure 2-2	VDRAM Main Memory	2-8
Figure 3-1	Memory Interface Overview	3-2
Figure 3-2	Simple Access With Bus Invalid	3-5
Figure 3-3	Single-Bank Instruction Access State Machine	3-6
Figure 3-4	Instruction Access With Burst And Terminate	3-7
Figure 3-5	Single-Bank SRAM Block Diagram	3-9
Figure 3-6	Instruction Access With Burst Suspension/Termination	3-10
Figure 3-7	Instruction Access With Suspended Burst	3-11
Figure 3-8	Mapped Instruction Space	3-12
Figure 3-9	Using A31 To Specify Code Space	3-12
Figure 3-10	ROM Space To Instruction Space	3-13
Figure 3-11	Data Access With Instruction Burst Termination	3-15
Figure 3-12	Burst Data Access To Instruction Space	3-16
Figure 3-13	Two-Bank Interleaved SRAM Block Diagram	3-17
Figure 3-14	Interleaved Instruction Access State Machine	3-20
Figure 3-15	Interleaved Instruction Access	3-21
Figure 3-16	Data Access State Machine	3-22
Figure 3-17	Data Byte Read/Write Access	3-23
Figure 3-18	Simple Data Access Block Diagram	3-24
Figure 3-19	Data Access With $\overline{B}iN\overline{V}$ And Burst	3-26
Figure 3-20	Burst Data Access Block Diagram	3-27
Figure 3-21	Interleaved SRAM Block Diagram	3-28
Figure 3-22	Simple Data Access Block Diagram	3-29
Figure 3-23	Single-Bank SRAM Block Diagram	3-30
Figure 3-24	Interleaved SRAM Control Equations	3-31
Figure 3-25	Interleaved SRAM Address Counter Equations	3-34
Figure 3-26	Simple Data Access Equations	3-36
Figure 3-27	Single-Bank SRAM Decode Control Equations	3-37
Figure 3-28	Single-Bank SRAM Address Counter Equations	3-38
Figure 3-29	Single-Bank SRAM State Control Equations	3-40
Figure 4-1	Access State Diagram	4-2
Figure 4-2	EPROM System Block Diagram	4-4
Figure 4-3	16-MHz Timing	4-5
Figure 4-4	Burst Address Counter Equations	4-5
Figure 4-5	Address Counter/Latch Equations	4-6
Figure 4-6	Address Latch Equations	4-7
Figure 5-1	Basic Memory System	5-2
Figure 5-2	Burst Mode Memory System	5-3
Figure 5-3	Dual-Bank Interleaved Memory System	5-5
Figure 5-4	Read/Write Memory With Combined Instruction/Data Buses	5-6
Figure 5-5	Addition Of Burst Mode Data Access	5-7
Figure 5-6	Static Column DRAM Memory System	5-9

Figure 6-1	System Block Diagram	6-2
Figure 6-2	Clock Diagram	6-4
Figure 6-3	State Machine Flow Diagram	6-5
Figure 6-4	$\overline{\text{BINV}}$ Critical Path Timing	6-7
Figure 6-5	CAS Critical Path Timing	6-7
Figure 6-6	Low-Cost Am29000 Processor Design	6-9
Figure 6-7	Clock Generator For Low Cost Am29000 Processor Design Pattern	6-20
Figure 6-8	Bus Controller For Low Cost Am29000 Processor Design	6-20
Figure 6-9	RAS And CAS Decoder For Low-Cost Am29000 Processor Design	6-22
Figure 6-10	Refresh Controller Pattern	6-23
Figure 6-11	Instruction Or Data Access	6-24
Figure 6-12	Refresh Cycle	6-25
Figure 7-1	Interface Logic Block Diagram	7-5
Figure 7-2	SCDRAM Memory State Diagram	7-6
Figure 7-3	AmPAL22V10-25 SCDRAM Refresh Counter/Request Generator Device U2	7-20
Figure 7-4	PAL16R6-D DRAM Refresh State Generator—Interleaved Device U15	7-21
Figure 7-5	PAL16R6-D DRAM Precharge State Generator—Interleaved Device U16	7-22
Figure 7-6	PAL20L8-B DRAM State Decoder—Interleaved Device U4	7-22
Figure 7-7	PAL20L8-B DRAM State Decoder—Interleaved Device U5	7-23
Figure 7-8	PAL16R4-D DRAM Instruction State Generator—Interleaved Device U17	7-23
Figure 7-9	PAL16R4-D DRAM Data State Generator—Interleaved Device U18	7-24
Figure 7-10	PAL16R6-D DRAM $\overline{\text{RAS}}$ Generator—Interleaved Device U19	7-25
Figure 7-11	PAL16R6-D DRAM $\overline{\text{CAS}}$ Generator—Interleaved Device U20	7-26
Figure 7-12	PAL16L8-B DRAM Counter Load—Interleaved Device U1	7-26
Figure 7-13	PAL16R4-D DRAM Address Counter—Interleaved Section 0—Even Bank Device U6	7-27
Figure 7-14	PAL16R6-D DRAM Address Counter—Interleaved Section 1—Even Bank Device U7	7-27
Figure 7-15	PAL16R4-D DRAM Address Counter—Interleaved Section 0—Odd Bank Device U9	7-28
Figure 7-16	PAL16R6-D DRAM Address Counter—Interleaved Section 1—Odd Bank Device U16	7-29
Figure 7-17	PAL16L8-D DRAM Row Address Latch—Interleaved Device U8	7-30
Figure 7-18	PAL16L8-D DRAM Row Address Latch—Interleaved Device U11	7-30
Figure 7-19	PAL16R8-D DRAM Write Enable Controls Device U112	7-31
Figure 7-20	SCDRAM Interleaved Bank Memory Decode Cycle	7-33
Figure 7-21	SCDRAM Interleaved Bank Memory $\overline{\text{RAS}}$ Cycle	7-33
Figure 7-22	SCDRAM Interleaved Bank Memory Burst Access	7-34

Figure 8-1	System Block Diagram	8-2
Figure 8-2	EPROM Instruction Access	8-3
Figure 8-3	Simple Instruction Access To DRAM	8-4
Figure 8-4	Burst Instruction Access To DRAM	8-5
Figure 8-5	Simple Data Access To DRAM	8-6
Figure 8-6	Burst Data Access To DRAM	8-7
Figure 8-7	Instruction Burst Pre-empted By a Data Access	8-8
Figure 8-8	Simple Instruction Access Followed By Data Access	8-9
Figure 9-1	Am29000 Processor With Interleaved VDRAM Memory	9-2
Figure 9-2	Interleaved VDRAM Memory Block Diagram	9-3
Figure 9-3	VDRAM Memory State Diagram	9-7
Figure 9-4	AmpPAL22V10-25 VRAM Refresh Counter/Request Generator Device U3	9-9
Figure 9-5	PAL20L8-B VRAM State Decoder—Interleaved Device U2	9-10
Figure 9-6	PALCE16V8-D VRAM Instruction State Generator—Interleaved Device U9	9-11
Figure 9-7	PAL16R4-D VRAM Data State Generator—Interleaved Device U10	9-11
Figure 9-8	PAL20L8-D VRAM Transfer Generator—Interleaved Device U13	9-12
Figure 9-9	PAL20R8-D VRAM RAS-CAS Generator—Interleaved Device U11	9-13
Figure 9-10	PAL20R4-D Byte-Write Enable Generator—Interleaved Device U12	9-14
Figure 9-11	PALCE16V8-D VRAM Address Incrementer Device U1	9-15
Figure 9-12	VDRAM Interleaved Bank Memory Decode Cycle	9-26
Figure 9-13	Row Address Timing	9-26
Figure 9-14	$\overline{\text{CAS}}$ -to-Data Ready Timing	9-28
Figure 9-15	NEC Memory Write Data Hold Time	9-29
Figure 9-16	Fujitsu Transfer Enable Timing	9-30
Figure 9-17	NEC Transfer Enable Timing	9-31
Figure 9-18	Burst Access Timing	9-31
Figure 9-19	VDRAM Instruction Burst Timing	9-32
Figure 9-20	VDRAM Data Read Timing	9-33
Figure 9-21	VDRAM Data Write Timing	9-34
Figure 10-1	Am29000 Processor With VDRAM Memory	10-2
Figure 10-2	Single-Bank VDRAM Memory Block Diagram	10-3
Figure 10-3	VDRAM Memory State Diagram	10-6
Figure 10-4	AmpPAL22V10-25 VRAM Refresh Counter/Request Generator Device U2	10-8
Figure 10-5	PAL20L8-15 VRAM State Decoder Device U1	10-9
Figure 10-6	AmpPAL22V10-15 VRAM Instruction State Generator—Single Bank Device U6	10-10
Figure 10-7	PAL20L8-10 VRAM Transfer Generator—Single Bank Device U7	10-10

Figure 10-8	PAL20R8-B VRAM RAS-CAS Generator—Single Bank Device U8	10-11
Figure 10-9	PAL20R4-B Byte Write Enable Generator—Single Bank Device U9	10-11
Figure 10-10	VDRAM Interleaved Bank Memory Decode Cycle	10-21
Figure 10-11	Row Address Timing	10-22
Figure 10-12	CAS-to-data Ready Timing	10-23
Figure 10-13	NEC Memory Write Data Hold Time	10-23
Figure 10-14	Fujitsu Transfer Enable Timing	10-25
Figure 10-15	NEC Transfer Enable Timing	10-25
Figure 10-16	Burst Access Timing	10-26
Figure 10-17	VDRAM Instruction Burst Timing	10-26
Figure 10-18	VDRAM Data Read Timing	10-27
Figure 10-19	VDRAM Data Write Timing	10-28
Figure 11-1	V29BMC-Based Memory System Block Diagram	11-2
Figure 11-2	V29BMC Configuration Word	11-4
Figure 11-3	Am29000 Processor-Based Laser Printer Controller Block Diagram	11-6

LIST OF TABLES

Table 6-1	16-Bit Architecture Parts List	6-26
Table 7-1	Am29000 Interleaved Dynamic RAM Interface Parts List	7-35
Table 9-1	Interleaved VRAM Interface Parts List	9-35
Table 10-1	Single-Bank VRAM Interface Parts List	10-29

PREFACE



The 29K™ Family of microprocessors changes the meaning of “high performance” for 32-bit CMOS Reduced Instruction Set Computers (RISC). First-generation RISC provided performance in the 4 to 5 million instructions per second (MIPS) range. But the 29K Family of three-bus RISC microprocessors (the Am29000™, Am29005™, and Am29050™ processors) can sustain performance in the 10- to 32-MIPS range.

The 29K Family brings high performance to a wide range of cost-sensitive applications ranging from laser printers to network bridges/routers and embedded controllers using DRAM or VDRAM (10 to 17 MIPS), to extremely high-performance graphic accelerators and multi-processor systems, using cache or SRAM (17 to over 32 MIPS).

The 29K Family of microprocessors gives the computer-system designer an entire spectrum of cost-effective system performance solutions using a single hardware and software platform. These microprocessors provide many features for easing the performance burden placed on system memory so slower, lower-cost memory systems can be used at any given level of system performance.

This handbook provides 29K Family memory system design information and specific examples helpful in determining how to design a memory system to give you the best cost/performance capabilities in the Am29000, Am29005, and Am29050 microprocessors. The designs shown in this manual illustrate memory interface examples using the 29K Family of three-bus processors. Since the Am29000, Am29050 and the Am29005 processors are pin-, bus-, and software-compatible, references to the Am29000 processor are interchangeable with the Am29050 and Am29005 processors. This manual does not provide examples for the Am29030™ or Am29035™ processors since these two devices are implemented with a two-bus architecture.

Chapter 1 summarizes the performance capabilities of the Am29000 32-bit CMOS microprocessor.

Chapter 2 contains basic information on memory system architectures and how to choose between them.

Chapters 3 through 11 explore memory system design options in detail, often providing detailed design examples. The types of designs and examples are:

- Chapter 3: The Design Process—SRAM Example
- Chapter 4: The Design Process—Simple EPROM Example
- Chapter 5: Connecting the Instruction/Data Buses
- Chapter 6: 16-Bit Memory Architecture
- Chapter 7: Interleaved SCDRAM
- Chapter 8: Single-Bank SCDRAM
- Chapter 9: Interleaved VDRAM
- Chapter 10: Single-Bank VDRAM
- Chapter 11: Integrated Memory Interface Controllers

In many applications, the simplest and most cost-effective method of interfacing memory with the Am29000 processor is to use an integrated memory controller device, such as the ones described in Chapter 11. In other applications, a custom-designed interface may be appropriate, as described in Chapters 3 through 10.

Application notes are available from your AMD® representative for many of the design examples presented in this handbook. The handbook contains basic, high-level information on the design examples, while the application notes provide both basic and detailed information (such as parts lists and performance benchmarks).

Additional information on the 29K Family of products can be obtained by calling the AMD 29K hotline number: 800 2929-AMD (800 292-9263) or 512 462-5651.



OVERVIEW

The Advanced Micro Devices 29K Family of three-bus, streamlined-instruction processors is a new generation of CMOS 32-bit, high-performance microprocessors. The Family is based on Reduced Instruction Set Computer (RISC) architecture principles, providing the ability to execute one instruction almost every clock cycle. The processors in the 29K Family provide the following features:

- A streamlined set of instructions, each of which can be executed in a single clock cycle. The instruction set is generally less complex than those of prior-generation processors, while still providing support for all the basic and most frequently needed algorithm steps. These simpler instructions serve to break complex algorithms down into a series of simple steps that are then exposed to powerful optimization techniques embodied in the latest generation of language compilers.
- An on-chip instruction cache and extensive register set, allowing fast execution by reducing the number of accesses to external system memory.
- A load-store method of access to external resources, often allowing parallel execution of internal (register-to-register) instructions and memory-I/O (register-to-external) instructions.
- Independent instruction and data buses that provide support for concurrent and continuous accesses of external instruction and data memory. Instruction memory can feed the processor with a new instruction in each cycle while the 29K Family memory bus simultaneously provides access to data operands.

Through the use of RISC techniques and the latest in advanced high-speed CMOS technology, the highest-speed 29K Family members are able to sustain performance of 23 to 32 Million Instructions Per Second (MIPS), with a peak of 40 MIPS, when clocked at 40 MHz. This is roughly equivalent to between 22 and 30 times the performance of a VAX 11/780.

PERFORMANCE/COST OPTIONS

If the designer's target is to sustain the highest possible level of performance, the memory system must be able to supply the microprocessor at a rate of one instruction per clock cycle. In that case, the memory-system architecture becomes a critical element in supporting the overall system performance, and also contributes significantly to the overall cost.

However, it is important to understand that the 29K Family members can also achieve very good performance in lower-cost designs. System costs are reduced by using DRAM, which has a far lower cost per bit than static RAM, and by using lower-speed, lower-cost 29K Family members such as the Am29005 processor. Performance in the 6- to 17-MIPS range can be achieved by using EPROM, static-column DRAM, or video DRAM, at clock rates in the 16- to 25-MHz range. Yet in this kind of lower-cost design, the system performance still far exceeds that of comparably priced prior-generation microprocessors, and even that of many current-generation RISC microprocessors.

The 29K Family members offer various levels of performance while sharing a common pin structure, bus structure, and instruction set, together with an extensive set of software tools for use in a wide spectrum of cost-effective, high-performance systems. The 29K Family thus provides a wide choice of performance at reasonable cost, without requiring a change in processor architecture or software.

MEMORY LATENCY AND PERFORMANCE

A processor capable of executing instructions at a rate of one per clock cycle must have a memory system that can sustain that rate of access. The key to high performance in a system is to provide burst mode access in the memory architecture. The memory system design will maintain high performance if it can sustain a burst access rate of one access per cycle, even if there is some initial access latency at the beginning of each burst access.

The 29K Family is designed to minimize internal execution-pipeline latency, while allowing the memory system as much latency as possible without loss of performance. Therefore, lower-cost and slower memory systems can often meet the system requirements.

Low-speed memory systems can use techniques such as pipelining and bank-interleaving to sustain the required burst access rate. In addition, burst mode access is intrinsically supported by modern dynamic-memory devices having the property of high-speed sequential access after a slower initial random-access time. Examples of these memory devices are: DRAM with page mode, nibble mode, static-column mode, or video (serial output) capability.

The allowance for initial latency is provided by a number of 29K Family features:

- For instruction accesses, the Am29000 and Am29050 processors contain an on-chip Branch Target Cache™ memory, which provides up to four cycles for the memory to begin supplying a sequential burst of instructions without incurring a performance penalty.
- For data accesses, the 29K Family members can overlap memory load and store operations with instruction execution, so memory latency occurs in parallel with continued instruction execution. The compiler or programmer can schedule a memory access in advance of when the data is required.
- Once data is read from the memory, it is forwarded directly to the execution stage for use in the next cycle. Again, this minimizes the internal pipeline latency to allow additional access time in the memory.
- The large register file (192 registers) of the Am29000 processor acts as an on-chip stack cache to help reduce the number of off-chip data accesses.
- The on-chip Memory Management Unit (MMU) in the Am29000 and Am29050 processors minimizes pipeline latency by making translated addresses available to the memory early in the cycle following execution. In addition, the MMU simplifies the memory design by performing the address-translation task on-chip.
- The 29K Family of three-bus microprocessors uses separate, non-multiplexed data and instruction buses to simplify the memory interface and to maximize the information transfer rate.



HOW TO USE THIS HANDBOOK

This handbook shows how to use the Am29000, Am29005, and Am29050 processors in a non-cache memory environment with standard, currently available memory devices. Examples of several specific memory systems are shown, often providing block diagrams, state diagrams, and PAL® device equations.

Chapter 2, *Basic Issues for Am29000 Processor Memory Designs*, provides basic information on memory system architectures and how to choose between them. Memory architecture options, key considerations, and trade-offs are introduced. Memory interface signals and other implementation details are described.

Chapter 3, *The Design Process—SRAM Example*, takes you through the process of deciding what type of architecture is best for your application. Although static RAM is used as an example, the basic principles explained in Chapter 3 apply to other types of memory as well.

It is recommended you read Chapters 1, 2, and 3 before you read the other chapters. Chapters 4 through 11 explore additional memory system design options in detail, usually providing detailed examples. You can read these chapters in any order or consult them as needed.

At the end of Chapter 3 is detailed information on two specific examples: a dual-bank interleaved SRAM memory, and a single-bank non-interleaved SRAM memory. SRAM memory is appropriate for systems where speed is important and memory size requirements are modest.

Chapter 4, *The Design Process—Simple EPROM*, shows a simple, low-cost instruction memory made with a single bank of fast EPROM.

Chapter 5, *Connecting the Instruction/Data Buses*, describes a form of memory architecture in which the instruction bus and data bus are tied together into a single bus. This architecture offers one method of trading performance for cost savings.

Chapter 6, *16-Bit Memory Architecture*, describes a memory organized into 16-bit words, rather than the usual 32 bits. Using a special set of clocks, 16-bit words are put together to form the 32-bit words used by the Am29000 processor. This scheme is useful in systems with moderate speed and memory size requirements.

Chapter 7, *Interleaved SCDRAM*, is a detailed design example using dual interleaved banks of Static Column DRAM (SCDRAM). In effect, a SCDRAM memory has a built-in cache consisting of one row of words. SCDRAM is appropriate for systems where performance and memory size requirements are important, combined with a need for lower cost and complexity.

Chapter 8, *Single-Bank SCDRAM*, is another SCDRAM design example. This low-cost design uses a single bank of non-interleaved SCDRAM. The intention of this design is to reduce the component count and power consumption to a minimum, while maintaining the high performance of single-cycle burst access to memory.

Chapter 9, *Interleaved VDRAM*, is a detailed design example using dual interleaved banks of Video DRAM (VDRAM). VDRAM memory allows independent and concurrent access through two ports: a conventional read/write random-access port (for the data bus), and a serial shift register port (for the instruction bus). VDRAM is appropriate for systems where simplicity and cost savings are important, and performance requirements are moderate.

Chapter 10, Single-Bank VDRAM, is another detailed design example similar to that in Chapter 9, but using a single-bank, non-interleaved VDRAM memory. Its complexity, cost, and performance are lower than the design in Chapter 9.

Chapter 11, Integrated Memory Interface Controllers, describes some integrated devices designed specifically for interfacing memory with 29K Family microprocessors. Although somewhat less flexible than a custom design, using an integrated controller is often the best solution because of the simplicity and reasonable cost of the interface.

Design Notes

Some of the design examples presented in this handbook are paper designs that have not been implemented in hardware by the authors. Although all designs have been thoroughly tested logically, they are not guaranteed to be error-free. They are presented in this handbook to show the methodology in designing memory systems for the 29K Family of microprocessors.

The SCDRAM and VDRAM designs in Chapters 7 through 10 have been functionally simulated on an Apollo workstation with Mentor CAD software. Behavioral models for memories, PAL devices, SSI and MSI logic, and the Am29000 processor were provided by Logic Automation. To the best of our knowledge and test vectors, we believe the SCDRAM and VDRAM designs work correctly.



BASIC ISSUES FOR Am29000 PROCESSOR MEMORY DESIGNS

The Reduced Instruction Set Computer (RISC) architecture of the 29K Family gives the user many more options in designing a memory system than a traditional Complex Instruction Set Computer (CISC) microprocessor. Built-in features in the 29K Family architecture, such as burst-mode addressing, allow faster execution out of relatively slow memory than most other processors. The use of these features are options, depending on performance needs. The memory system can be optimized for speed, low power, small board space, cost, or whatever is the key determining factor. In order to balance the trade-offs effectively, it is important to understand the processor interface to the memory system.

This chapter describes the memory access signals used by the processor, when the signals are used, and how. In addition, this chapter suggests some reasonable compromises that can be made in the memory design to meet specific application goals. In the actual design examples presented later, the design methodology is shown in detail.

KEY MEMORY SYSTEM FACTORS

There are several important factors to consider when designing a memory system. These factors include the memory access speed, memory size requirements, memory structure, design complexity, throughput requirements, and bus structure.

Access Speed

The main goal of using the 29K Family processors is to obtain a substantial performance improvement over other solutions, while maintaining or lowering the overall system cost. Unlike traditional microprocessors, the 29K Family offers a wide performance range depending on how the memory system is designed. Memory access speed is the key element in determining the performance limit of an Am29000 processor system. But there are two separate measures of access speed; the balance between them provides a wide range of performance-to-cost trade-offs.

The first measure of speed is how fast a random word of memory can be accessed; this is the initial access time. The second measure is how fast subsequent sequential words of memory can be accessed; this is the burst access time. The distinction between the two is important to understand.

The burst access time of the instruction memory system is normally tuned to the processor cycle time to allow single-cycle fetches during an instruction burst. Achieving a single-cycle burst instruction memory is the most important factor in achieving a high performance system.

In contrast, the initial access time applies only during the first non-sequential instruction or data fetch and is therefore of less importance. In addition, an instruction cache called the Branch Target Cache memory inside the processor hides the first cycles of the initial access time, so the initial latency in many designs in effect becomes invisible to the

processor. The combination of burst mode and the Branch Target Cache memory gives excellent performance characteristics, even when executing instructions in relatively slow DRAM.

The number of data loads and stores is minimized by an internal stack cache that has an image of the memory stack stored in registers. The registers are inside the processor and are therefore immediately accessible to all instructions being executed. Furthermore, the latest compilers have **early load generation** capability, where the compiler schedules loads as early as possible ahead of the first reference to the data. As a result, the data memory in many cases can be designed using only simple (rather than burst) access. The exceptions would be where very large amounts of data must be transferred quickly, as in DMA and in some graphics applications.

The initial access time is different from burst access time for the following reasons:

- When a new address is supplied by the processor, all bus devices must decode the address to determine whether or not to respond. So an initial access requires some time to decode the address and begin the access of a memory word.

A burst access is always to the next word in sequence after either an initial access or a previous burst access. Therefore, the burst access does not require any address decode time; the memory block already knows it is selected and only needs to increment the address from the last access. Note that the memory block does not need any special logic (i.e., added delay, to deal with the possibility of a burst access crossing memory chip or block boundaries because the Am29000 processor always supplies a new address at every 256-word address boundary).

- In the case of a memory block that recognizes its address, the selected word of memory must be accessed. Some memory devices like DRAMs require more time to access a random word of memory than to access a sequential word. This is generally due to time multiplexing the upper (row) and lower (column) halves of the memory address to the DRAM. Therefore, a random-word access requires both a row address and a column address.

A burst access needs only a new column address, or in some types of memories, only a signal to shift out the next sequential word. Thus, access to a sequential word is faster than access to a random location (new row and column address).

- When a new row is accessed, DRAM memories require delay time between the end of a previous access and the beginning of the new row access. This time is in addition to the delay time associated with transferring the new row address. This added delay is called the precharge time. When a random access immediately follows a previous access to the same memory, the new initial access incurs the precharge time delay. This delay is not incurred in a burst access because the same row is addressed.
- In a bank-interleaved memory system, the first access to each bank in a series gains no benefit from the overlapping of access time between banks. This is because all the banks must go through a full bank access time before the first (initial) word is available. Therefore, the initial access is always longer than subsequent burst accesses in an interleaved memory architecture. This concept is covered in more detail later.

Generally, an initial access is slower than a burst access due to the address decode, row-address entry, precharge delay, and initial bank access that may be required for an initial access, but do not apply to a burst access.

Memory Size

In a dedicated controller application, a few kilobytes of code and data space may be all that is needed. If so, the speed and simplicity of memory can be maximized by using Static RAM (SRAM). But if a few megabytes or more are required to handle a large embedded controller task, then the board space, power, and cost considerations usually favor DRAM over SRAM.

Memory Structure

Cost, power, and board-space considerations favor DRAM memory, while speed and simplicity considerations favor SRAM. Besides the two extremes of using only SRAM or only DRAM, there is also the option of mixing the two. Instruction memory may be built partly with SRAM, to provide fast access to some kernel routines, and the greater part with DRAM for economy. Or instruction memory may be built with SCDRAM, and the data memory built with a relatively slow type of SRAM, as described later in this chapter.

In addition, if performance is important, a multi-bank interleave access structure may be used. When using bank-interleave schemes, slower memories can achieve the same performance as a single bank of higher-speed memory during the critical burst-access mode. In the case of SRAM, it means less costly memories can still provide maximum burst performance. For DRAMs, it means these slower memories can still give maximum burst performance.

Where maximum speed is required along with large size, a compromise structure can be used with a little SRAM and a lot of DRAM. That option is called cache memory. A cache memory can be implemented, for example, as a **soft cache**, where the virtual tags are held in the TLB registers. As this is a software application, the details of such an application fall outside the scope of this book.

Complexity

The simplest memory system probably consists of one bank of EPROM for instructions and one bank of SRAM for data, with each bank capable only of simple (not burst) accesses. In a design such as this, there is virtually no control logic, no address decode logic, no buffers, and no refresh issues to deal with. Of course, this structure may not provide enough speed, flexibility, or memory size.

The other end of the complexity spectrum involves something like dual-interleave DRAM banks with burst access ability. Here, other considerations must be dealt with: refresh issues, bank sequencing, address counters, and dual porting of the instruction bank for both instruction and data accesses. Although this might seem complex, commercially available memory interface gate arrays now reduce all these design issues to a relatively easy task.

Throughput

Each 29K Family member is a synchronous machine. The timing of all its actions is in relationship to its clock. Information flow to or from the microprocessor must occur in time units that are integer multiples of the system clock cycle. This means if the memory access time does not fit into a single clock cycle, two cycles will be taken. Even if the access time only misses by a few nanoseconds, a whole cycle of time is lost. Depending on how often that situation comes up, it might be advantageous to slow the system clock down by a few nanoseconds so most of the memory accesses can occur

in a single cycle. Thus, the overall throughput of the system can be significantly improved in some cases by slowing the system down.

The option of slowing down the memory to match a slightly slower system clock can sometimes result in significant savings in cost and complexity. The best tool for finding the optimum cost-performance point is the architectural simulator available for the 29K Family members. This software simulator allows the designer to get a performance measurement of the application program, running the program with a simulated model of the processor and the memory system.

Bus Structure


The Am29000, Am29005, and Am29050 processors have three separate buses:

- Address Bus, shared between instruction, data, I/O, and coprocessor accesses;
- Instruction Bus, used to move instructions from the system memory to the processor; and,
- Data Bus, used to move data between the processor, system, memory, I/O devices, and coprocessors via load and store operations.

Together, these buses and their related control lines are called the channel. The channel provides concurrent access of instructions and data when the instruction and/or data memories are accessed via pipeline or burst requests. As shown in Figure 2-1, this structure, from a performance standpoint, favors memory systems with separate memory blocks for holding instruction and data for simultaneous access.

The instruction and data buses can be tied together to provide a system with a common instruction and data space. The benefit of doing this is a lower part count, as only one physical memory array is needed. The drawback is slightly less performance, because

Figure 2-1 Three-Bus Architecture

 

10623C-001

the processor cannot overlap instruction fetches with data operations. This option is described in more detail later. (See Chapter 5.)

The data bus is bidirectional, the address bus is **output only**, and the instruction bus is **input only** with respect to the Am29000 processor. When separate data and instruction memory blocks (in RAM) are used, the system design must provide a way to load the instruction memory, because the processor cannot directly write information into the instruction memory via the instruction bus. This is covered in more detail later in this chapter.

TRADE-OFFS

When attempting to determine the optimum memory system for a given application, there are a number of factors to consider. The real determining factor is usually one of cost, power, or board space. Some rough guidelines are given here.

Note that there are several types of integrated controller devices specifically designed to handle interfacing of DRAM and other types of memory with the 29K Family of processors. These devices often provide a simple and cost-effective method of implementing the memory system. See Chapter 11 for some examples of these devices.

SRAM

When building an embedded controller such as a network node processor, digital signal processor, or a mainframe-computer I/O processor, the main requirement is system speed. If the memory requirement is small (up to a megabyte or so), then high-speed SRAM works very well.

For small memory systems, the cost, power consumption, and board space of SRAM are reasonable, and the speed is the best possible. In a well-designed 40-MHz clock-rate system using the Am29050 processor, the initial access time is one to three cycles, the burst access speed is a single cycle, and the average sustained performance is in the 29- to 32-MIPS range. (Because of the internal caching in the processor, peak performance can reach up to 40 MIPS with any memory system, but it is the sustainable performance that counts.)

DRAM

SRAM designs provide the fastest initial access times. But SRAMs are not very dense and therefore consume a large amount of board space for a given size memory system. Also, they tend to be expensive and consume a good deal of power for a given size memory.

Dynamic RAMs can provide far more memory at lower cost and lower power in the available board space than is possible with SRAM. The main penalty for using DRAMs is a loss of speed in the initial memory access time. Burst-access performance can be maintained by using bank interleaving and Static Column DRAMs (SCDRAM). Fortunately, the Am29000 and Am29050 processors provide features that help compensate for a slower initial access time of system memory.

The Am29000 Branch Target Cache memory stores the first four instructions from the 32 most recently accessed branch target addresses. (The Am29050 Branch Target Cache memory operates in the same manner but is twice as large; instructions are stored from the 64 most recently accessed branch target addresses.) When a branch instruction is executed and the branch target address resides in the Branch Target

Cache memory, the first four instructions after the branch come from the internal cache. At the same time, the address of the first instruction following those in the cache is placed on the address bus. In effect, the first three cycles of the memory's initial access time (four cycles in the Am29050 processor) are hidden by the continued execution of instructions from the Branch Target Cache memory. Note: three cycles are saved in the Am29000 and Am29005 processors, rather than four, due to a cycle in which returning instructions must wait in the instruction prefetch buffer; in the Am29050 processor, instructions can bypass the prefetch buffer.

The Am29000 processor accesses virtually all its instructions in burst mode. This means the initial access time of the system memory can be amortized over multiple cycles of a burst access. This again lowers the penalty of a slower initial access time.

The large register file of the Am29000 processor provides a data cache for the most frequently used operands. This significantly reduces the number of times memory needs to be accessed for data as compared with what is required by most competitive microprocessors. Also, the Am29000 processor load and store operations may be overlapped with the execution of other instructions, which again reduces the impact of a slower initial access-time memory system.

As a result, DRAMs can significantly increase the size of system memory, while also improving system performance-to-price ratio. The cost per bit of memory in the system drops dramatically while performance is reduced only slightly.

SCDRAM

When building a large embedded controller, memory size is important, and typically, so is system speed. For this type of system, an architecture using Static Column DRAM (SCDRAM) offers cache-like performance but at a far lower cost and complexity than a SRAM cache.

An SCDRAM memory design using interleaved memory banks has an initial row access time of two to six cycles (depending on processor and memory speed), with single-cycle burst accesses. SCDRAM devices also provide a very important caching function. The static column capability means once a row is addressed for the first time, all subsequent accesses within that row can be made by simply changing the column address. Subsequent accesses to any address within the row will save the timing overhead of multiplexed row and column addresses. Random access within the row can occur in three cycles; subsequent burst accesses are single cycle.

In effect, the SCDRAM has a built-in cache with one row of words. The time required to do a complete cache re-load is the initial row access time.

This cache is put to best use when memory accesses tend to be sequential and localized, as they usually are for instruction memory. Also, many programs have data access patterns that benefit from the improved access speed within rows. Even when the accesses are not sequential, as long as the accesses remain local to one row of the memory, the initial access time is held down to three cycles, which is nearly what would be achieved with fast SRAM.

In a dual-bank interleaved SCDRAM memory using sixteen 1-Mbit by 4-bit SCDRAMs, the total memory size is 2M words (8 Mbytes), resulting from the two 1-Mbit by 32-bit memory banks. The cache size is 2K words (8 Kbytes), resulting from the two banks of memory, with a 1-kbit row cache in each memory device.

The Am29000 processor's large register file, independent instruction and data buses, overlapped load and store operations, and Branch Target Cache memory (in the Am29000 and Am29050 processors) are all key features that contribute to the 29K Family's high performance with low-cost DRAM memories.

Page Mode DRAM

In a fashion similar to SCDRAMs, page mode DRAMs can be used to allow cache-like performance by utilizing the faster access available within a page of memory. Page mode accesses are typically slower than static column accesses, so the performance of such a system is lower than a SCDRAM system. However, since all standard DRAMs support page mode accesses, this type of memory system is lower in cost than a SCDRAM system. The design can be made very simple by using special memory interface ASICs, specifically designed to be used with page mode DRAMs. An example of such a device is the V3 Corporation's V29BMC Burst Mode Memory Controller, described in Chapter 11.

Video DRAM (VDRAM)

For a simpler, medium-speed application, a Video DRAM (VDRAM) memory architecture may be appropriate. VDRAM does not quite have the same caching ability of the SCDRAM, but it does provide dual porting of a large common memory array.


One port of the VDRAM is a serial shift register that holds one row of bits from the internal DRAM array. A **by-4** organization memory has four shifters. This row is shifted out, providing consecutive memory words, just what the instruction bus of the Am29000 processor needs. The other VDRAM port is a bidirectional random-access bus permitting read or write operations on any word of the internal DRAM array. This is just what the data bus needs.

The two ports are controlled by a common address input of the VDRAM. As shown in Figure 2-2, that matches nicely with the common address of the 29K Family. Once the shifter port is loaded with a row of data, the shifter operation is independent of the internal DRAM array and the random I/O port. This permits simultaneous access to instructions and data by the processor.

Using the VDRAM, a single bank of fairly dense memory can serve both the instruction and data buses of the Am29000 processor in a very simple and efficient manner. The trade-off here is in speed. The initial access time for a VDRAM in a 25-MHz system is three to seven cycles, depending on the memory speed. The burst access speed for instructions can still be single cycle with a 25-MHz shift rate on the serial port. The burst access speed on the random I/O port is limited by the speed of page-mode access, which requires cycling of a column address strobe; data-burst accesses are three to four cycles each. This could be improved by bank interleaving.

Considering the simplicity and low cost of the VDRAM design, it still delivers respectable performance.

Figure 2-2 VDRAM Main Memory

 

VDRAMs:

- Allow simultaneous instruction fetch and data access from a common internal memory array.

10623C-002

MEMORY IMPLEMENTATION ISSUES

Once the overall architecture has been decided, it is important to get a good conceptual understanding of the interface between the processor and memory. The most important signals and the protocols used by the processor will be examined first.

Memory Control Signals and Protocol

The 29K Family has been designed to fully utilize the bandwidth of the memory system and hence ensure the system cost remains at a minimum. State-based bus signaling is used, greatly reducing the memory interface complexity normally associated with RISC processors. In order to achieve this level of simplicity, innovative and somewhat novel architectural features are incorporated. These features might appear complex at first and warrant some further explanation.

The 29K Family memory interface is **state** based. For instance, in the case of a system supporting only simple instruction fetches, the processor will start the instruction fetch sequence by providing an address and an active $\overline{\text{IREQ}}$ (Instruction Request) signal. The memory system responds, once it has obtained the required instruction, by returning an active $\overline{\text{IRDY}}$ (Instruction Ready) signal. The **state** based nature of the processor means then $\overline{\text{IREQ}}$ will simply stay active. In very simple terms, the interface signal edges have no meaning; the active state during the rising edge of the clock provides the meaning.

The processor therefore expects the memory system to track the state of the processor throughout the memory accesses. By far the simplest way of supporting this requirement is to implement the memory system control paths with a state machine.

Simple Access

The start of a simple (non-burst) access to instruction memory is notified by the $\overline{\text{IREQ}}$ signal going active. This signal also tells the memory system that a valid instruction address is on the address bus. The memory system, on seeing $\overline{\text{IREQ}}$ active, is expected to respond with an instruction word and assert $\overline{\text{IRDY}}$. This sounds very simple and in fact is. However, a few more signals are required for correct operation.

The Am29000 processor has several logical address spaces and distinguishes between the two possible instruction spaces by the signal IREQT (Instruction Request Type). This signal must be included and decoded as if it were an address line.

The final signal that must be monitored for a simple access is $\overline{\text{BINV}}$ (Bus Invalid). This signal, if active, is asserted in the second half of the first cycle of an initial access; it signals that the state of $\overline{\text{IREQ}}$ and the address are invalid, and the access must be ignored.

Instruction Burst Access

The Am29000 processor burst mode access mechanism takes advantage of the fact that instruction code is sequential in nature, usually with blocks of four to ten instructions executed in succession. A sequential block ends when a program branch occurs. The burst mode protocol allows single-cycle access to be easily achieved from a memory system, thus providing a cost-effective, high-performance solution.

The processor informs the memory system it would like to start a burst access by asserting $\overline{\text{IBREQ}}$ (Instruction Burst Request). Due to timing constraints, this signal is normally not usable until the second clock cycle of an access. However, this does not impose any problem, because most burst memory systems require a minimum of two clock cycles for the initial access. The signal is therefore normally captured in a register and the resultant signal used in the second cycle.

In order to support burst mode accesses, the addition of an address latch and an 8-bit counter is required. The latch and the counter provide the subsequent addresses to the memory system, rather than coming from the Am29000 processor. The exception to this are VDRAM systems where no counter is needed.

To sustain the burst, the memory system responds to $\overline{\text{IBREQ}}$ by asserting $\overline{\text{IBACK}}$ (Instruction Burst Acknowledge). Whenever the processor sees an active $\overline{\text{IBACK}}$, it assumes the memory system has accepted the initial address and hence will remove $\overline{\text{IREQ}}$, whether or not an $\overline{\text{IRDY}}$ has been supplied. (This sequence of events is very important to understand in order to correctly handle the situation described in the next paragraph.) In the cycle following the assertion of $\overline{\text{IBACK}}$, the processor releases $\overline{\text{IREQ}}$ and the address bus, freeing it to be used for other types of accesses.

As long as the processor outputs an active $\overline{\text{IBREQ}}$, it expects the burst to continue. If the processor's prefetch buffer becomes full due to a pipeline stall, the processor will request a temporary suspension of the instruction supply. This is signaled by the processor de-asserting $\overline{\text{IBREQ}}$. At this point, the $\overline{\text{IRDY}}$ signal must also be de-asserted following the completion of any outstanding access.

If $\overline{\text{IBACK}}$ is asserted throughout the suspension, then when the stall condition is removed, the processor will re-assert $\overline{\text{IBREQ}}$ and expect the burst to continue. If $\overline{\text{IBACK}}$ is de-asserted during the suspension, the burst is not restarted. Instead, the processor will inform the memory system of a new access by asserting $\overline{\text{IREQ}}$ with a new address.

The memory system has no way of knowing the difference between a suspended burst (stall) and a completed burst (branch). Therefore, it is recommended the signal $\overline{\text{IBACK}}$ be based on combinatorial logic using $\overline{\text{IBREQ}}$, the instruction burst state, and $\overline{\text{IREQ}}$, such that $\overline{\text{IBACK}}$ is forced inactive in the first cycle of a new access, when $\overline{\text{IREQ}}$ goes active. Forcing $\overline{\text{IBACK}}$ inactive causes the processor to keep $\overline{\text{IREQ}}$ and the address stable long enough for the memory system to capture the new address.

An instruction burst access may be preempted by de-asserting $\overline{\text{IBACK}}$. However, if $\overline{\text{IBREQ}}$ was active along with $\overline{\text{IBACK}}$ during the last cycle in which $\overline{\text{IRDY}}$ was active, or when no access is pending (such as when a suspended burst access is resumed by the assertion of $\overline{\text{IBREQ}}$), one last word of information must be transferred before the burst access is ended. That word can be transferred in the same cycle that the burst acknowledge is de-asserted or in some later cycle. Until it is transferred, the burst access is not complete and no new access of the memory may begin.

Data Burst Access

The sequence of events for data burst access is similar to that for instruction burst access. The corresponding memory interface signals are named $\overline{\text{DREQ}}$, $\overline{\text{DRDY}}$, etc.

Theoretically, the Am29000 processor always executes a Load Multiple or Store Multiple operation as a single contiguous burst access with no suspended access cycles. All information transferred during the Load or Store Multiple operation goes to or from the registers in the internal register file. In the actual Am29000 processor implementation, the Load and Store Multiple operations are executed as a burst of $n-2$ Loads or Stores with the first and the final (n th) Load or Store issued as simple accesses rather than as part of the burst. The result is that all data burst accesses begin with a simple access and are suspended one cycle before the end, and are immediately followed by a single, simple access cycle to complete the Load or Store Multiple operation. Following this rule, a Load or Store Multiple two cycles long is executed as two simple accesses in sequence. Depending on the state of the instruction pipeline, it is possible for an instruction fetch to occur between the suspended data burst access and the final data simple access. If the data burst access performance is critical, extra steps can be taken in the design of the memory or bus-interface logic to anticipate this behavior.

Pipeline Enable Signal

The Am29000 processor has separate but equivalent request and response control-line sets for instruction and data accesses. The exception to this rule is the Pipeline Enable ($\overline{\text{PEN}}$) signal. This response signal must be shared between all instruction and data accesses. Therefore, it is important to note that the only device that should drive the $\overline{\text{PEN}}$ signal in a given cycle is a device being selected by a valid address on the address bus (selected during a primary access). The $\overline{\text{PEN}}$ signal can be tied Low (active) if all bus devices will handle pipelined access, or tied High if all bus devices will not handle pipelined access.

Memory Response Control Signals

The following signals from the memory interface to the processor must be in a valid state at the end of each clock cycle: the ready signals $\overline{\text{IRDY}}$ and $\overline{\text{DRDY}}$, the error signals $\overline{\text{IERR}}$ and $\overline{\text{DERR}}$, the acknowledge signals $\overline{\text{IBACK}}$ and $\overline{\text{DBACK}}$, and the $\overline{\text{PEN}}$ signal. In systems with multiple memory control interfaces, each interface must be able to drive these response control signals. Only one memory interface can actively drive these signals in each clock cycle. As different memory interfaces are addressed by the



processor, the control over these signals must pass from interface to interface. This transfer of control must be accomplished within a single cycle to ensure the lines are valid on each cycle.

At a 25 MHz or faster cycle rate, it is very difficult to implement the transfer of control by selectively driving the control lines via three-state buffers as commonly done in slower memory systems. Wire ORing with open-collector drivers is also impractical.

The solution is to logically OR the respective control lines from each memory interface via an SSI logic gate such as a NOR or AND gate. Where there are several memory interfaces to be logically ORed, a PAL device such as the PAL16L8 may be used instead of SSI logic gates.

The “Late Show” Signals

Three memory control signals from the Am29000 processor arrive rather late in each clock cycle, requiring some special handling. The signals are $\overline{\text{IBREQ}}$, $\overline{\text{DBREQ}}$, and $\overline{\text{BINV}}$. The bus request signals are valid relatively late after the falling edge of the processor clock cycle (SYSCLK). The state of these signals is therefore best captured in a register, and used in the next clock cycle. As pointed out earlier, this does not impose any problems, because the signals are normally used only in the initial access when establishing a burst.

While the burst request signals are used only in a burst access system, $\overline{\text{BINV}}$ must be included as a qualification signal in all memory designs. In every Am29000 processor design, there are situations where the processor outputs $\overline{\text{BINV}}$ to indicate to the memory system that the other signals are not valid for that cycle. The easiest way to treat $\overline{\text{BINV}}$ is to design the memory interface logic to ignore either $\overline{\text{IREQ}}$ or $\overline{\text{DREQ}}$ when asserted, when $\overline{\text{BINV}}$ is also asserted.

The meaning of $\overline{\text{BINV}}$ applies only to the instruction or data bus access being started. $\overline{\text{BINV}}$ is always asserted during the first (and only) cycle of an aborted (canceled) access. Any burst or pipelined access already in progress in the unaffected portion of the channel is considered able to continue during the $\overline{\text{BINV}}$ cycle. In other words, if a data burst access is in progress (active or suspended) when an instruction access begins ($\overline{\text{IREQ}}$ is asserted), and $\overline{\text{BINV}}$ is also asserted late in the cycle, only the instruction access is canceled; the data access could continue, even transferring a word ($\overline{\text{DRDY}}$ active) during the cycle $\overline{\text{BINV}}$ is active.

Note that for all of these cases, the memory interface knows only that a burst access is preempted, terminated, or canceled when it sees a new access of the same type requested (instruction or data). When the processor preempts, terminates, or cancels a burst access, it simply makes the Burst Request signal inactive. To the memory interface, that action means only that the access is suspended, not necessarily ended. So the memory interface must continue to monitor and react to all the channel control signals.

$\overline{\text{BINV}}$ can become active in the following situations:

- When a Memory Management Unit (MMU) translated address is placed on the address bus to begin a new access and the processor recognizes the address is actually invalid due to a protection violation in the Translation Look-Aside Buffer. The new address is effectively canceled by $\overline{\text{BINV}}$ going active. $\overline{\text{BINV}}$ will appear with $\overline{\text{DREQ}}$ or $\overline{\text{IREQ}}$, depending on the type of access.

- When a jump instruction is immediately followed by another jump. The second jump instruction eliminates the need for any instruction following the first jump. This recognition causes the processor to cancel the memory access for instructions following the first jump by $\overline{\text{BINV}}$ going active.
- On a **partial hit** in the Branch Target Cache memory. This situation happens when the cache line contains a branch instruction in the first or second position in the cache. The processor will then cancel the planned access to instruction target + 4, an access which is no longer needed, by asserting $\overline{\text{BINV}}$.
- An internal or external trap is detected.
- Any combination of a load and/or store instruction directly following one another. The pipeline does not advance on the first instruction.
- When there is an unaligned data access and the TU bit is set in the Current Processor Status register.

Again, in these situations $\overline{\text{BINV}}$ is only defined to disrupt the access being started in the cycle that the signal is active. An access on the alternate bus continues even though $\overline{\text{BINV}}$ is active.

- $\overline{\text{BINV}}$ is also involved in the transfer of channel ownership. It goes active during the cycle when the processor releases control of all buses and control lines to another channel master requesting the channel. It also goes active during the cycle that the processor retakes control over the channel being returned to the processor by another channel master.

During the cycles that $\overline{\text{BINV}}$ is active in this situation, all the channel lines are in a state of transition. One channel master is putting its drivers into a high-impedance state and the other has yet to begin actively driving the channel. Therefore, there is no guarantee of what the logic levels on the channel might be, and all control lines and bus lines should simply be ignored while $\overline{\text{BINV}}$ is active. This condition is described in detail in the section below.

Using Another Bus Master

When a transfer of channel ownership occurs, the processor completes any simple access or suspends any burst access before $\overline{\text{BGRT}}$ (Bus Grant) is made active. This leaves any burst access in a state of suspension during the transfer of channel ownership. A suspended access in this situation is later preempted by the new channel owner beginning a new access of the same type as the suspended access. Or, if the new channel owner never requests an access of the same type as the suspended one, the suspended access is preempted by the original channel master after ownership is returned. This occurs when the suspended access is resumed by the original channel owner issuing the address of the point where the burst transfer was suspended. Again, note that until preemption occurs, a burst transfer is merely suspended from the memory view; this is a subtle but important point.

During the channel transfer when $\overline{\text{BINV}}$ is active, the state of the channel-control lines is not guaranteed. Situations where spurious information is detected as valid can be prevented simply by ignoring any channel-control signals during the time $\overline{\text{BINV}}$ is active during a transfer of channel ownership.

It is fairly difficult for a memory interface to clearly separate the first situation, a channel transfer, from the second, a canceled access request on only one channel bus. In the first, $\overline{\text{BINV}}$ active means all control signals must be ignored during the transfer of channel ownership. In the second situation, $\overline{\text{BINV}}$ active only cancels the access on the bus

requesting a new access. Control signals for the other bus can still be treated as valid and may affect the state of any access in progress. If the separation between these two situations cannot be clearly made, the memory-interface logic must be designed so $\overline{\text{BINV}}$ is always used as a signal to ignore any bus control or data signal during the cycle when $\overline{\text{BINV}}$ is active.

When $\overline{\text{BGRT}}$ first goes active, it indicates a transfer of channel ownership from the processor to another channel master. The first contiguous set of $\overline{\text{BINV}}$ active cycles to follow $\overline{\text{BGRT}}$ going active identifies a period when all channel signals should be ignored. When $\overline{\text{BINV}}$ goes inactive at the end of the channel-transfer sequence, a period begins during which any further assertions of the $\overline{\text{BINV}}$ signal indicate that only the access request being initiated with $\overline{\text{BINV}}$ asserted needs to be ignored. This period ends when $\overline{\text{BREQ}}$ first goes inactive, which indicates the return of control over the channel back to the processor. The first contiguous set of $\overline{\text{BINV}}$ active cycles to follow $\overline{\text{BREQ}}$ going inactive identifies another period during which all channel signals should be ignored. Following this period, any future assertions of $\overline{\text{BINV}}$ apply only to the request being started in conjunction with $\overline{\text{BINV}}$ going active, until $\overline{\text{BGRT}}$ again goes active to start the cycle over again.

All the above just gets more complicated if there is more than one channel master in the system which could gain control of the channel without the processor gaining control. In this case, the $\overline{\text{BINV}}$ recognition logic would have to keep track of all channel master $\overline{\text{BREQ}}$ and $\overline{\text{BGRT}}$ lines.

For all that effort, the savings would be one extra cycle of information transfer on an unaffected bus for each cycle $\overline{\text{BINV}}$ is asserted, if the unaffected bus is, in fact, ready to transfer information during the cycle. This savings would occur very infrequently. Therefore, it is best to simply define $\overline{\text{BINV}}$ as a signal defining an idle cycle for the entire channel. Design the memory system so no action (change of state) occurs as a result of any signal on the channel when $\overline{\text{BINV}}$ is active.

Memory Write Enable

For memories able to perform data-write operations in a single clock cycle, (e.g., CMOS static RAMs), the Write Enable (WE) signal to these memories must be a pulse occurring during the latter half of the write cycle. In general, an Am29000 processor has a short positive data hold time after the rising edge of System Clock (SYSCLK); refer to the processor data sheet for exact timing information. If the memory being used has a nonzero data-input hold time relative to the active edge of WE, then that edge must occur early enough for the processor to satisfy the memory-data-input hold time.

For most single-cycle memories, this situation implies SYSCLK is a convenient signal to use as a WE qualifying signal to ensure WE ends at the rising edge of SYSCLK. The delay of the final write-enable logic gate can then be masked by the propagation delay of a buffer on the data lines so at the memory, the WE signal ends at or before the time data goes invalid.

Byte and Half-Word Accesses

The 29K Family supports two modes of access to byte (8 bit) or half-word (16 bit) data elements. The mode selection is made via the Data Width (DW) bit in the configuration register (bit 5 in special purpose Register 3). The bit defines the data width as follows:

- When the DW bit is zero (the power up default mode), the data memory is assumed to have no data alignment hardware and will support only full word-wide (32 bit) write

accesses. When a write operation is performed, all four bytes of the word accessed are written.

- When the DW bit is one, the data memory is assumed to support individual write-enable control lines for each byte within a data word so partial word writes may be performed.

When used with the default mode (DW = 0), the memory interface logic provides only a single write-enable control. In this mode, the processor implements only full-word read and write operations on word-address boundaries directly in hardware. Access to a specific byte or half word within a word is provided by software instructions operating on internal registers.

This software approach to byte, half-word, and unaligned accesses provides a general-purpose mechanism for manipulating external byte and half-word quantities, without the requirement for special support hardware in the memory system. However, each byte or half-word access requires at least an additional cycle for extraction on a read operation and two or more cycles for the load, insert byte or half word, and store (i.e., read-modify-write sequence for a write operation).

To achieve full compatibility with existing and future commercially available software products such as operating systems, resident monitors, and application software, it is required that the memory system be designed to support byte writes (i.e., the processor mode where DW = 1). The memory system control logic must decode the Option (OPT) 0–2 lines and the lowest two bits on the address bus, and generate the correct enable signals to memory. When DW = 1, these codes control the alignment and masking of data on load operations and the selection of byte WE signals during store operations. The encoding of the OPT bits is shown in the *Am29000 32-Bit Streamlined Instruction Processor User's Manual* (#10620) or in Chapter 3 of the *Am29050 Microprocessor User's Manual* (#14778).

In mode DW = 1, a load selects a byte/half word from each addressed word based on the OPT 0–2 bits, the Byte Order (BO) bit, and the least-significant two bits of the address (for bytes) or the next-to-least-significant bit of the address (for half words). The selected byte/half word is placed right-justified within the destination register of the load. If the Set Byte Pointer (SB) bit of the load instruction is 0, the rest of the word is zero-extended. If the SB bit is 1, the rest of the word is sign-extended with the sign of the selected byte or half word.

A store operation, when DW = 1, replicates the low-order byte/half word of each source A register (SRCA) into every byte/half word position of each word written. It is the responsibility of the external memory to form the proper byte/half word write enables based on the OPT 0–2 bits indicating word, half word, and byte accesses, the two least significant bits of the address, and the implied byte order of the memory system. Note also the memory must not drive any of the data lines, even though some byte locations are not enabled for writing. That is, not being write enabled should not be misunderstood as permission to perform a Read operation, which drives data onto the data bus; the processor drives all the data lines.

If the DW bit is 1 and the SB bit of the load or store is 1, the Byte Pointer is set to the complement of the BO bit. This causes any subsequent extract or insert instruction to use the least-significant byte or half word of the specified register, thus ensuring compatibility with software written for the default mode of DW = 0.

Byte and half-word accesses with DW = 1 work as specified for a single load or store. An additional benefit is that byte and half word accesses may also be performed if the

Freeze (FZ) bit is set during execution of interrupt code, so these accesses may also be done during interrupt routines, as long as the interrupt-routine code does not rely on the value of the byte pointer. Extract and Insert instructions depend on the byte pointer, which is not updated during Freeze mode.

Software written for the DW = 0 mode runs in a system designed for the DW = 1 mode, but the reverse is not true. Software written (compiled) for a DW = 1 mode system will not run correctly in a system without support for byte-write enables. This requires that systems without byte-write enables use only code compiled for the DW = 0 mode. Therefore, it is strongly recommended that data memory systems for the Am29000 processor provide byte-write enables permitting the use of the DW = 1 mode of operation.

In either DW mode, word and half-word accesses not aligned on respective word or half word address boundaries can be accomplished via software trap routines executed when a non-aligned access is attempted.

Memory Error Signals

The Am29000 processor has error inputs ($\overline{\text{IERR}}$, $\overline{\text{DERR}}$) for both instruction bus and data bus accesses. These signals are only monitored by the Am29000 processor when an instruction or data access is pending. Therefore, if an error condition such as a parity error is to be reported, the appropriate error signal must be driven active at or before the time when the memory-ready ($\overline{\text{IRDY}}$, $\overline{\text{DRDY}}$) signals would normally go active. In some cases this may require that the memory access time be increased to allow time for error-detection logic to check the validity of the data.

An alternative to requiring memory-error signals to be valid with or before memory-ready signals is to use the WARN, TRAP0, TRAP1, or INTR0–INTR3 signals in a subsequent cycle to abort the affected process. Another alternative to extending the memory-cycle time, to allow time for Error Detection or Correction (EDC), is to add a pipeline stage to the memory access path. This would provide an entire cycle time to perform an EDC function, while increasing only the initial access time by one cycle. Subsequent burst accesses can continue to be single cycle.

Invalid Address Situation

If no valid bus device is addressed by a bus-access attempt, no ready response will ever be provided. This would cause a bus master to hang up forever, waiting for some response. It is therefore advisable to have some kind of time-out mechanism for bus accesses. If an invalid address is accessed by mistake, the time-out mechanism can end the access with an error response.

Access to Instruction RAM

As noted earlier, the 29K Family makes best use of memory systems containing separate instruction and data memories for simultaneous access to instructions and data. In a memory system with separate instruction and data memory blocks, design of the data memory block is straightforward. The memory data I/O pins are simply connected to the Am29000 processor data bus. All reading and writing of the data memory is done via the data bus. Access to the data memory can be by either the processor or any other bus master.

The instruction bus is designed to be used only for instruction fetches by the processor, and hence cannot be driven by the processor. Therefore, the instruction memory cannot be directly loaded (written) with information by the processor via the instruction bus in a manner analogous to the data bus.

Depending on the application, there might be a need to read from or write to the instruction memory as if it were data. Here are some of the ways to provide system access to the instruction memory:

- Buffers and some control logic can be added to the instruction memory so the processor can read information onto either the instruction or data bus. Using this configuration, the instruction memory can be both read and written via the data bus by either the Am29000 processor or another bus master. AMD has defined that $OPT2-OPT0 = 100$ is a data access of instruction ROM.
- A Direct Memory Access (DMA) controller with access to both the instruction and data buses could be used to request the channel from the processor, and could then access the instruction memory via the instruction bus. In which case, the instruction memory block would be exactly like the data-memory block. The system restriction is that the DMA controller would be the only means of writing information into the instruction memory.
- Dual-port memory such as a VDRAM could be used to build the instruction memory. One port of the memory, the video shifter port, provides read access for the instruction bus, and the other port provides read and write access via the data bus. This scheme has an additional benefit: the VDRAMs simplify the whole memory structure. Since the two ports share access to the same internal memory array, there is no need for an internal distinction between instruction and data information. The VDRAMs can be used to serve as both instruction and data memory within a single device. VDRAMs thereby support both the simultaneous access of instruction and data from a common memory array, and a data-bus access path to instruction memory.

Simple Dual-Bus, Single-Port Instruction Memory

The first method of accessing instruction RAM described above implements a simple dual-port access scheme for the instruction memory using buffers and arbitration logic. The arbitration logic resolves the contention between data and instruction accesses made to the same block of RAM.

This situation can occur when either the Am29000 processor or a DMA device in the system accesses the instruction RAM via the data bus. In each case, the interface logic is faced with a slightly different set of conditions as outlined below.

- If the processor is performing the data access, there can be a conflict with the processor's own instruction fetching activity. In this case, the data access is the result of instruction execution, and for program execution to continue, the data access must eventually complete. The data access request can occur during a burst-instruction fetch or an instruction fetch can occur during the data access if the data access is a burst request. If, at the time the data access starts, the processor is in the middle of an instruction access, the data access must be held off until the instruction access is completed or stalls. If an instruction fetch begins during a data burst request, the instruction fetch must be held off until the data access is completed.
- In the case of a DMA device access, the processor releases the bus to the control of the DMA device, so it is not possible for the processor to start an instruction fetch during burst-data accesses. But it is still possible for the DMA access to begin during

an already established (but suspended) instruction-burst request. Here again, the memory must be able to preempt the instruction-burst request and proceed with the data access.

Instruction Bus DMA

The second method of accessing instruction RAM described above requires hardware outside of the memory system. All access to the instruction memory is done for the processor by a DMA controller, specifically one that can access both the instruction and data buses. A DMA controller with this capability can request the processor to give up all the buses (address, data, and instruction) so the controller has complete access to all memory and I/O devices.

Once the controller owns the buses, there is no rule preventing it from both reading and writing information in the instruction memory via the instruction bus. As long as the instruction memory has been designed for read and write access via the instruction bus, there is no problem with a DMA controller performing these functions. By having access to both the instruction and data buses, the DMA controller can transfer information between I/O devices, instruction memory, data memory, and ROM.

In fact, if it can be assumed the DMA controller can move all the information to and from the instruction memory (including the performance of memory diagnostics), there is no reason for the instruction memory to have a second port for access to the data bus. In this case, the control logic and buffering of the instruction memory can be very simple, in fact, identical to that of the data memory.

True Dual-Port Instruction Memory

True dual-port memory used by the third approach, noted above, provides not only dual-bus access but also includes built-in structures that permit simultaneous access to the memory array from both the instruction and data buses. VDRAM is one very elegant and economical means to provide this type of memory. There are of course other true dual-port memories and dual-access memory controllers.

ADDRESS AND CONTROL DRIVER ISSUES

In high-speed memory designs for the Am29000 processor, the emphasis is on using the slowest memory possible while still achieving the necessary performance for high-speed systems. This means control logic and signal drivers must be the fastest available (i.e., 5–10 ns t_{pd} PAL devices are recommended for control logic devices above 25 MHz). It is also recommended that these devices directly drive the memory-address and control lines.

Directly driving the memories eliminates the added delay of separate buffers often used to drive memory-array signals. However, PAL devices generally have worst-case delay times specified for driving a 50-pF load capacitance. Often a memory array has 32 or more memory devices, each with an input capacitance of 5 pF to 10 pF. In addition, typical strip-line PC board traces add an additional 20 pF of capacitance and 100 to 200 nH of inductance per foot of trace length. Such a memory array can represent a capacitive load of 180–380 pF or more, and an inductive load of 100 nH or more. Therefore, the worst-case delay times for the affected PAL device outputs must be increased to account for the added load.

SPEED LIMIT

It can be useful to determine and analyze the limiting factors for memory speed. For any memory architecture, there are three signal paths with critical timing:

- The address to data-valid path during a read access
- The address to end-of-write path during a write access
- The channel master control signal active to response-signal-active path during any access

There are also two access cycles of interest: the initial access and the burst access. For this analysis, the channel master of interest is the Am29000 processor.

Address to Data-Valid Path

For the address to data-valid path in an initial access cycle, the memory system is subject to the following key parameters:

- Clock-to-processor address, data, and control signals valid
- Address control logic delay
- Memory access time
- Data bus buffer delay
- Data setup time

In a burst-access cycle, the same parameters are used, except the **clock-to-address and control signals valid** delay and the address control logic delay are replaced by the clock-to-output delay of the memory address counter.

Clock-to-processor address and control signals valid—During the first access to a non-sequential location in memory, the processor must provide a new address and instruction or data-request control signals to indicate a new memory request is being made.

Address control logic delay—Some memory designs must select between the initial address and the output of an address counter used for burst access cycles. The logic to select the address adds some delay, equivalent to the delay in the PAL device if such a device is used.

Memory access time—This is one factor the memory designer has some control over. The speed limit of the memory system is reached when this delay goes to zero.

Data bus buffer delay—In some cases, a buffer is used to isolate the memory-array outputs from the processor data bus. The propagation delay through the buffer must be considered.

Data setup time—The Am29000 processor requires some setup time for instructions and data.

The combination of the Am29000 processor address to data path delay and the data input setup time implies the initial access time will be two cycles for a maximum speed system.

In a burst-access cycle, the speed limit is set by the clock-to-output time of the address counter (t_{co} for the PAL device used), data-buffer delay, and the processor setup time. In a maximum speed system, burst accesses can be single-cycle from a single bank of

memory with the use of fast SRAMs. Bank interleaved memory can achieve single-cycle burst access with much slower memory.

Address to End-of-Write Path

For the address to end-of-write path in an initial access cycle, the memory system is subject to the following key parameters:

- Clock-to-processor address, data, and control signals valid
- Address/control logic delay, in parallel with data bus buffer delay
- Memory address and data setup time to write enable active

In a burst-access cycle, the same parameters are used, except that the **clock-to-address and control signals valid** delay and the address and control logic delay are replaced by the clock-to-output delay of the memory address counter. That means the clock-to-data-valid delay may predominate.

Clock-to-processor address, data and control signals valid—During the first access to a non-sequential location in memory, the processor must provide a new address and data-request control signals to indicate a new memory request is being made.

Data-bus buffer delay—In some designs, a buffer is used to isolate the memory-array outputs from the processor data bus. The propagation delay through the buffer must be considered. During an initial access this delay is masked by the address/control logic delay. During the burst access this delay adds to the data-valid delay.

Memory address and data setup time to write enable active—This is one factor the memory designer has some control over. The speed limit of the memory system is reached when this delay goes to zero.

Control to Response Path

For the control signal to response signal path, the time restrictions are the same in all access cycles. The key parameters are:

- Clock-to-output time of a register
- Propagation delay of a PAL device
- Propagation delay of a logic-OR gate on the response signals from each memory block
- Control-signal setup time of the processor

Exceeding the Limit

It is possible to build specially restricted memories that do not need the address/control logic or the data-bus-buffer, avoiding their associated delays. This is done by having only a single bank of memory for instructions or data. Then there is no need for address decoding or bus isolation. In this type of memory, the worst-case path delay involves the Chip Enable (CE) signal to memory, which is controlled by the system clock. Using the clock to control the CE signal eliminates bus contention between the processor and memory and possible false WE signals.

BANK INTERLEAVING

For high-speed designs, bank interleaving is a method of increasing the bandwidth of the memory system without the cost penalty of using fast memory devices.

A simple way to reduce the memory-access speed requirements by half or more is to make use of a bank-interleave memory architecture. In bank interleaving, one set of memories contains the even words and another set contains the odd words. The two banks are accessed on alternate clock cycles so each bank is allowed two cycles of access time. The banks alternately supply data words so there is one new data word available in each bus cycle. Of course, this scheme relies on sequential word accesses, which is exactly the nature of a burst access by the Am29000 processor. This scheme can be further extended to three, four, or more banks in order to further lengthen the allowable memory access time. The penalty is extended initial access time and increased complexity of the control logic. However, only the initial access requires the full delay of a two-cycle (or longer) access.

INSTRUCTION VS. DATA ACCESS SPEEDS

In the discussion of memories, a careful distinction has been made between the initial access and burst access times. This is important to help make the trade-off of memory-access speed and initial access time clear. Single-cycle burst access speed can be maintained even with rather slow memories, given the initial access speed can suffer. Where burst accesses are the predominant mode of memory access and where the bursts are relatively long, the initial access time can be amortized across many accesses. In this case, slow interleaved memory is ideal. But the more often a non-sequential access is done, the more the initial access time lowers the overall memory system performance.

Instruction accesses are always attempted in burst mode. Statistically **average** instruction streams branch every six to ten instructions. Therefore the initial access time of instruction fetches can be amortized over six to ten access cycles.

Burst access speed is thus important to instruction accesses. Further, the Branch Target Cache memory can hide up to three cycles of an instruction memory's initial access time when the target of the branch is in the cache. The **hit rate** of the Branch Target Cache memory is application-dependent, but typical hit ratios are 50% or more for the Am29000 processor, or 80% or more for the Am29050 processor. Thus the importance of burst-access time over initial-access time is further emphasized.

Data accesses are different because most are individual load or store operations. They are done more often as individual non-sequential reads or writes of single words. Burst accesses are usually done only at context switch time and during some procedure entries and exits. This means over 95% of data accesses are to non-sequential locations. Therefore, the initial access time is a much more important factor for data memories than for instruction memories.

In general, it is best to emphasize burst access speed in instruction memories and initial access speed in data memories.

TEST HARDWARE INTERFACE

Memory designs must account for the special needs of diagnostics hardware. The key issue is development systems will, at times, want to take control of buses and control lines in a system under test. In particular, to perform Reads and Writes of internal

registers of the Am29000 processor, a development system may want to masquerade as a system memory device during a diagnostic load or store operation so it can directly observe and control register values. Several emulators available on the market perform this function for the Am29000 processors.

The emulator operates as a system monitor and controller permitting logic-analyzer-like tracking of the Am29000 processor system activity. It is also able to insert diagnostic instructions into the normal processor instruction stream, read and write processor registers, and read and write system memory. The discussion below is general and applicable to all types of instruments the designer may want to use to debug the system. It may or may not be applicable to a certain vendor's emulator, so it is recommended that you consult the emulator vendor for a description of the access method used, and what considerations have to be taken when designing the memory system.

Taking Control

The emulator system must somehow indicate when it will take control of the signal lines from the system under test. There are two ways to do this: use pin 169 on the Am29000 processor's socket, or use a special code on the DREQT0–DREQT1 (Data Request Type) and the OPT0–OPT2 lines.

Pin 169 is the device-locator pin on the PGA package and is not electrically used by the processor. The prototype system under development can simply use the signal on pin 169 as a disable of the selection logic for all system memories. This ensures that when pin 169 is driven, the emulator system is free to take control of the prototype system buses.

The advantage of using pin 169 is that it is a simple, direct, and **pre-decoded** indication the emulator is taking control. The disadvantage is that it is not a consistent and intrinsic part of an Am29000 processor system. It requires that the system under test be modified to expect this special signal that will only come from specific development hardware. Recognizing the limitations of pin 169, AMD has defined another way to signal an emulator's use of processor system buses.

The combination of $DREQT1-DREQT0 = 00$ and $OPT2-OPT0 = 110$ is defined as the equivalent of the pin-169 signal. Under these conditions, the emulator controls the Instruction bus, Data bus, Ready, and Error lines, even though the address presented would appear to be directed at some other system device. The emulator uses this definition, referred to as an emulator access, when reading or writing the Am29000 processor's internal register. To do this, an emulator access load or store instruction is placed in the processor instruction register via the load Test instruction mode ($CNTL1-CNTL0$ lines = 00). When the load or store is executed, the DREQT and OPT codes appear on the bus and keep the system memory from responding while the development system directly moves data to or from the processor.

Note: Qualification by the DREQT code = 00 (instruction/data-type access) is required, since the OPT bits have other defined meanings for I/O and coprocessor access types.

The advantage of this scheme is that no **special** signal connections are required between the prototype and development systems. All communication is via the standard Am29000 processor's socket. Also, it may be possible to use decoding circuits already present for the DREQT/OPT bits to decode the needed signal equivalent to the pin 169 indication, thus saving on special-purpose hardware.

MEMORY DESIGN DOCUMENTATION

The remaining chapters of this handbook often include detailed system design examples, sometimes including block diagrams, schematics, logic equations, state diagrams, and parts lists.

Assumptions

In each of the memory design examples in this handbook, the following assumptions are made:

- Any system bus master observes the same bus protocol as the Am29000 processor. Protocol examples: new addresses are provided for each 1K byte boundary crossing; read and write operations may not be mixed within a burst transaction.
- Each memory monitors pin 169 of the Am29000 processor socket for interface with emulators or other test equipment, if needed.
- Memories drive memory response lines or data lines only when also driving memory Ready or Error signals. This ensures the memories do not contend with test hardware during diagnostic operations, since the processor will complete any pending memory access before entering the Halt or Single-step states preceding test instruction execution.

Boolean Notation

The Boolean equations in this handbook use the conventional Boolean symbols for identifying logic functions such as AND and OR. By way of review, the logic connectives for Boolean symbols are:

• = AND

+ = OR

The complement of a variable used in a Boolean equation is represented by an overbar above the variable. For example:

- The complement of X is \bar{X} . The complement of a variable is also referred to as the **negation** or **not** operation.
- **Double overbar** is used over a variable when a complemented variable is nested in brackets and the bracketed expression is also complemented. For example:

$$X = A \cdot B \cdot \overline{(\bar{C} + D)}$$

Programmable Array Logic (PAL device) Notation

Depending on the nature of the output signal being described, there are two basic types of PAL device-related equations used in this handbook: registered and combinatorial.

A registered equation shows the calculation of a PAL device output signal that is a function of the inputs and must pass through a register. Thus, the output signal is dependent on a clock (transfer) signal. A registered equation is usually identified by the special operator :=. For example:

$$X := A \cdot B + C$$

The combinatorial equation, on the other hand, shows the calculation of a PAL device output signal based only on the PAL device input signals. That is, the output signal is a time-delayed function of the inputs without any intervening state elements. A combinatorial equation is identified by operator =. For example:

$$Z = Q \bullet X + Y$$

THE DESIGN PROCESS—SRAM EXAMPLE



The 29K Family of microprocessors has been designed to make use of the full bandwidth available from the memory system, allowing simple, cost-effective, yet high-performance systems to be built. The simplest design for any microprocessor system is based on static RAM (SRAM). This chapter describes the design process that may be followed to produce an SRAM-based memory design. The basic principles, however, are applicable to other types of memory as well. With the assistance of examples, this chapter demonstrates the enormous range of system price and performance that the 29K Family provides.

INTERFACE DECISIONS

The Am29000 processor's state-based bus signaling ensures that the memory interface complexity normally associated with RISC processors is greatly reduced. In order to achieve this, innovative and somewhat novel architectural features have been incorporated. These features, while ensuring maximum performance, can appear a little strange at first and warrant further explanation.

The manner of this explanation will be to consider the various system options in turn, and choose a typical set for further investigation and detailed analysis. The subsequent design will then be developed to highlight the available implementation options and the reasons behind particular selections.


System Speed

The first, and somewhat obvious, decision is that of system clock speed. This is not such a simple question because the elements of cost and performance immediately become important issues. However, some simple guidelines are available that will allow a design to be started, and as the processor is cycle-based, this parameter can be changed. Assuming the speed is not fixed by other items, a gauge of performance can be formulated from the demonstrable fact that the performance of Am29000 processors is typically four to six times that of 32-bit CISC processors, even when using similar memory speeds.

Included with the AMD tools is an architectural simulator that allows memory speeds to be varied along with system clock speed for a particular piece of executable code. Hence, as the system architecture decisions are made, the effect on performance can be determined. This is particularly useful if an area of the application software is known to be time-critical. The design discussion throughout this chapter will assume 25-MHz operation is required, although discussion of critical timing areas will introduce ideas regarding slower clock speeds.

On reading the Am29000 processor data sheet, it can be seen that the processor has been designed such that the instruction and data buses are physically separate, although instruction and data space are logically the same.

Figure 3-1 Memory Interface Overview

 

10623C-003

Instruction Memory

The Am29000 processor is a RISC microprocessor, and as such demands an instruction every cycle. This therefore places a requirement on the memory system to supply a new instruction on each clock cycle. In traditional CISC-based systems, this requirement has been implemented using cache technology; while providing performance, the cost of such cache memory is not practical for most embedded applications. The Am29000 processor approach to provide a separate path for instruction flow allows a simpler, non-cache memory system to be implemented without complex multi-phase clocks, while minimizing system costs and maintaining high performance.

Traditionally, a cache is used because main memory is slow or must be shared in such a manner that the access bandwidth to the main memory is not consumed by a single user. (In this case, the users are the instruction fetch and data fetch state machines of the system processor.) The cache provides a fast-access copy of a limited portion of the main memory dedicated to one user (either instruction or data fetch), thus improving access speed and eliminating main memory accesses for frequently used information maintained in the cache. This is a good solution, but it usually comes at a high price, with expensive fast memories and additional control logic.

The Am29000 processor architecture allows the instruction memory to be completely separated from the main data memory. This is essentially what is done in most

computer systems anyway, since instructions are normally maintained in a separate area of memory, often in a different type of memory such as EPROM. The difference is that by physically separating instructions from data and giving each memory a private bus to the process, instructions can be fetched in parallel with data accesses, increasing system performance and eliminating the need to share bus bandwidth between instruction fetches and data accesses (via a common bus or from a common memory). This solves the information transfer bandwidth needs of a high-performance system without the expensive memories or complex control logic of a cache.

The Am29000 processor architecture allows high-speed memory access via a burst mode protocol. Burst mode provides a way to take advantage of the generally sequential nature of instruction execution such that lower-cost, lower-performance memories may be used in a high-performance system. In burst mode, one address is presented by the processor at the beginning of a burst access. The memory system then loads that address into a counter and increments the address for each successive instruction fetched. Since accesses in a burst are sequential, a simple bank interleaving approach in the memory design allows relatively slow memories to deliver instructions at the rate of one per clock cycle to the process.

The separate instruction supply path, combined with burst mode accesses to instruction memory, produces a high-performance, yet cost-effective system.

Note, however, that while burst mode protocol is a powerful technique for providing high performance at lower cost, burst mode support is not required. Many embedded systems have quite acceptable performance when executing instructions directly from EPROMs requiring multiple cycles for each instruction access. Burst and non-burst memory designs can be mixed in the system to optimize trade-offs between cost and performance.

The decision whether or not burst mode support should be used in a given memory system depends on the system performance required. System performance can be estimated by running representative code through different simulated memory systems via the Am29000 processor architectural simulator, a utility provided as part of the 29K Family software tool set.

In general, burst mode support becomes more important as the system clock frequency increases. Also recognize that the Am29000, Am29005, and Am29050 processor members of the 29K architecture family use three buses: an instruction bus, a data bus, and a common address bus. The common address bus significantly lowers the cost of 29K Family processors relative to RISC processors having dual address buses, but it does require that only a data or only an instruction address be provided in any one cycle. If burst mode is not supported, then the address bus can only be used for one type of access at a time, thus reducing the potential performance of the system. However, if burst mode is supported, the address bus is used only during the cycle that a burst access is started, thus freeing the address bus to be used in a data access in parallel with the instruction burst access.

It is therefore highly recommended that burst mode be supported for instruction memories to maximize system performance.

Data Memory

When burst mode instruction memory is supported, the Am29000 processor no longer requires the address bus to support instruction supply; this allows the data access mechanism to use the same address bus for both instruction and data accesses. The data addressing mechanism supports both simple accesses and burst mode accesses.

A data burst access loads to, or stores from, the registers within the processor. The Am29000 processor provides 192 registers for the complete software environment to use. Of these 192 registers, 128 are a cache of the run-time stack; it is the management of these registers that in most applications makes most use of the data burst facility.

The Am29000 processor uses a stack frame similar to that of CISC processors. However, in the case of the Am29000 processor, a window of the stack is cached in the local registers. During code execution, as the number of stack frames held in the processor vary, the executing code places two trap handlers into action, called **spill** and **fill**. The code in these trap handling routines starts the data burst mechanism in order to provide additional register space or to restore previously saved stack frames. Hence, the more varied the nesting level is during execution of the application code, the greater the number of spills and fills that occur. The result is to spread the cost of saving the registers (something performed by all processors) across many procedural call interfaces, improving code execution performance.

If a system includes a Real Time Operating System, and hence is likely to perform context switches, the internal state of the processor can be transferred to memory using a data burst. This burst transfer again ensures that, when needed, the full memory bandwidth is utilized.

The decision to provide data burst support is not as clearly defined as that of instruction accesses. The Am29000 processor overlaps LOAD instruction execution with internal instruction execution (for example, a LOAD and an ADD can execute in parallel). This means for regular data accesses the access time is often hidden by the concurrent instruction execution. Also, burst data transfer instructions are generally not generated by Am29000 processor compilers, except in special assembly code routines such as the spill and fill traps. Thus, the value of burst data access is very much dependent on the system code. In summary, burst access to data is a feature of limited value in typical applications.

INSTRUCTION MEMORY DESIGN

The Am29000 processor memory interface is typically designed as a state machine. For instance, in the case of a system that only supports simple instruction fetches, the processor starts the instruction fetch sequence by providing an address and an active $\overline{\text{IREQ}}$ (Instruction Request) signal. The memory system responds, once it has obtained the required instruction, by returning an active $\overline{\text{IRDY}}$ (Instruction Ready). The state-based nature of the processor means that if the following access is another instruction fetch, then $\overline{\text{IREQ}}$ will simply stay active. In very simple terms, the interface signal edges have no meaning; it is the active state at the clock edge that provides the meaning.

The processor therefore expects the memory system to track the state of the processor throughout the accesses. By far the simplest way of to meet this requirement is to implement the memory system control paths with a state machine.

The following design analysis and the subsequent detail assume the use of lower-cost memory devices. Thus, the design attempts not to break the **Am29000 speed record**, but to show how an Am29000 processor-based system can be produced quickly with very respectable performance at a reasonable cost.

Instruction Memory: Simple Access

The start of a simple access is signified by the signal $\overline{\text{IREQ}}$ going active. This signal also states that a valid instruction address is on the address bus. The memory system, on

seeing $\overline{\text{IREQ}}$ active, is required to fetch the requested instruction and place it on the pins, signaling this with an active $\overline{\text{IRDY}}$ signal.

The Am29000 processor has many logical address spaces, and in terms of instruction memory, supports two types: instruction/data and read-only. The distinction is provided by the signal IREQT (Instruction Request Type), and hence this must be included as if it were an address line in the address decode circuit. The signal IREQT, like the address bus, is only valid while $\overline{\text{IREQ}}$ is active.

Also, for simple accesses, $\overline{\text{BINV}}$ (Bus Invalid) must be monitored. If this signal goes active, it will do so only in the second half of the initial access clock cycle, indicating the $\overline{\text{IREQ}}$ and address are invalid for the cycle and the access must be ignored (Figure 3-2).


With this information on the memory interface signals, the **state machine** design can be started, and the condition that will take the Instruction Access State Machine into an instruction access state is:

$$\text{Instruction Access (IA)} = \text{Inst_Add} \cdot \text{IREQT} \cdot \overline{\text{BINV}}$$

$$\text{Instruction Memory Access (IMA)} = \text{IA} \cdot \overline{\text{IREQ}}$$

The Am29000 processor data sheet states that $\overline{\text{BINV}}$ is active 7 ns after the falling edge of SYSCLK; however, it also states that the setup time of $\overline{\text{IRDY}}$ is 12 ns. At 25 MHz, this leaves 1 ns to cancel the $\overline{\text{IRDY}}$ if single-cycle accesses are desired. The address and $\overline{\text{IREQ}}$ signal are active 14 ns after the rising edge of SYSCLK, which with an I Bus setup of 6 ns, leaves 20 ns to decode and access the instruction memory. These timing constraints require the use of a delay line or multiple clocks and different phases to

Figure 3-2 Simple Access with Bus Invalid

 


support single-cycle access. As will be discussed next, this level of complexity is not necessary for a high-performance design (17+ MIPS) using the Am29000 processor. So what about a design using two-cycle initial accesses?

Instruction Memory: Burst Access

Initially, it appears a two-cycle design will be slower and therefore less desirable. However, as already mentioned, the Am29000 processor provides support for burst mode instruction fetches. For example, it is often stated that typical code has non-sequential operations (e.g., jumps, calls, etc.) every six instructions or so on the average. If this is the case, then with single-cycle burst mode instruction fetches and a two-cycle initial access, the Am29000 processor will require seven cycles to execute six instructions. Hence, near-zero wait-state performance is achieved, which combined with the Branch Target Cache memory of the Am29000 processor, provides far greater cost/performance benefits.

Accepting a two-cycle initial access, we can start constructing the state machine. The IMA (Instruction Memory Access) condition will cause a transition in the state machine from the *idle* state to the *Istart* state. On the following clock, the transition will be back to *idle* and \overline{IRDY} made active (see the state diagram, Figure 3-3). This completes the simple access, and if another is required, then \overline{IREQ} will stay active (see the timing diagram, Figure 3-4) and the state machine will repeat the sequence.


Figure 3-3 Single-Bank Instruction Access State Machine

 

Note:

- Lowercase used to signify actual signals (i.e., *ibreq.d*)
- Instruction Access = $A[31] \cdot \text{Inst_Address} \cdot \overline{\text{ireq}} \cdot \overline{\text{binv}}$
- Instruction Memory Access = $IA \cdot Ireq$
- Instruction as Data Access = $A[31] \cdot \text{Inst_Address} \cdot \overline{\text{dreq}} \cdot \overline{\text{dreq}0} \cdot \overline{\text{dreq}1}$
- Instruction as Data Memory Access = $IDA \cdot \overline{\text{binv}}$

10623C-005

 Figure 3-4 Instruction Access with Burst and Terminate

The Am29000 processor provides a hardware error reporting mechanism for instruction fetches. Although this is not included in the general discussion, this mechanism can be easily added to protect from instruction fetches outside the implemented address range. In fact, it is a simple case of adding to the instruction address decode logic such that the signal $\overline{\text{IERR}}$ is asserted when an illegal address is provided by the processor. This action will cause the Am29000 processor to terminate the current request and take a trap to the installed error handler, which can be held in ROM or instruction/data address space.

The Am29000 processor provides support for in-circuit debuggers by allowing control of the processor using external pins (cntl1,0). Also, because the PGA package uses pin 169 only for alignment, some debuggers use this pin to inform the memory system it is accessing the processor and the signals should be ignored. Another mechanism is to assume the memory system is not driven when $\overline{\text{IREQ}}$ or $\overline{\text{IBREQ}}$ are inactive, hence allowing for surface mounted Am29000 devices to be controlled. In all cases where an in-circuit debugger is to be used, follow the debugger manufacturer's instructions to ensure the correct considerations are incorporated in the design.

INSTRUCTION MEMORY: SINGLE-BANK BURST ACCESS

The majority of application code executes sequentially between four and ten instructions before branching. The Am29000 burst mode access mechanism for instruction fetch

allows single-cycle access to be easily achieved from a memory system, thus maintaining a cost-effective, high-performance solution (see the block diagram, Figure 3-5).

State Machine: Single-Bank Burst Access

The processor informs the memory system it would like to start a burst by taking $\overline{\text{IBREQ}}$ active. This signal is one of the late signals, valid 14 ns after the falling edge of SYSCLK . This means the signal cannot be used much in the initial cycle unless multiple-phase clocks are used. However, as will be shown, this signal is not actually required in a two-cycle initial access system until the second cycle. Therefore, the signal only has to be captured by a register (see Figure 3-5), and the resulting registered signal $\overline{\text{IBREQD}}$ used throughout the design.

The addition of instruction burst is therefore very simple. A state called **Iburst** is added to the Instruction Access State Machine and the condition ibreqd is used to force the transition. In order to support burst mode, the addition of an address latch and 8-bit counter is required. The latch and counter combination provide the subsequent addresses to the memory system and provide a single-cycle supply of instructions.

The state machine, on seeing the IMA condition, will now transition from **iidle** to **istart** and set ILD active to load the address latch and counter. On the next cycle, if $\overline{\text{IBREQD}}$ is not active, the simple access cycle will complete as before. However, if $\overline{\text{IBREQD}}$ is active, then the state machine will transition to the state **Iburst** and provide an active $\overline{\text{IRDY}}$. In order to sustain the burst, the processor requires $\overline{\text{IBACK}}$ to be active (a form of handshake), and it is this transition that provides the $\overline{\text{IBACK}}$ signal to the processor (see the timing diagram, Figure 3-6).

It is a common mistake to assume $\overline{\text{IRDY}}$ is the $\overline{\text{IREQ}}$ acknowledgement. This is incorrect, for as soon as $\overline{\text{IBACK}}$ is active, whether $\overline{\text{IRDY}}$ has been supplied or not, the processor will remove $\overline{\text{IREQ}}$ and the address. In the design example being used, the signal $\overline{\text{IBACK}}$ is formed using combinatorial logic based on $\overline{\text{IBREQD}}$, the **Iburst** state, and $\overline{\text{IREQ}}$ to ensure this condition is handled properly.

The signal $\overline{\text{IBACK}}$, combined with the signal $\overline{\text{IBREQD}}$, can provide the signal $\overline{\text{ICOUNT}}$, which is used to increment the instruction address counter throughout the burst access.


Once the burst has started, the state machine will stay in the **Iburst** state until a new, non-sequential access is started. On each cycle, the $\overline{\text{ICOUNT}}$ signal increments the address counter and the state machine makes $\overline{\text{IBACK}}$ active and $\overline{\text{IRDY}}$ active, maintaining the supply of an instruction every cycle.

This continues as long as the processor requires sequential instructions. If the processor's prefetch buffer becomes full due to a pipeline stall, the processor will request a temporary suspension of the instruction supply. This event is signaled by the de-assertion of $\overline{\text{IBREQ}}$, which should signify the withholding of the $\overline{\text{IRDY}}$ signal. Once the stall condition has been removed and the prefetcher has space, the processor will signal for the instruction supply to be continued by re-asserting $\overline{\text{IBREQ}}$, hence allowing the $\overline{\text{IRDY}}$ signal to continue. In terms of the state machine, this demands the addition of a holding state to allow instruction fetch suspension (see the timing diagram, Figure 3-7).

If the suspension is not re-started but a new initial access is required, then the processor will inform the memory system by keeping $\overline{\text{IBREQ}}$ inactive and asserting $\overline{\text{IREQ}}$ with a new address.


Examination of the Instruction Access State Machine diagram (Figure 3-3) shows two conditions holding it in the state of **Iburst**. The first is $\overline{\text{IBREQD}}$ active, which continues

Figure 3-5 Single-Bank SRAM Block Diagram

 

10623C-007

Figure 3-6 Instruction Access with Burst Suspension/Termination

 

the instruction burst supply, outputting \overline{IRDY} , \overline{IBACK} , and \overline{ICOUNT} active. The other is the instruction supply suspended condition. When this is true, the state machine still maintains \overline{IBACK} active, but de-asserts \overline{IRDY} and \overline{ICOUNT} . The typical cause of instruction supply suspension is a data burst to data space. The burst takes many cycles and hence prevents the processor from continuing instruction execution. However, as soon as the burst is completed, instruction execution and supply can immediately continue at one per clock cycle.


From this description it can be seen instruction burst suspension and termination cannot be distinguished at the point \overline{IBREQ} is de-asserted. In fact, this can only be decided when either \overline{IBREQ} is re-asserted (continue) or \overline{IREQ} is asserted (new start).

Now that we have managed to produce the necessary state machine, we can investigate the system timing to determine any implementation constraints.

Instruction Timing: Single-Bank Burst Access

The initial access in a two-cycle simple access system has to decode and capture the address for the memory system. The Am29000 processor generates the address and related signals 14 ns after the SYSCLK rising edge. From this time, the memory system must identify the access as an instruction fetch to Instruction/Data memory and provide the ILD signal to capture the address.

Figure 3-7 Instruction Access with Suspended Burst

 

$$\text{Instruction Load (ILD)} = (\text{idle} \bullet \text{IMA}) + (\text{Iburst} \bullet \text{IMA})$$

The following cycle starts the memory access cycle and provides $\overline{\text{TRDY}}$ active to signify a valid instruction is available. If a typical latch/counter is assumed for the address, then the clock-to-output delay is around 8 ns. This, combined with an instruction bus setup time of 6 ns, leaves 26 ns to access the memory in a 25-MHz system. For this particular analysis, 20-ns SRAM is recommended, although in a 16-MHz system, this speed requirement would be greatly reduced to around 40 ns.

Write Access to Instruction Memory

The available in-circuit debugging systems and the simple target resident debug monitors use a specific instruction to set software breakpoints. If support for this form of breakpoint is required, then a mechanism for writing the specific instruction to instruction memory will need to be implemented. This mechanism also allows for code downloading, if required, by executing from ROM space while writing to instruction RAM space.

In order to support software breakpoints, the instruction memory must be able to accommodate data accesses to it. Typically, this is provided by defining a data bus memory map that places data space from 0–2 Gigabyte(s) and instruction space starting from 2 Gigabyte(s) up to the maximum address range of 4 Gigabyte(s). This makes the


determination of the address area simple, as it only requires that address bit 31 be included in the decoder. In other words:

Data Space = 0x00000000 to 0x7FFFFFFF

Instruction Space = 0x80000000 to 0xFFFFFFFF


Figures 3-8 and 3-9 show the mapping of the instruction spaces.

Figure 3-8 Mapped Instruction Space

 

10623C-010

Figure 3-9 Using A31 to Specify Code Space

 

10623C-011

This requires a modification of the original IMA equation such that two new conditions can be determined. These conditions are:

$$IMA = A[31] \cdot IA \cdot \overline{IREQ}$$


$$IDA = \overline{A[31]} \cdot Inst_Address \cdot DREQ \cdot \overline{DREQT0} \cdot \overline{DREQT1}$$

$$IDMA = IDA \cdot \overline{BINV}$$

This implies instruction memory does not exist at location zero, which may be of concern to some designers. However, the Am29000 processor starts execution from read-only instruction space (IREQT = 1) at location 0x0. Once the processor has been initialized and the software execution environment installed, code execution is usually continued by passing control to Instruction/Data memory space (see Figure 3-10). Therefore, it is not necessary to start SRAM instruction memory space at 0x0, and for debugging simplicity it is better not to map the various spaces (refer to Figures 3-8 and 3-9), as setting a breakpoint at 0x200, for example, would need knowledge of the mapping by the debugger (i.e., 0x200 instruction = 0x80000200 data).

The task of the instruction access logic is to provide for this type of data access mechanism, because only it is aware of the instruction memory state. Simply put, the data

Figure 3-10 ROM Space to Instruction Space

 

access cannot be allowed to be started while an instruction fetch is in progress, and therefore arbitration is necessary.

To provide support for the data access to instruction space, the state machine requires an additional state, **IDstart**. The condition **Instruction as Data Memory Access (IDMA)** must have a higher priority than **Instruction Memory Access (IMA)**, otherwise a **dead-lock** may occur. If instruction accesses had higher priority and an instruction burst was running, a data request into the instruction space would be ignored; then sooner or later the instruction burst would suspend, waiting for the data access to complete. This would not happen and the processor would stall indefinitely.

To simplify the explanation, it will be assumed data burst accesses will not be supported into instruction memory space. This means that only the **IDstart** state is required. (For cases where data burst into instruction space is required, refer to the timing diagram in Figure 3-11.) The support of **byte write** is also deferred until normal data access is discussed.

The Am29000 processor will not produce the condition where $\overline{\text{IREQ}}$ and $\overline{\text{DREQ}}$ are active at the same time because there is only a single address bus. It is therefore safe to assume the state machine accommodates the situation of simple instruction fetches and simple data accesses to instruction space. However, some additional thought is needed for the case of instruction burst fetches.

While the state machine is in the state **Iburst**, the burst should continue as long as $\overline{\text{IBREQD}}$ is active. However, in the case where $\overline{\text{IBREQD}}$ is inactive and the state machine is in the state **Iburst**, then the state must be held unless the burst is terminated by the condition **IMA** or **IDMA** becoming true. Another condition that must be accommodated is when an instruction request is made to a different instruction space. In this situation, the current instruction burst, if suspended, must be terminated; this is signified by $\overline{\text{IREQ}}$ active when the condition **IMA** is false (Figure 3-3).


In conclusion, assuming the processor is running an instruction burst, the data request will only be recognized when $\overline{\text{IBREQ}}$ is inactive. This mechanism ensures the prefetcher is full before the burst is terminated. Not allowing the data access to occur, and hence forcing the processor to stall, will cause $\overline{\text{IBREQ}}$ to be de-asserted. When this condition is recognized via $\overline{\text{IBREQD}}$, the signal $\overline{\text{IBACK}}$ should be de-asserted. The **IDMA** condition causes a transition to **IDstart** and $\overline{\text{IBACK}}$ inactive will terminate the instruction burst. During this state transition, **ILD** is asserted to load the address into the latch/counter combination. This allows the actual data access to be started in the following cycle, and once completed, will cause the processor to assert $\overline{\text{IREQ}}$ and start a new initial access. The condition of **BINV** must also be accommodated with the active $\overline{\text{DREQ}}$ signal, and if asserted, must hold the state machine in the **Idle** state and prevent the access from occurring. The full prefetcher will buffer the instruction stream such that if the data access was not an access to the instruction memory, then code execution can continue without delay, thereby minimizing the effect of the instruction stream restart.

Figure 3-12 shows the timing for a burst data access to instruction space.

INSTRUCTION MEMORY: DUAL-BANK BURST ACCESS

The Am29000 processor burst addressing mechanism has an additional benefit. It has removed the addressing restrictions occurring with standard CISC processors and has handed the addressing decisions to the designer.


Figure 3-11 Data Access with Instruction Burst Termination

 

Once the burst accesses have been started, the mechanism of single instruction supply does not concern the processor. This flexibility allows the designer to take advantage of innovative memory architectures and provide high performance, yet maintain realistic system cost. In the case of SRAM, this benefit can easily be realized by implementing the instruction memory as two or more interleaved banks.

The principle of interleaving is actually very simple. For example, the memory space can be divided into two blocks, one on even addresses the other on odd addresses. In the case of burst accesses, the memory is addressed in a sequential manner, so while one bank of memory is supplying the processor bus, the other is accessing the information required for the following access. Hence, by staggering the accesses, each bank in a two-bank system can take two cycles for each access, yet the overall effect is to supply information every cycle.

Figure 3-12 Burst Data Access to Instruction Space

 


Considering the two-bank system for this example, the cost is that the first access will, in most cases, take two cycles. In the case of the Am29000 processor, the latency of the first access is more than compensated by the ability to take advantage of single-cycle subsequent accesses. A typical two-bank memory SRAM system for the Am29000 processor uses two to three cycles for the initial access and requires very little additional logic compared to the single-bank memory system (compare the single-bank block diagram, Figure 3-5, with the two-bank block diagram on the next page, Figure 3-13).

Dividing the memory into two banks requires two counters so the odd and even banks can be addressed separately. The same high-order address bits still require only a single latch, as both banks are addressed within the same page area.

When using two counters, some additional logic is required to provide for instruction addresses requesting an initial access to the odd bank. Basically, if the first address is to an even word, then simply setting bit 2 will access the odd word. However, if the initial word is a word in the odd memory bank, then the even address must be incremented.

Figure 3-13 Two-Bank Interleaved SRAM Block Diagram

 

10623C-D15

First Access Even:

Even Address		Odd Address	Description
00000	→	00100	Set A[2] for Odd bank
01000	→	01100	Counter is A[3...9]
10000	→	10100	

First Access Odd:

Even Address		Odd Address	Description
00100	→	01000	Increment Even Count
01100	→	10000	Counter is A[3...9]
10100	→	11000	

Because the address lines A[0] and A[1] do not change, these are not connected to the memory and are only used to inform the control logic of partial word accesses. Also, as address line A[2] does not actually change, it need not be connected to the respective memory banks. In fact, the simplest mechanism to implement the two-bank memory system is to wire the top 7 bits of each counter to their respective memory banks. Then use address line A[2] from the initial address to signify which memory bank OE signal to start with, and then toggle the OE signals alternately for each bank.

This leaves the least significant bit of each counter to form the count-enable signal for each bank and hence cause each bank address to be incremented on every other cycle. Even though there are two banks, only one count-enable signal is actually required, that for the even bank address counter. The odd bank address counter only needs to copy the even counter's least significant bit each cycle, and if set to a 1, increment the count on the following cycle.

The even address incrementer then needs to be considered. The easiest method (and the one chosen here) is to allow three cycles for the initial access. The first cycle is used to decode and capture the address, the second to increment the even counter if needed and start the access, and the third to complete the access and supply the initial instruction.

Cycle	Odd Address	Even Address	Odd Counter	Even Counter
1	001-00	001-00	00-0	001
2	001-00	010-00	00-1	010
3	011-00	010-00	01-0	011
4	011-00	100-00	01-1	100
5	101-00	100-00	10-0	101
6	101-00	110-00	10-1	110
...				

The address lines A[0] and A[1] have been separated for clarity, as has the least significant bit of the Odd Counter. The Odd Counter is simply the least significant bit of the Even Counter delayed by a cycle. The Even Counter is a standard 8-bit counter that increments whenever the count-enable signal is active. The least significant bit of both the Odd Counter and Even Counter is used as output enables.

This compromise might seem to force a large reduction in performance. However, in the worst case this will mean six instructions executed in eight cycles for a typical burst of six instructions. With the Branch Target Cache memory accelerating frequent non-sequential operations, this will typically be reduced to around 6.5 cycles for six instructions on the average.

The performance has been maintained and the design is still very easy to implement. The choice of three-cycle first access also allows for cost reduction to be considered. As the decode can occur within the first cycle, and the first requested location address does not need to be incremented, there are two cycles available for the initial access. If we consider a 25-MHz design, this provides 80 ns to complete the memory access, which will allow 55-ns SRAM to be used, allowing for address generation and processor setup time.


Referring to the state diagram in Figure 3-14, it can be seen that the modifications to the single-bank memory system state machine are minimal. If the case of an instruction burst is considered as an example, then IMA initiates the access as with a single-bank system. The LD signal is set active during the transition from **lidle** to **lwait** (see the timing diagram, Figure 3-15). On the next cycle, the state machine will move on to **lstart**, and from there back to **lidle** if $\overline{\text{IBREQD}}$ is not active.

However, assuming $\overline{\text{IBREQD}}$ is active, the state machine will progress to **lburst**, $\overline{\text{IBACK}}$ is asserted, and the burst access starts as the single-bank memory system. Prior to a new instruction request, $\overline{\text{IBREQD}}$ will go inactive, and on the new IMA condition, the state machine will transition to **lwait**, capturing the address and starting a new access.

DATA MEMORY DESIGN

While the instruction and data space are the same as seen from the software, the Am29000 processor provides two independent hardware paths for instructions and data. This allows the accesses to operate concurrently and hence prevents code execution stalls caused by data accesses.

Figure 3-14 Interleaved Instruction Access State Machine

 

10623C-016

The data access mechanism is very similar to that of instructions. However, it is far simpler because the Am29000 processor does not require access suspension when performing a burst. In fact, as mentioned earlier, many designs do not require burst data access and only implement simple accesses.

When a simple data access is started, the processor is still able to continue to execute and fetch instructions. The load or store is actually overlapped with the code execution and, unless a register dependency is detected, will not cause the processor to stall. Therefore, in many cases, the actual latency of the data memory will not affect the performance of the processor. This is further enhanced by the processor implementing an internal 128-word stack cache, reducing the number of external data accesses.


Like instruction access, the following analysis avoids the use of very fast memories and multiple phase clocks, and while zero wait-state access may be attractive for performance reasons, it is not needed when using an Am29000 processor. As with instruction access, the performance is maintained, yet the memory performance is still realistic.

Data Memory: Simple Access

The processor expects the data memory system to track its state as with instruction accesses. However, this only requires a simple **two-state** state machine for simple accesses (see Figure 3-16).

The start of a simple access is signified by the assertion of \overline{DREQ} (Data Request), which states a data request is being made and the address and related signals are valid. The memory system is expected to respond with \overline{IRDY} active.

Figure 3-15 Interleaved Instruction Access

 


Interleaved Instruction Access: Simple, Burst (even1*), Terminate, Burst (add 1*), Suspend 10623C-017

Because the Am29000 processor has four address spaces, and three of these are related to data accesses, there are a few more signals that must be considered if correct operation is to be ensured.

When \overline{DREQ} is active, the processor supplies two signals to inform the memory system of the type of access required (DREQ0, DREQT1). From the Am29000 processor data sheet, the following table can be found:

DREQT1	DREQT0	Meaning
0	0	Instruction/Data Space
0	1	Input/Output Space
1	X	Am29027 Coprocessor Space

Many designs do not use the math coprocessor and do not place peripherals (i.e., serial I/O) in I/O space. In these types of designs, the DREQT0 and DREQT1 signals can be ignored by the external memory logic during any accesses. However, if \overline{DERR} (data

 Figure 3-16 Data Access State Machine

Note:

Lower case used to signify actual signals (i.e., dbreq.d)

DMA = Data Memory Access • $\overline{A[31]}$ • Data_Address • dreq • $\overline{dreq[1..0]}$ • \overline{binv}

10623C-018

error) processing is required, then the memory logic should recognize that DREQT1 and DREQT0 should both be low and generate an active \overline{DERR} signal if this is not true.

If the coprocessor is required, or at least considered as an option, the recommended method to determine whether it is present is to use the signal CDA combined with DREQT1 as follows:

- Coprocessor optional: Connect CDA to 0V via a 33K resistor. When DREQT1 = 1, ensure \overline{DRDY} and \overline{DERR} are inactive.
- Coprocessor never present: Connect CDA to 0V directly and ensure \overline{DRDY} and \overline{DERR} are inactive for a coprocessor store.

The Am29000 processor provides support for byte (8 bit) and half-word (16 bit) accesses, as well as word (32 bit) accesses. This support can be used in one of two ways. The simplest way, in terms of hardware, is to only support complete 32-bit word accesses and allow the software (via INBYTE, EXBYTE, etc.) to manipulate the partial word. This naturally produces additional instructions and will therefore affect performance.

The other method is to provide **byte-write** hardware support, and on setting up the processor, set the Configuration Register bit 5 (DW) to a 1. The Data Width Enable (DW) bit, when set, informs the processor to perform the necessary operations internally to support partial word accesses.

For example, in the case of a byte read, the processor will execute a load instruction with the option bits and address lines set accordingly. The memory system is expected to supply a complete 32-bit word and the processor will, on receiving the word, manipulate the specified byte into the correct position of the destination register. The case of a byte store is similar, except the processor will actually replicate the specified byte in all the byte positions of the provided 32-bit word and expect

the memory system to assert the relevant write enable (see Figure 3-17). Making the data memory byte writable is strongly recommended.

In simple terms, to provide efficient support of byte and half-word accesses, the hardware need only provide separate Write signals to the memory system. The processor supplies Option Control signals (OPT0-OPT2) and address lines 0 and 1 to allow the hardware to determine what is required. The address lines 0 and 1 state which byte or half-word is to be written to, and the OPT bits state which type of access is needed; these are only valid when $\overline{\text{DREQ}}$ is active. In other words:


OPT2-0	Meaning
000	Word (32-bit) Access
001	Byte Access
010	Half-Word Access

The other OPT bits define whether a data access to ROM is required (e.g., checksum access), or a debugger is accessing. These are not necessary requirements for all implementations and, in the case of a debugger, may differ slightly on the action required. So for this analysis, they have been excluded. Generally the conditions of $\overline{\text{DREQT1}}$, $\overline{\text{DREQT0}} = 0x00$ and $\text{OPT2-0} = 110$ signify that the $\overline{\text{DREQ}}$ active should be ignored by the memory system; the $\overline{\text{DRDY}}$ active signal will, in this case, be generated by the in-circuit debugger.

The overlapping of loads and stores with instruction execution allows the consideration of $\overline{\text{BINV}}$ to be incorporated easily without affecting performance. The condition of $\overline{\text{BINV}}$ has most significance for store operations, as the memory must not be affected. This involves preventing the write-enable signal from asserting until it is certain $\overline{\text{BINV}}$ is not going active. As stated in the case of instruction accesses, the signal $\overline{\text{BINV}}$ is only asserted during the initial cycle. Therefore, if a two-cycle data memory system is used, then $\overline{\text{BINV}}$ can be accommodated with ease.

In simple terms, the DMA condition will transition the Data Access State Machine from **Didle** to **Dstart**. If $\overline{\text{BINV}}$ is asserted during this initial cycle, then the condition DMA will not be satisfied and the transition will not occur. Once the state machine is in state **Dstart**, the memory system is sure the access is valid and may continue. This causes a

Figure 3-17 Data Byte Read/Write Access

 

10623C-019

transition from **Dstart** back to **Didle**, which provides the assertion of \overline{DRDY} and the respective write-enable if needed (determined by the processor signal R/\overline{W}).


The block diagram for the simple data access memory interface appears in Figure 3-18.

Data Memory: Single-Bank Burst Access

As the processor will hide the latency of data accesses by overlapping the load or store with instruction execution, the addition of burst mode support is not always necessary. Simulation of **typical** code execution will highlight the data bus activity, and unless the nesting levels of functions are deep and variable or a real-time operating system is in use, then the additional complexity can be avoided.

If the sequence **load,load** occurs frequently in simulation, an investigation into implementing pipelined accesses may be fruitful. Pipelined addressing allows the processor to use the address bus earlier, and is implemented by the external memory system capturing the current address. Therefore, in order to incorporate this mechanism, a

Figure 3-18 Simple Data Access Block Diagram

 

10623C-020

simple latch to capture the address and a small amount of control logic to provide \overline{PEN} are all that is necessary.

Assuming the decision is to include data burst access, then knowledge of the signal \overline{DBREQ} is required by the memory system. As with instruction burst, the signal \overline{DBREQ} will need to be held by a latch, and the latched signal \overline{DBREQD} will be used throughout the system.

The processor only attempts to start a burst if the instruction **loadm** (load multiple) or **storem** (store multiple) is executed. The length of the burst is determined by the setting of an internal register with length minus 1. The load and store multiple instructions only apply to the 192 user registers, and therefore the maximum transfer size is 192 words. However, the internal burst address counter field is 8 bits, so an actual burst address range of 255 words must be accommodated. Thus, as with the instruction memory, provision for burst data accesses is just a simple case of adding an 8-bit counter and address latch.

When the condition \overline{DMA} is valid, the Data Access State Machine (Figure 3-16) will transition from **Didle** to **Dstart** and assert \overline{DLD} to load the address counter and latch. If \overline{DBREQD} is not active on the next cycle, then the access will complete as a simple access. However, if \overline{DBREQD} is active, then the state machine will transition to the state **Dburst** and assert \overline{DRDY} and \overline{DCOUNT} , thereby starting the data burst.

The data burst mechanism is much simpler than that of instruction burst. Additional data accesses do not have to be accommodated, and neither do burst suspensions. If, for example, an interrupt occurs while the processor is performing a data burst, the processor will de-assert \overline{DBREQ} , which in turn will de-assert \overline{DBREQD} . In the case of data burst, this signifies a termination. The processor, once it has returned from the interrupt, will restart the burst from where it left off with a new \overline{DREQ} and address.

The state machine is therefore greatly simplified as the condition \overline{DBREQD} inactive while in the state **Dburst** can take the state machine straight to the state **Didle**.

This is not the complete story; a further performance enhancement can be added to accommodate an access immediately following the last burst access. Referring to the timing diagram in Figure 3-19, it can be seen, as the state machine is using \overline{DBREQD} , that the condition \overline{DREQ} active and \overline{IBREQD} inactive while in the state **Dburst** signifies a new data access. When this condition is recognized, instead of returning to the state **Didle**, the state machine can transition straight to **Dstart**.


Data Timing: Single-Bank Burst Access

Comparing the non-interleaved instruction memory block diagram, Figure 3-6, with the burst data access block diagram, Figure 3-20, it can be seen that the data memory system is an exact subset of the instruction memory system design. This simplifies the timing analysis greatly, as the work already done for the instruction memory system can be used directly for the data memory system.

Data Memory: Dual-Bank Burst Access

As with the Dual Bank memory system described earlier, the Am29000 burst addressing mechanism allows for system performance to be maintained while cost reductions are made. Again, the design for a dual bank data memory system is an exact subset of that for instruction memory. However, as burst suspension and additional accesses do not have to be accommodated, the logic can be simplified substantially.

Figure 3-19 Data Access with $\overline{\text{BINV}}$ and Burst

 

Simple and Burst Data Access, including $\overline{\text{BINV}}$


10623C-021

CONCLUSION

A common belief is that RISC microprocessors require expensive memory to provide high performance. This stems from the assumption that bandwidth is expensive. In fact, bandwidth is inexpensive; it is low latency that is expensive. This chapter has attempted to address these concerns and show the Am29000 processor allows the latency and bandwidth to be separated, providing access to some major system cost reductions. A few particular examples were chosen to illustrate that while the dependency on low latency, high bandwidth memories has been eased, the logic required to support these features is not complex.

After reading this chapter, the reader should be able to understand the decisions required before starting a system design. One of the more common configurations, a dual-bank interleaved SRAM memory, is described as an example below.

Figure 3-20 Burst Data Access Block Diagram

 

10623C-022

EXAMPLE SRAM DESIGNS — DETAILS


The equations for implementing SRAM designs in hardware are shown in this section for two designs described earlier in this chapter. Both designs have a two-cycle first access, single-cycle burst access instruction memory, and a two-cycle data access memory. The first design is a dual-bank interleaved SRAM implementation; the second design is a single-bank non-interleaved SRAM implementation.

Dual-Bank Interleaved SRAM Design

A dual-bank interleaved design was described previously in this chapter. A generalized block diagram of the design was shown in Figure 3-13.

The control logic for this design can be implemented in one MACH 110 device, as depicted in Figure 3-21.

Figure 3-21 Interleaved SRAM Block Diagram

 

10623C-023

The interleaved memory system requires two counters to supply the burst address. This part of the memory interface, like the control logic, fits into a single MACH 110 device. The required logic equations are shown at the end of this chapter.


The two independent paths for instruction memory and data memory used by the Am29000 processor allow performance to be maintained economically. The two separate paths allow concurrent accesses of data and instructions.

The block diagram of the data access circuit is shown in Figure 3-22. The required logic equations are shown at the end of this chapter.

Single-Bank Non-Interleaved SRAM Design

A single-bank design was described previously in this chapter. A generalized block diagram of the design was shown in Figure 3-5.

Figure 3-22 Simple Data Access Block Diagram

 


10623C-024

The control logic for this design can be implemented in a few PAL devices, as depicted in Figure 3-23. The required logic equations are shown at the end of this chapter.

The data memory design is the same as the dual-bank interleaved design (see Figure 3-22).

Figure 3-23 Single-Bank SRAM Block Diagram

 

10623C-025

Equations

The equations for implementing the SRAM design examples are shown in Figure 3-24 through Figure 3-29.

Discussion of the methods required to implement a two-cycle first access, single-cycle burst instruction memory system and a two-cycle data memory system are covered previously in the text.

The control logic can be contained in one MACH 110 device.

Figure 3-24 Interleaved SRAM Control Equations

CHIP cntrl_sram MACH110		
PIN	35	CLK
PIN	3	$\overline{\text{IREQ}}$
PIN	7	$\overline{\text{IREQT}}$
PIN	5	$\overline{\text{DREQ}}$
PIN	15,17	$\overline{\text{DREQ}}[1..0]$
PIN	24, 36, 37, 13, 32	$\overline{\text{A}}[31..27]$
PIN	9	$\overline{\text{P169}}$
PIN	33	$\overline{\text{IBREQ}}$
PIN	11	$\overline{\text{BINV}}$
PIN	25, 26	$\overline{\text{OPT}}[1..0]$
PIN	30, 27, 39	$\overline{\text{A}}[2..0]$
PIN	41	$\overline{\text{RW}}$
PIN	10	$\overline{\text{RESET}}$
NODE	26	WE
NODE	29	IME
NODE	27	DME
NODE	25	LD_FB PAIR LD
NODE	33	CNT_FB PAIR CNT
NODE	30	IBACK_FB PAIR IBACK
NODE	31	$\overline{\text{IBREQ_D}}$
NODE	23, 21, 19	$\overline{\text{Q}}[3..1]$
NODE	1	GLOBAL
PIN	31	$\overline{\text{LD}}$
PIN	43	$\overline{\text{CNT}}$
PIN	42	$\overline{\text{DEN}}$
PIN	28	$\overline{\text{TRDY}}$
PIN	38	$\overline{\text{XDRDY}}$
PIN	40	$\overline{\text{IBACK}}$
PIN	4, 2	$\overline{\text{OE}}[1..0]$
PIN	16, 14, 8, 6	$\overline{\text{WE0}}[3..0]$
PIN	21..18	$\overline{\text{WE1}}[3..0]$

10623C-026

Figure 3-24 Interleaved SRAM Control Equations (continued)

$$\begin{aligned}
 \text{STRING IDLE} &= \overline{Q[1]} \cdot \overline{Q[2]} \cdot \overline{Q[3]} \\
 \text{STRING IQ1} &= \overline{Q[1]} \cdot \overline{Q[2]} \cdot Q[3] \\
 \text{STRING IQ2} &= \overline{Q[1]} \cdot Q[2] \cdot \overline{Q[3]} \\
 \text{STRING IQB} &= \overline{Q[1]} \cdot \overline{Q[2]} \cdot Q[3] \\
 \text{STRING DQ1} &= \overline{Q[1]} \cdot \overline{Q[2]} \cdot \overline{Q[3]} \\
 \text{STRING DQ2} &= \overline{Q[1]} \cdot \overline{Q[2]} \cdot Q[3] \\
 \text{STRING DQ3} &= \overline{Q[1]} \cdot Q[2] \cdot \overline{Q[3]} \\
 \text{STRING IQ12} &= \overline{Q[1]} \cdot \overline{Q[3]} \\
 \text{STRING DQ12} &= \overline{Q[1]} \cdot \overline{Q[2]} \\
 \text{STRING DQ23} &= \overline{Q[1]} \cdot Q[3] \\
 \text{STRING IEXIT} &= (\text{IME} + \text{DME} \cdot \overline{\text{IBREQ_D}}) \\
 \text{STRING WEN} &= \overline{\text{OPT}[1]} \cdot \overline{\text{OPT}[0]} \\
 \text{STRING HEN0} &= \overline{\text{OPT}[1]} \cdot \overline{\text{OPT}[0]} \cdot A[1] \\
 \text{STRING HEN1} &= \overline{\text{OPT}[1]} \cdot \overline{\text{OPT}[0]} \cdot A[1] \\
 \text{STRING BEN0} &= \overline{\text{OPT}[1]} \cdot \text{OPT}[0] \cdot A[1] \cdot \overline{A[0]} \\
 \text{STRING BEN1} &= \overline{\text{OPT}[1]} \cdot \text{OPT}[0] \cdot A[1] \cdot A[0] \\
 \text{STRING BEN2} &= \overline{\text{OPT}[1]} \cdot \text{OPT}[0] \cdot \overline{A[1]} \cdot \overline{A[0]} \\
 \text{STRING BEN3} &= \overline{\text{OPT}[1]} \cdot \text{OPT}[0] \cdot \overline{A[1]} \cdot A[0] \\
 \text{IME} &= \overline{\text{IREQ}} \cdot \overline{\text{IREQT}} \cdot P169 \cdot \overline{A[31]} \cdot \overline{A[30]} \cdot \overline{A[29]} \cdot \overline{A[28]} \cdot \overline{A[27]} \\
 \text{DME} &= \overline{\text{DREQ}} \cdot \overline{\text{DREQT}[1]} \cdot \overline{\text{DREQT}[0]} \cdot P169 \cdot \overline{A[31]} \cdot \overline{A[30]} \cdot \overline{A[29]} \cdot \overline{A[28]} \\
 &\quad \cdot \overline{A[27]} \\
 \text{IBREQ_D} &= \text{CLK} \cdot \overline{\text{IBREQ}} = \overline{\text{CLK}} \cdot \text{IBREQ_D} \\
 \text{IBACK} &= \text{IQ2} \cdot \text{IBREQ_D} + \text{IQB} \cdot \text{IBACK_FB} \cdot (\overline{\text{IREQ}} + \overline{\text{IBREQ_D}} \cdot \text{DME}) \\
 \text{IBACK} &= \text{IQ2} \cdot \text{IBREQ_D} + \text{IQB} \cdot \text{IBACK_FB} \cdot (\text{IREQ} + \overline{\text{IBREQ_D}} \cdot \text{DME}) \\
 \text{IBACK} &= \text{IQ2} \cdot \text{IBREQ_D} + \text{IQB} \cdot \text{IBACK_FB} \cdot (\text{IREQ} + \overline{\text{IBREQ_D}} \cdot \text{DME}) \\
 \text{IBACK_FB} &= (\text{IBACK}) \\
 \text{LD} &= \text{IDLE} \cdot (\text{IREQ} + \text{DREQ}) \\
 \text{LD_FB} &= (\text{LD}) \\
 \text{CNT} &= \text{IQ2} + \text{IQB} \cdot \text{IBREQ_D} \\
 \text{CNT_FB} &= (\text{CNT}) \\
 \text{IRDY} &= \text{IQ2} + \text{IQB} \cdot \text{IBREQ_D} \\
 \text{DEN} &= \text{DQ12} + \text{DQ23} \\
 \text{XDRDY} &:= \text{DQ2} \\
 \text{Q[1]} &:= \overline{\text{BINV}} \cdot \text{IDLE} \cdot \text{DME} + \text{DQ12} \\
 \text{Q[2]} &:= \text{DQ2} + \text{IQ12} + \text{IQB} \cdot \overline{\text{IEXIT}} \\
 \text{Q[3]} &:= \overline{\text{BINV}} \cdot \text{IDLE} \cdot \text{IME} + \text{IQ1} + \text{DQ12} \\
 \text{OE[0]} &:= \overline{\text{BINV}} \cdot \text{LD_FB} \cdot \overline{A[2]} \cdot (\text{IME} + \text{DME} \cdot \text{RW}) + \overline{\text{LD_FB}} \cdot (\text{CNT_FB} ::= \text{OE[0]})
 \end{aligned}$$

Figure 3-24 Interleaved SRAM Control Equations (continued)

$$\begin{aligned} \text{OE}[1] &:= \overline{\text{BINV}} \cdot \text{LD_FB} \cdot \text{A}[2] \cdot (\text{IME} + \text{DME} \cdot \text{RW}) + \overline{\text{LD_FB}} \cdot (\text{CNT_FB} \text{ :+} : \text{OE}[1]) \\ \text{WE} &:= \overline{\text{BINV}} \cdot \text{IDLE} \cdot \text{DME} + \text{DQ1} \\ \text{WE0}[0] &= \text{WE} \cdot \overline{\text{RW}} \cdot \overline{\text{A}[2]} \cdot (\text{WEN} + \text{HEN0} + \text{BEN0}) \\ \text{WE0}[1] &= \text{WE} \cdot \overline{\text{RW}} \cdot \overline{\text{A}[2]} \cdot (\text{WEN} + \text{HEN0} + \text{BEN1}) \\ \text{WE0}[2] &= \text{WE} \cdot \overline{\text{RW}} \cdot \overline{\text{A}[2]} \cdot (\text{WEN} + \text{HEN1} + \text{BEN2}) \\ \text{WE0}[3] &= \text{WE} \cdot \overline{\text{RW}} \cdot \overline{\text{A}[2]} \cdot (\text{WEN} + \text{HEN1} + \text{BEN3}) \\ \text{WE1}[0] &= \text{WE} \cdot \overline{\text{RW}} \cdot \text{A}[2] \cdot (\text{WEN} + \text{HEN0} + \text{BEN0}) \\ \text{WE1}[1] &= \text{WE} \cdot \overline{\text{RW}} \cdot \text{A}[2] \cdot (\text{WEN} + \text{HEN0} + \text{BEN1}) \\ \text{WE1}[2] &= \text{WE} \cdot \overline{\text{RW}} \cdot \text{A}[2] \cdot (\text{WEN} + \text{HEN1} + \text{BEN2}) \\ \text{WE1}[3] &= \text{WE} \cdot \overline{\text{RW}} \cdot \text{A}[2] \cdot (\text{WEN} + \text{HEN1} + \text{BEN3}) \\ \text{OE}[0..1].\text{CLKF} &= \text{CLK} \\ \text{Q}[1..3].\text{CLKF} &= \text{CLK} \\ \text{XDRDY}.\text{CLKF} &= \text{CLK} \\ \text{WE}.\text{CLKF} &= \text{CLK} \\ \text{GLOBAL}.\text{RSTF} &= \text{RESET} \\ \text{GLOBAL}.\text{SETF} &= \text{GND} \end{aligned}$$

Figure 3-25 Interleaved SRAM Address Counter Equations

CHIP dual_cntr MACH110

PIN	35	CLK
PIN	10	\overline{LD}
PIN	11	\overline{CNT}
PIN	31, 28, 27, 4, 24, 33, 32, 13	A[9..2]
PIN	19, 18, 15, 14, 8, 7, 5, 3	QE[9..2]
PIN	42, 40 .. 36, 30, 29	QO[9..2]
NODE	22, 20, 18	AX[9..7]
NODE	1	GLOBAL

STRING AX3 '(A[3] :+: A[2])'

STRING AX4 '(A[4] :+: (A[3] • A[2]))'

STRING AX5 '(A[5] :+: (A[4] • A[3] • A[2]))'

STRING AX6 '(A[6] :+: (A[5] • A[4] • A[3] • A[2]))'

GROUP MACH_SEG_A QE[9..2]

GROUP MACH_SEG_B QO[9..2] AX[9..7]

;PRE-INCREMENT OF EVEN COUNTER

AX[7] = A[7] :+: (A[6] • A[5] • A[4] • A[3] • A[2])

AX[8] = A[8] :+: (A[7] • A[6] • A[5] • A[4] • A[3] • A[2])

AX[9] = A[9] :+: (A[8] • A[7] • A[6] • A[5] • A[4] • A[3] • A[2])

;EVEN COUNTER

QE[2].T := LD • ($\overline{A[2]}$:+: QE[2]) + \overline{LD} • CNT

QE[3].T := LD • (AX3 :+: QE[3]) + \overline{LD} • CNT • QE[2]

QE[4].T := LD • (AX4 :+: QE[4]) + LD • CNT • QE[2] • QE[3]

QE[5].T := LD • (AX5 :+: QE[5]) + \overline{LD} • CNT • QE[2] • QE[3] • QE[4]

QE[6].T := LD • (AX6 :+: QE[6]) + \overline{LD} • CNT • QE[2] • QE[3] • QE[4] • QE[5]

10623C-027

Figure 3-25 Interleaved SRAM Address Counter Equations (continued)

```

QE[7].T      := LD • (AX[7] :+: QE[7]) +  $\overline{\text{LD}}$  • CNT • QE[2] • QE[3] • QE[4] • QE[5] • QE[6]
QE[8].T      := LD • (AX[8] :+: QE[8]) +  $\overline{\text{LD}}$  • CNT • QE[2] • QE[3] • QE[4] • QE[5] • QE[6]
              • QE[7]
QE[9].T      := LD • (AX[9] :+: QE[9]) +  $\overline{\text{LD}}$  • CNT • QE[2] • QE[3] • QE[4] • QE[5]
              • QE[6] • QE[7] • QE[8]

QE[9..2].CLKF = CLK
;ODD COUNTER
QO[2].T      := LD • (A[2] :+: QO[2]) +  $\overline{\text{LD}}$  • CNT
QO[3].T      := LD • (A[3] :+: QO[3]) +  $\overline{\text{LD}}$  • CNT • QO[2]
QO[4].T      := LD • (A[4] :+: QO[4]) +  $\overline{\text{LD}}$  • CNT • QO[2] • QO[3]
QO[5].T      := LD • (A[5] :+: QO[5]) +  $\overline{\text{LD}}$  • CNT • QO[2] • QO[3] • QO[4]
QO[6].T      := LD • (A[6] :+: QO[6]) +  $\overline{\text{LD}}$  • CNT • QO[2] • QO[3] • QO[4] • QO[5]
QO[7].T      := LD • (A[7] :+: QO[7]) +  $\overline{\text{LD}}$  • CNT • QO[2] • QO[3] • QO[4] • QO[5] • QO[6]
QO[8].T      := LD • (A[8] :+: QO[8]) +  $\overline{\text{LD}}$  • CNT • QO[2] • QO[3] • QO[4] • QO[5] • QO[6]
              • QO[7]
QO[9].T      := LD • (A[9] :+: QO[9]) +  $\overline{\text{LD}}$  • CNT • QO[2] • QO[3] • QO[4] • QO[5] • QO[6]
              • QO[7] • QO[8]

QO[9..2].CLKF = CLK
GLOBAL.RSTF = GND
GLOBAL.SETF = GND

```

Figure 3-26 Simple Data Access Equations

CHIP Simple_Data_Control AmPAL22V10

PIN	1	SYCLK	COMBINATORIAL
PIN	2..4	A[31..29]	COMBINATORIAL
PIN	5	dreq	COMBINATORIAL
PIN	6,7	dreq[1..0]	COMBINATORIAL
PIN	8	xdrdy	COMBINATORIAL
PIN	9	rw	COMBINATORIAL
PIN	10	binv	COMBINATORIAL
PIN	12	GND	
PIN	11,13,14	opt[2..0]	COMBINATORIAL
PIN	15,16	A[1..0]	COMBINATORIAL
PIN	17	Q	REGISTERED
PIN	18	doe	COMBINATORIAL
PIN	19	drdy	COMBINATORIAL
PIN	23..20	we[3..0]	COMBINATORIAL
PIN	24	VCC	

```

STRING DATA_SPACE '(A[31])'
STRING READ          '(rw)'
STRING WRITE        '(rw)'
STRING Didle        '(Q)'
STRING Dstart       'Q'
STRING WEN          '(opt[2] • opt[1] • opt[0])'
STRING HEN0         '(opt[2] • opt[1] • opt[0] A[1])'
STRING HEN1         '(opt[2] • opt[1] • opt[0] A[1])'
STRING BEN0         '(opt[2] • opt[1] • opt[0] A[1] • A[0])'
STRING BEN1         '(opt[2] • opt[1] • opt[0] A[1] • A[0])'
STRING BEN2         '(opt[2] • opt[1] • opt[0] A[1] • A[0])'
STRING BEN3         '(opt[2] • opt[1] • opt[0] A[1] • A[0])'
STRING Data_Address '(A[30] • A[29])'
STRING DMA '(DATA_SPACE • Data_Address • dreq • dreq[0] • dreq[1] • binv)'
    
```

```

opt[0].TRST = GND
A[1..0].TRST = GND
Q.TRST      = VCC
doe.TRST   = VCC
drdy.TRST  = VCC
we[3..0].TRST = VCC
    
```

Figure 3-26 Simple Data Access Equations (continued)

$$Dstart := DMA \bullet Didle$$

$$drdy = Dstart + xdrdy$$

$$doe = DMA \bullet Dstart \bullet READ$$

$$we[0] = WRITE \bullet Dstart \bullet (WEN + HEN0 + BEN0)$$

$$we[1] = WRITE \bullet Dstart \bullet (WEN + HEN0 + BEN1)$$

$$we[2] = WRITE \bullet Dstart \bullet (WEN + HEN1 + BEN2)$$

$$we[3] = WRITE \bullet Dstart \bullet (WEN + HEN1 + BEN3)$$
A Non-Interleave SRAM Implementation

Covered in detail in earlier text is a decision about the methods required to implement a two-cycle first access, single-cycle burst instruction memory system and a two-cycle data memory system using single memory banks.

Instruction Memory Design

The control logic can be contained in a few PAL devices. The required logic is:

Figure 3-27 Single-Bank SRAM Decode Control Equations

PIN	1	\overline{IREQ}
PIN	2	\overline{IBREQD}
PIN	3	\overline{DREQ}
PIN	4	\overline{DBREQD}
PIN	5,6,7	A[31..29]
PIN	8	PIN169
PIN	9	IREQT
PIN	10,11	DREQT[1..0]
PIN	12	GND
PIN	13	$\overline{Q[1]}$
PIN	14	$\overline{Q[2]}$
PIN	15	LD
PIN	16	DTR
PIN	17	DEN
PIN	19	RW
PIN	20	\overline{IME}
PIN	21	\overline{DME}
PIN	22	\overline{CNT}
PIN	23	$\overline{Q[3]}$
PIN	24	VCC
STRING IDLE		$'(\overline{Q[1]} \bullet \overline{Q[2]} \bullet Q[3])'$
STRING IQ1		$'(Q[1] \bullet \overline{Q[2]} \bullet \overline{Q[3]})'$
STRING IQB		$'(\overline{Q[1]} \bullet \overline{Q[2]} \bullet Q[3])'$
STRING DQ1		$'(\overline{Q[1]} \bullet Q[2] \bullet \overline{Q[3]})'$
STRING DQB		$'(Q[1] \bullet Q[2] \bullet Q[3])'$

10623C-029

Figure 3-27 Single-Bank SRAM Decode Control Equations (continued)

$$\begin{aligned}
 \text{IME} &= \text{IREQ} \cdot \overline{\text{IREQT}} \cdot \text{PIN169} \cdot \text{A}[31] \cdot \overline{\text{A}[30]} \cdot \overline{\text{A}[29]} \\
 \text{DME} &= \text{DREQ} \cdot \overline{\text{DREQT}[1]} \cdot \text{DREQT}[0] \cdot \text{PIN169} \cdot \text{A}[31] \cdot \overline{\text{A}[31]} \cdot \overline{\text{A}[29]} \\
 \text{DEN} &= \text{EQ1} + \text{DEN} \cdot \text{DBREQD} \\
 \text{DTR} &= \text{RW} \cdot \overline{\text{DBREQD}} + \text{DTR} \cdot \text{DBREQD} \\
 \text{LD} &= \text{IREQ} \cdot (\text{IDLE} + \text{IQB}) + \text{DREQ} \cdot (\text{IDLE} + \text{DQB}) \\
 \text{CNT} &= \text{IQB} \cdot \text{IBREQD} + \text{DQB} \cdot \text{DBREQD}
 \end{aligned}$$

Figure 3-28 Single-Bank SRAM Address Counter Equations

CHIP Address_Counter AmpAL22V10

PIN	1	SYSCLK
PIN	2	$\overline{\text{CNT}}$
PIN	3	$\overline{\text{LD}}$
PIN	4..11	$\overline{\text{A}[2..9]}$
PIN	12	GND
PIN	15	$\overline{\text{Q}[2]}$
PIN	16	$\overline{\text{Q}[3]}$
PIN	17	$\overline{\text{Q}[4]}$
PIN	18	$\overline{\text{Q}[9]}$
PIN	19	$\overline{\text{Q}[8]}$
PIN	20	$\overline{\text{Q}[7]}$
PIN	21	$\overline{\text{Q}[6]}$
PIN	22	$\overline{\text{Q}[5]}$
PIN	24	VCC

$$\text{Q}[2] := \text{LD} \cdot \text{A}[2] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[2] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[2]$$

$$\text{Q}[3] := \text{LD} \cdot \text{A}[3] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[3] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[2] \cdot \text{Q}[3] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[2] \cdot \text{Q}[3]$$

$$\text{Q}[4] := \text{LD} \cdot \text{A}[4] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[4] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[2] \cdot \text{Q}[3] \cdot \text{Q}[4] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[2] \cdot \text{Q}[4] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[3] \cdot \text{Q}[4]$$

$$\text{Q}[5] := \text{LD} \cdot \text{A}[5] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[5] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[2] \cdot \text{Q}[3] \cdot \text{Q}[4] \cdot \text{Q}[5] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[2] \cdot \text{Q}[5] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[3] \cdot \text{Q}[5] + \overline{\text{LD}} \cdot \text{CNT} \cdot \text{Q}[4] \cdot \text{Q}[5]$$

10623C-030

Figure 3-28 Single-Bank SRAM Address Counter Equations (continued)

$$\begin{aligned} Q[6] := & \overline{LD} \cdot A[6] \\ & + \overline{LD} \cdot CNT \cdot Q[6] \\ & + \overline{LD} \cdot CNT \cdot Q[2] \cdot Q[3] \cdot Q[4] \cdot Q[5] \cdot Q[6] \\ & + \overline{LD} \cdot CNT \cdot Q[2] \cdot Q[6] \\ & + \overline{LD} \cdot CNT \cdot Q[3] \cdot Q[6] \\ & + \overline{LD} \cdot CNT \cdot Q[4] \cdot Q[6] \\ & + \overline{LD} \cdot CNT \cdot Q[5] \cdot Q[6] \end{aligned}$$

$$\begin{aligned} Q[7] := & \overline{LD} \cdot A[7] \\ & + \overline{LD} \cdot CNT \cdot Q[7] \\ & + \overline{LD} \cdot CNT \cdot Q[2] \cdot Q[3] \cdot Q[4] \cdot Q[5] \cdot Q[6] \cdot Q[7] \\ & + \overline{LD} \cdot CNT \cdot Q[2] \cdot Q[7] \\ & + \overline{LD} \cdot CNT \cdot Q[3] \cdot Q[7] \\ & + \overline{LD} \cdot CNT \cdot Q[4] \cdot Q[7] \\ & + \overline{LD} \cdot CNT \cdot Q[5] \cdot Q[7] \\ & + \overline{LD} \cdot CNT \cdot Q[6] \cdot Q[7] \end{aligned}$$

$$\begin{aligned} Q[8] := & \overline{LD} \cdot A[8] \\ & + \overline{LD} \cdot (Q[8] :+: (CNT \cdot Q[2] \cdot Q[3] \cdot Q[4] \cdot Q[5] \cdot Q[6] \cdot Q[7])) \end{aligned}$$

$$\begin{aligned} Q[9] := & \overline{LD} \cdot A[9] \\ & + \overline{LD} \cdot (Q[9] :+: (CNT \cdot Q[2] \cdot Q[3] \cdot Q[4] \cdot Q[5] \cdot Q[6] \cdot Q[7] \cdot Q[8])) \end{aligned}$$

Figure 3-29 Single-Bank SRAM State Control Equations

Chip State_Control AmPAL22V10

PIN	1	SYSCLK
PIN	2	\overline{IME}
PIN	3	\overline{DME}
PIN	4	\overline{IBREQD}
PIN	5	\overline{DBREQD}
PIN	6	RW
PIN	7,8	OPT[1..0]
PIN	9,10	A[1..0]
PIN	11	\overline{BINV}
PIN	12	GND
PIN	13	\overline{OE}
PIN	14	\overline{IRDY}
PIN	15,16	$\overline{WE[1..0]}$
PIN	17..19	$\overline{Q[3..1]}$
PIN	20	\overline{IOE}
PIN	21,22	$\overline{WE[3..2]}$
PIN	23	XDRDY ; "To be Or'd with Data DRDY!"
PIN	24	VCC

STRING IDLE ' $\overline{Q[1]} \cdot \overline{Q[2]} \cdot \overline{Q[3]}$ '
 STRING IQ1 ' $\overline{Q[1]} \cdot \overline{Q[2]} \cdot \overline{Q[3]}$ '
 STRING IQB ' $\overline{Q[1]} \cdot \overline{Q[2]} \cdot \overline{Q[3]}$ '
 STRING DQ1 ' $\overline{Q[1]} \cdot \overline{Q[2]} \cdot \overline{Q[3]}$ '
 STRING DQB ' $\overline{Q[1]} \cdot \overline{Q[2]} \cdot \overline{Q[3]}$ '
 STRING IEXIT ' $\overline{DME} \cdot \overline{IBREQD}$ '
 STRING WEN ' $\overline{OPT[1]} \cdot \overline{OPT[0]}$ '
 STRING HEN0 ' $\overline{OPT[1]} \cdot \overline{OPT[0]} \cdot A[1]$ '
 STRING HEN1 ' $\overline{OPT[1]} \cdot \overline{OPT[0]} \cdot A[1]$ '
 STRING BEN0 ' $\overline{OPT[1]} \cdot \overline{OPT[0]} \cdot A[1] \cdot A[0]$ '
 STRING BEN1 ' $\overline{OPT[1]} \cdot \overline{OPT[0]} \cdot A[1] \cdot A[0]$ '
 STRING BEN2 ' $\overline{OPT[1]} \cdot \overline{OPT[0]} \cdot A[1] \cdot A[0]$ '
 STRING BEN3 ' $\overline{OPT[1]} \cdot \overline{OPT[0]} \cdot A[1] \cdot A[0]$ '

$$IRDY = IQ1 + IQB \cdot IBREQD$$

$$IOE = IQ1 + IQB + RW \cdot (DQ1 + DQB) + IOE \cdot DBREQD$$

$$XDRDY := DQ1 + DQB \cdot DBREQD$$

10623C-031

Figure 3-29 Single-Bank SRAM State Control Equations (continued)

$$Q[1] := \overline{BINV} \cdot IDLE \cdot IME + IQ1 \cdot IBREQD + IQB \cdot \overline{EXIT}$$

$$Q[2] := \overline{BINV} \cdot IDLE \cdot DME + DQ1 \cdot DBREQD + DQB \cdot DBREQD + DQB \cdot DME$$

$$Q[3] := IQ1 \cdot IBREQD + IQB \cdot \overline{EXIT} \cdot \overline{IME} + DQ1 \cdot DBREQD + DQB \cdot DBREQD$$

$$WE[0] = \overline{RW} \cdot DQ1 \cdot (WEN + HEN0 + BEN0) + WE[0] \cdot DREQD$$

$$WE[1] = \overline{RW} \cdot DQ1 \cdot (WEN + HEN0 + BEN1) + WE[1] \cdot DBREQD$$

$$WE[2] = \overline{RW} \cdot DQ1 \cdot (WEN + HEN1 + BEN2) + WE[2] \cdot DBREQD$$

$$WE[3] = \overline{RW} \cdot DQ1 \cdot (WEN + HEN1 + BEN3) + WE[3] \cdot DBREQD$$



THE DESIGN PROCESS— SIMPLE EPROM EXAMPLE

This chapter describes a simple low-cost interface between the AMD Am29000 processor and a standard EPROM instruction memory. Two to three standard PALCE16V8H-D PAL devices are employed to deliver single-cycle burst access at 16 MHz (62.5 ns clock period) using 45-ns EPROM. Using the same design architecture, single-cycle burst access performance can also be achieved at 20 MHz (50-ns clock period) using 35-ns EPROM.

BACKGROUND

The low cost and high performance of the Am29000 processor contribute to its effectiveness as an embedded control processor. A key element of its strength is its burst mode address capability. Since the Am29000 processor is capable of executing its instructions in a single clock, issuing instructions at that rate is a definite advantage.

Because instruction execution tends to be sequential in nature, it is not necessary for the processor to issue a new address on every cycle. It is better to use an address counter and simply increment it on each access. This avoids the address output delay time of the microprocessor. Instead, there is only the delay of the counter output, t_{co} .

As an example, the address valid output delay of the 16-MHz Am29000 processor is 16 ns, while t_{co} of the PALCE16V8H-D, used as the address counter, is 8 ns. With the 8-ns savings, a slower, less costly memory may be employed. The Am29000 processor is capable of burst lengths up to 256 instructions; the upper address lines are latched. Therefore, implementing an 8-bit counter in the PAL device is sufficient.

Another advantage of burst mode addressing is that with the counter and latches providing instruction address, the processor address bus is free for data transfers. The performance of a four-bus Harvard architecture (with separate instruction and data buses) is then realized with the reduced pin count of three buses.

EPROM MEMORY DESIGN ASSUMPTIONS

Some general assumptions are made for this design that are valid for a variety of embedded control applications:

1. EPROM is the only instruction memory in the system. This assumption simplifies the address decoding and chip select logic.
2. There is no path from the data bus to the instruction bus.

This assumption simplifies the memory architecture, but if an emulator is used for software development, it must have overlay memory capability. Emulators of this type are readily available.

DESIGN DESCRIPTION

A complete instruction memory can be achieved using only two or three low-cost PAL devices and four EPROMs. The design can be partitioned into three blocks: state

machine, address counter, and address latch. The counter is divided between two PAL devices, one also containing the state machine, the other containing address latches. A third PAL device serves as a latch for the upper address lines to support 128K words (512K bytes) of EPROM instruction memory. For memory systems requiring less than 2K words (8K bytes), the third PAL device can be omitted.

Signals used from the Am29000 processor are $\overline{\text{IREQ}}$, $\overline{\text{IBREQ}}$, $\overline{\text{IBACK}}$, $\overline{\text{IRDY}}$, and $\overline{\text{BINV}}$. All are active-low signals. Refer to the 29K Family Data Book for a more detailed description of 29K Family signals.


$\overline{\text{IREQ}}$ indicates an instruction request from the Am29000 processor. $\overline{\text{IBREQ}}$ is active for establishing burst mode, while $\overline{\text{IBACK}}$ acknowledges to the Am29000 processor that the burst is supported. $\overline{\text{IRDY}}$ indicates a valid instruction is on the bus. $\overline{\text{BINV}}$ will invalidate the current access when a trap occurs, when there is a TLB miss, or for other reasons explained in the 29K Family literature.

The memory access state diagram is shown in Figure 4-1. Using only a single bit called $\overline{\text{ACC}}$ (access), the state machine output indicates either an idle condition or a pending instruction access. $\overline{\text{ACC}}$ is also used to drive the Chip Enable inputs of the EPROMs, as well as $\overline{\text{IRDY}}$ to the Am29000 processor. From the idle state, $\overline{\text{IREQ}}$ active with $\overline{\text{BINV}}$ inactive will move to the access pending state. While $\overline{\text{IBREQ}}$ is active (i.e., the burst mode is requested), the access pending state is continued. The access state can also be entered from idle with $\overline{\text{IBREQ}}$ active and $\overline{\text{IREQ}}$ inactive. This would be the case for resuming a previously suspended burst transfer for which a new address is not issued.

Revision D of the Am29000 processor does not allow $\overline{\text{IBACK}}$ to be active when $\overline{\text{IBREQ}}$ is inactive. For this reason, $\overline{\text{IBACK}}$ is a registered version of $\overline{\text{IBREQ}}$. A side effect is if the Am29000 processor suspends a burst, $\overline{\text{IBACK}}$ is de-asserted, which in turn terminates the burst. The next instruction access will then assert $\overline{\text{IREQ}}$ and place a new address on the bus, asserting $\overline{\text{IBREQ}}$ if a burst is needed.

Revision F of the Am29000 processor allows $\overline{\text{IBACK}}$ to be active when $\overline{\text{IBREQ}}$ is active; then $\overline{\text{IBACK}}$ can always be asserted. With $\overline{\text{IBACK}}$ active, a burst access can be resumed, which does not require a new address. The state machine already supports burst mode resumption. (Revision E is an intermediate revision, not released outside of AMD.)

Figure 4-1 Access State Diagram

 

Note:
 "/" indicates inactive state (not asserted)
 irrespective of signal polarity.

10623C-032



The address counter for the lower eight bits is loaded whenever a valid instruction address is issued by the Am29000 processor. Since single-cycle burst is supported, it is incremented on every clock while ACC is active.

The upper address bits are also latched when a new instruction is issued. The memory size determines the number of latched bits, and therefore the number of PAL devices used to implement the function.

DETAILED DESCRIPTION

The following paragraphs and figures describe the instruction memory design in detail. Complete PALASM® equations are included at the end of the chapter.

The state machine and lower five bits of the address counter are in a single 16V8 (see Figure 4-2, Block Diagram). A second PAL device contains the upper three counter bits and three latched address bits. If additional address lines are required, a third 16V8 houses them.

There are only a handful of timing parameters critical to the design (see Figure 4-3, 16-MHz Timing). Since \overline{IBREQ} and \overline{BINV} are asserted late in the bus cycle, the PAL device must have adequate setup time. For \overline{IBREQ} at 16 MHz, the value is 13 ns, and \overline{BINV} requires 20 ns. The 16V8H-10 with a 10-ns setup time fits the bill.

To determine the required PROM access time, both the setup time of 8 ns on the 29K data inputs, as well as the t_{CO} of 8 ns on the PAL device, are taken in account.

With a 16-MHz clock:

$$t_{acc} = 62.5 - 8 - 8 = 46.5 \text{ ns}$$

So a 45-ns PROM is required.

CONCLUSIONS

When combined with a two-cycle simple access data memory, this 16-MHz Am29000 processor implementation can yield 22,900 Dhrystones, providing a very cost-effective high-performance solution for embedded control applications.


For 20-MHz operation with this architecture, a t_{CO} of 7 ns is needed to allow use of 35-ns PROMS. To allow the use of slower memories, interleaving could be utilized, further lowering the memory cost.

REFERENCES

The following AMD documents are valuable references:


- Am29000 User's Manual (Order #10620)
- PAL Device Data Book (Order #10173)

Figure 4-2 EPROM System Block Diagram

 

Note:
In this diagram, the overbar indicates that a signal is active Low, not that it is inverted.

Figure 4-3 16-MHz Timing

 

10623C-034

PAL DEVICE EQUATIONS

Figure 4-4 Burst Address Counter Equations

CHIP IBUS_1 PAL 16V8 device

sysclock /ireq /ibreq /binv a2 a3 a4 a5 a6 gnd

/oe /iback /acc ra2 ra3 ra4 ra5 ra6 cout vcc

MINIMIZE_OFF

```
acc := /acc • ireq • /binv           ; idle state, begin access
      + /acc • ibreq • /binv        ; idle state, resume access
      + acc • ibreq                 ; access
                                      ; also drives IRDY, CE
```

```
iback := ibreq
```

```
ra2 := ireq • /binv • /acc • a2     ; load
      + /acc • /ireq • ra2          ; hold
      + acc • /ra2                  ; increment
```

Figure 4-4 Burst Address Counter Equations (continued)

```

ra3 := ireq • /binv • /acc • a3           ; load
      + /acc • /ireq • ra3                 ; hold
      + acc • (ra3 :+: ra2)                ; increment

ra4 := ireq • /binv • /acc • a4           ; load
      + /acc • /ireq • ra4                 ; hold
      + acc • (ra4 :+: (ra3 • ra2))        ; increment

ra5 := ireq • /binv • /acc • a5           ; load
      + /acc • /ireq • ra5                 ; hold
      + acc • (ra5 :+: (ra4 • ra3 • ra2)) ; increment

ra6 := ireq • /binv • /acc • a6           ; load
      + /acc • /ireq • ra6                 ; hold
      + acc • (ra6 :+: (ra5 • ra4 • ra3 • ra2)) ; increment

cout = ra6 • ra5 • ra4 • ra3 • ra2

```

Figure 4-5 Address Counter/Latch Equations

CHIP IBUS_2 PALCE16V8

sysclk /ireq /binv /acc a7 a8 a9 a10 a11 gnd

/oe a12 ra12 ra11 ra10 ra9 ra8 ra7 cout vcc

```

ra7 := ireq • /binv • /acc • a7           ; load
      + /acc • /ireq • ra7                 ; hold
      + acc • (ra7 :+: cout)              ; increment

ra8 := ireq • /binv • /acc • a8           ; load
      + /acc • /ireq • ra8                 ; hold
      + acc • (ra8 :+: (ra7 • cout))      ; increment

ra9 := ireq • /binv • /acc • a9           ; load
      + /acc • /ireq • ra9                 ; hold
      + acc • (ra9 :+: (ra8 • ra7 • cout)) ; increment

if (ireq • /binv • /acc) then             ; load upper address
  begin
    ra10 := a10
    ra11 := a11
    ra12 := a12
  end

else                                       ; hold upper address
  begin
    ra10 := ra10
    ra11 := ra11
    ra12 := ra12
  end
end

```

Figure 4-6 Address Latch Equations

CHIP IBUS_3 PALCE16V8

sysclk /ireq /binv /acc a13 a14 a15 a16 a17 gnd

/oe nc ra13 ra14 ra15 ra16 ra17 ra18 a18 vcc

```
if (ireq • /binv • /acc) then                                ; load upper address
begin
    ra13 := a13
    ra14 := a14
    ra15 := a15
    ra16 := a16
    ra17 := a17
    ra18 := a18
end

else                                                         ; hold upper address
begin
    ra13 := ra13
    ra14 := ra14
    ra15 := ra15
    ra16 := ra16
    ra17 := ra17
    ra18 := ra18
end
```




CONNECTING THE INSTRUCTION/DATA BUSES

The Am29000 processor bus architecture provides separate buses for instructions and data. This feature allows the high-performance system designer to separate the instruction and data fetches by providing a two-bank memory system.

For minimal-cost systems, however, using two banks of 32-bit wide memory (one each for data and instructions) may be too expensive. One solution to this problem is to connect the instruction and data buses together, via some suitable buffering, and to have a single bank of 32-bit wide memory.

The following design description is an example of how to build such a system, for both very low-cost systems and for higher performance systems at slightly higher cost.

INSTRUCTION RAM DESIGN

Initially, only instruction accesses will be described. Typically, because instruction fetches occur much more frequently than data accesses, this is the area where the maximum performance can be gained. Later, data accesses will be described.

Figure 5-1 shows the simplest memory system that can be connected to the Am29000 processor and corresponding timing. The memory system consists of an asynchronous decoder. PAL device generating the CE and OE strobes for the EPROM (or RAM), and also the $\overline{\text{IRDY}}$ signal back to the Am29000 processor. This system can support single-cycle accesses for all instruction accesses when used with fast enough memory devices.

The required memory access time in Figure 5-1 is calculated as follows:

$$t_{\text{acc}} = t_{\text{cyc}} - t_{\text{ad}} - t_{\text{pd}} - t_{\text{ds}}$$

where:

$$t_{\text{acc}} = \text{Memory access speed}$$

$$t_{\text{cyc}} = \text{Am29000 processor clock speed}$$

$$t_{\text{ad}} = \text{Address delay from Am29000 processor}$$


$$t_{\text{pd}} = \text{PAL device propagation delay}$$

$$t_{\text{ds}} = \text{Am29000 processor data setup}$$

$$t_{\text{acc}} = t_{\text{cyc}} - 16 - 7.5 - 6$$

$$t_{\text{acc}} = t_{\text{cyc}} - 29.5$$

Figure 5-1 Basic Memory System

 

10623C-035

Using memory devices with standard access times, the maximum frequency at which the Am29000 microprocessor can be clocked is:

Memory Access Time	Max Freq (MHz)
35 ns	15.5
55 ns	11.8
70 ns	10.0

Although this memory system can achieve the maximum possible bandwidth from the memory, the frequency at which the system can be clocked is somewhat low, thus reducing the overall performance.

Closer inspection of the memory access equation shows the only parameter that could possibly be reduced is the address propagation delay from the processor. If a fast external counter can generate the address then this value could be reduced from 16 ns to just the counter update time. This is a practical approach because most instructions are stored in consecutive memory locations.

One disadvantage with this method is that the first access in any instruction sequence would take two clock cycles, as the counter must be loaded. However, the overall performance is increased due to the higher clock frequency at which the processor can operate, as the majority of the instructions will still execute in a single clock cycle, but at a higher frequency.

Figure 5-2 shows this improved memory design and the corresponding timing.

The required memory access time in Figure 5-2 is calculated as follows:

$$t_{acc} = t_{cyc} - t_{iv} - t_{pd} - t_{ds}$$


where:

t_{iv} = clock inverter delay

$$t_{acc} = t_{cyc} - 5 - 7.5 - 6$$

$$t_{acc} = t_{cyc} - 18.5$$

Figure 5-2 Burst Mode Memory System

 

10623C-036

Using memory devices with standard access times, the maximum frequency at which the Am29000 processor can be clocked is:

Memory Speed	Max Freq (MHz)
35 ns	18.6
55 ns	13.6
70 ns	11.3

Extra performance has been gained with the addition of the extra hardware generating the address, with an added side effect that the processor address bus is now only used during the first instruction access and not during the subsequent or "burst" accesses.

This in itself does not gain much performance in data memory accesses in systems with a common instruction/data memory, as the memory devices that could be accessed with this bus are probably being accessed for instructions. However, it may significantly speed up I/O accesses that do not access the memory.

Having now generated a memory system performing two-cycle initial access and single-cycle burst access, it is also possible to build a similar system using lower-speed memories, but using two interleaved banks, as shown in Figure 5-3. This approach is probably more useful when larger code sizes are needed (more than four 8-bit wide memory devices are being used).

The required memory access time in Figure 5-3 is calculated as follows:

$$t_{acc} = 1.5 \cdot t_{cyc} - t_{pd} - t_{ds} - t_{dd}$$

where:


$$t_{dd} = \text{buffer propagation delay}$$

$$t_{acc} = 1.5 \cdot t_{cyc} - 30$$

Using memory devices with standard access times, the maximum frequency at which the Am29000 processor can be clocked is:

Memory Speed	Max Freq (MHz)
35 ns	23.0
55 ns	17.6
70 ns	16.0

Figure 5-3 Dual-Bank Interleaved Memory System

 

INSTRUCTION EPROM SUMMARY

Using 40-ns EPROMs on an Am29000 processor system employing the modified simple single-bank access design, 16-MHz operation is possible. The chip count of this system would consist of the following:

- 1 Am29000 processor
- 2 PAL devices for high-order addresses
- 2 PAL devices for low-order addresses
- 1 PAL device for decode, etc.
- 4 EPROMs

ADDITION OF READ/WRITE MEMORY


In a system with separate instruction and data memories, the data memory design can proceed relatively independent of the instruction memory design. In a combined system, certain considerations have to be made.

In order to connect the Am29000 processor instruction and data buses together, buffers have to be used to ensure both the processor and the memory subsystem do not attempt to drive the bus simultaneously. This could occur due to the fast switching of the Am29000 processor outputs, coupled with slow turn-off of the memory subsystem.

Because the buffers have to be used, the read access time of the data memory must be reduced by the propagation delay of the buffer. This implies that data memory access times must be approximately 10 ns faster than the equivalent instruction-only memory. The major drawback is that in minimal systems, the same physical memory is used for both instruction and data storage. The only practical solution for data accesses is to take two clock cycles, because implementing them as single-cycle accesses imposes a high memory cost. This solution would need to be implemented on all the previously discussed memory models. See Figure 5-4.

One potential drawback with this approach is the amount of time the address bus is utilized by the data memory. When performing multiple LOADs or STOREs, a minimum of one free clock cycle is required between the termination of one access and the

Figure 5-4 Read/Write Memory with Combined Instruction/Data Buses

 

10623C-038

commencement of the next. For example, to fill half the contents of the register file (i.e., perform 64 LOADs) 191 clocks would be required rather than 128 as first thought. This is a loss of 30% (worst case) of the available data bus bandwidth. This performance impact would only be seen on programs performing many multiple LOADs and STOREs.


To compensate for this, the data accesses can be accomplished in burst mode. In the examples shown in Figures 5-2 and 5-3, the address counting logic is already provided and thus a data memory system allowing three clocks for the first access and two-cycle burst can easily be built. See Figure 5-5.

This requirement is also necessary when looking at the data write timing, as the delay for the write data from the processor is 20 ns.

READ/WRITE MEMORY SUMMARY

Adding read/write capability to the Am29000 processor requires extra buffers be provided to ensure no data contention occurs between the processor and the memory. The minimum chip count capable of performing this task is two Am29C883A Multiple Bus Exchange devices. To maintain high performance, it is mandatory that the speed of

Figure 5-5 Addition of Burst Mode Data Access

 

10623C-039

instruction execution not be impaired by the buffer delay. Therefore, all data type memory accesses, whether they be reads or writes, will take longer than one clock cycle to execute.

DRAM SUPPORT

For systems requiring more than 256K words of memory, a DRAM solution can provide a cost-effective solution when using 1M x 1 static column DRAMs.

The advantage of static column DRAM over standard DRAMs is twofold. First, they can sustain high bandwidth, because only the column (not row) information needs to be updated on every cycle. Second, the CS strobe only has to be generated at the beginning of the cycle, as all subsequent accesses are fully combinatorial accesses from the column address. See Figure 5-6.

Refresh also must be provided for the DRAM. This is in the form of a simple 10-bit counter whose output drives refresh addresses onto the bus every 8 ms. During this time, the Am29000 processor must be suspended from making any accesses, and thus the refresh logic behaves like a bus master and takes control of the bus.

With simple timing, and using 100-ns DRAM devices, a system can offer three-cycle initial access, single-cycle burst access for instruction and data reads, and two-cycle burst access for data writes.

The required memory access time in Figure 5-6 for instructions is calculated as follows:

$$t_{acc} = t_{cyc} - t_{pd} - t_{su} - t_{iv}$$

$$t_{acc} = t_{cyc} - 7.5 - 6 - 5$$

$$t_{acc} = t_{cyc} - 18.5$$

The required memory access time in Figure 5-6 for data, assuming a buffer delay of 10 ns, is calculated as follows:


$$t_{acc} = t_{cyc} - 28.5$$

Therefore, standard 100 ns static column DRAMs, with a $t_{acc} = 40$ ns, can support a maximum clock frequency of 14.6 MHz.

The chip count of this system consists of the following:

- 1 Am29000 processor
- 2 29C983A MBE for data buffers
- 1 10-bit latch for high-order address
- 2 PAL devices for low-order address counter
- 3 PAL devices for control logic
- 1 10-bit counter for refresh address + refresh counter
- 32 DRAMs

Figure 5-6 Static Column DRAM Memory System

 

10623C-040

FURTHER INCREASES IN PERFORMANCE

To further increase the performance of our minimal system, there are several avenues which can be pursued.

First, the clock speed of the processor can be increased along with corresponding upgrades to the memory system. This provides a direct linear performance improvement over the slower system. The major disadvantage of this approach is the increase in cost and lack of availability of faster memory devices.

A second alternative is to increase the processor clock speed, combined with increasing the initial access time of the memory, while still maintaining fast burst capability. This provides a slightly lower performance upgrade, while maintaining the cost of the memory. The integral Branch Target Cache memory of the Am29000 processor helps to maintain high performance.

A third solution, as mentioned earlier, is to separate the instruction and data buses, thus simplifying the separate memory interfaces while potentially doubling the number of memories needed to build the system.

The final method is to use a dual-port memory array, providing separate instruction and data paths. This is easily achieved using Video DRAM devices, with the video shift port providing the instruction stream and the standard random access port providing the data memory. In this case it is not necessary to double the memory size.

To decide which approach is most appropriate for any particular application, various factors other than cost must be considered. Performance of the system is also key to any design. The use of AMD's simulation tools can be of help in determining which design provides the best combination of cost savings, performance, and ease of upgrade.



16-BIT MEMORY ARCHITECTURE

In order to meet the ever-increasing appetite for throughput by today's processors, there has been a natural migration from 8-, to 16-, and then to 32-bit buses. However, as the bus size increases, so does system cost, and with DRAM now at the 4 Megabit level, the amount of memory just 32 devices provide is far more than the requirements of many embedded processor systems.

The Am29000 processor has not only one, but two 32-bit buses, one for data and one for instructions. For applications where blazing speed is needed, this architecture is appropriate. However, the Am29000 processor is not limited to the highest-performance and highest-cost end of the embedded processor spectrum. The cost and performance of Am29000 processor-based systems can be varied across a wide range by changing the architecture of the memory system. This allows a single processor and software architecture to be applied to both high-performance and low-cost environments.

This chapter illustrates one solution to providing a low-cost DRAM-only system offering performance greater than many current CISC processor systems requiring expensive cache memory.

OVERVIEW OF THE 16-BIT DESIGN

As DRAM devices have grown in size, speed has increased as a byproduct. Today's 1 Megabit DRAMs achieve 60-ns RAS access time, while in the mid-1980s, 64K DRAM devices were only capable of 100 ns. The cost, on a per-bit basis, of DRAM memories of today is astoundingly low. Yet when 32 DRAM devices are placed on the board, their total cost can easily exceed that of the processor. The challenge is to make the design less expensive by reducing the number of memory components.

As noted earlier, increased memory bit density has allowed traditional 32-bit wide memory systems to far exceed the needs of many processor systems. One bank of 1-Megabit x 1 DRAM devices provides 4 Mb of memory. If separate instruction and data banks are used to increase performance, the memory system size would double to 8 Mb. Even if 256 Kbit x 4 DRAM devices were used, two banks of memory would total 2 Mb, far exceeding the needs for many lower-cost embedded processor systems.

The approach used in the memory design presented here is to cut the memory width in half to 16 bits and access two successive 16-bit words to build each 32-bit instruction or data value needed by the processor. The fast access speed of currently available memories allows a memory cycle rate of 16 MHz, which places the overall system speed at a still-respectable 8 MHz. The size of the memory system is further reduced by sharing the single bank of memory between the instruction and data buses of the processor.

The common instruction/data space eliminates the buffers and control logic usually needed to allow access to the instruction bus from the data bus (necessary for loading the instruction memory). This also simplifies some software issues related to the separation of instruction and data spaces.

The design presented in this chapter uses 256 Kbit x 1 DRAM devices, supplying 512 Kbytes of memory; 1 Mbit x 1 DRAM devices could be substituted to provide 2 Megabytes of memory; yet the design averages about 5 MIPS execution. This very respectable level of performance is maintained by the unique features of the Am29000 processor that help offset the effects of relatively slow DRAM memory. These features include the on-chip Instruction Branch Target Cache and the 192-location, three-port register file (used as a stack cache).


The system design in this chapter can be described as having an 8-MHz clock rate; two-clock first access DRAM with single-cycle burst access of both instructions and data. The ROM (for boot up) has a fixed two-cycle access time.

The design illustrates the use of both ROM and DRAM. I/O is not specifically addressed, although it is an easy extension to the design. This chapter is a general description; complete information on the design (schematics, equations, and timing diagrams) is available separately as an application note.

THEORY OF OPERATION

Figure 6-1 is a high-level block diagram of the 16-bit memory design. This chapter will examine the block diagram and outline the operation of the design.

Figure 6-1 System Block Diagram

 

Memory Addressing Scheme

The Am29000 processor provides three modes of addressing: simple, pipelined, and burst. In this design, only the simple mode of addressing is explicitly used, but the control signals associated with burst mode are monitored in order to allow information transfer at the burst mode rate.

In the simple bus access mode, the Am29000 processor presents the address for each word of memory accessed and holds the address valid until a Ready response is provided by the memory. In the burst access mode, the Am29000 processor provides the initial address of a sequence of words to be accessed and then removes the initial address when a memory responds with a Burst Acknowledge signal, which establishes a burst access. Then the initial address is removed and the remainder of the burst transfer is managed by a Burst Request signal from the Am29000 processor. The Burst Request signal controls the incrementing of an address counter in the memory interface.

In a standard Am29000 processor system, the burst access mode allows an instruction burst access to be initiated, followed by a release of the address bus for subsequent use in accessing data words concurrent with instruction word access.

Whenever there are sequential words to be accessed, the Am29000 processor will assert the Burst Request signals in an attempt to establish a burst access so the address bus can be released. However, if a Burst Acknowledge is not received from the memory, the Am29000 processor will continue the access in simple mode, providing an address for each word accessed. The Burst Request signals will also remain active throughout a sequential access stream.

In this system design, the instruction and data buses are tied together, thus preventing concurrent instruction and data access; there is no need to share the address bus between concurrent burst accesses. The memory interface will therefore never respond with a Burst Acknowledge, which forces the Am29000 processor to always provide addresses. This eliminates the need for address counters or latches in the memory interface. However, the Burst Request signals are still monitored to help manage page mode access of the DRAM so a single-cycle access rate can be supported for sequential streams of memory words. Therefore, the access speed advantages of burst mode are retained, while eliminating the need for address counters in the memory interface.

Clock Generator


Clock generation represents the heart of this design. The Am29000 processor runs at 8 MHz, yet the oscillator for this design runs at 32 MHz. The 32-MHz signal is divided down to produce an asymmetrical clock with a 25% duty cycle.

The reason for using an asymmetrical clock is related to the Bus Invalid ($\overline{\text{BINV}}$) signal. After the Am29000 processor starts an instruction or data access, late in the cycle it can assert $\overline{\text{BINV}}$ and cancel that access. For that reason it is difficult to start any access in the first clock cycle in a normal symmetrical clock design.

By using a 25% duty-cycle clock, $\overline{\text{BINV}}$ is made valid early in the system cycle so an access can start halfway through the first clock. This allows a two-clock-cycle first access. The clock generator also creates a symmetrical System Clock (SYSCLOCK) and a 2-Times System Clock (2XSYSCLOCK) for the control state machines. The cost for this is that all state machines will run at 32 MHz and use 2XSYSCLOCK and SYSCLOCK for decode, timing, and state hold purposes. The clocks are related as shown in Figure 6-2.

Since the clock input of the Am29000 processor requires CMOS levels, the PAL device clock outputs are buffered through a CMOS buffer device (74HCT04). Two outputs are tied together to drive the 90-pf load of the SYSCLOCK input of the Am29000 processor. The other clocks are also buffered through the CMOS buffer device in order to minimize skew between system clocks.

Figure 6-2 Clock Diagram

 

Bus Control PAL Device


A master state machine PAL device arbitrates between the Am29000 processor bus cycle request pins ($\overline{\text{IREQ}}$ and $\overline{\text{DREQ}}$) and the refresh request signal ($\overline{\text{REFREQ}}$). The requests have the following priority:

1. Refresh (highest priority)
2. Data
3. Instruction (lowest priority)

The state machine flow diagram is shown in Figure 6-3.

IACCESS, DACCESS and REFRESH represent the various paths of the state machine flow diagram. These control signals are used by the Decode PAL device to generate RAS and CAS for the DRAM and/or PROM control.

The $\overline{\text{IRDY}}$ and $\overline{\text{DRDY}}$ signals are asserted in the second cycle of an access when that access is to RAM. They remain asserted for each additional cycle of a burst transfer (single cycle burst). If the Access is to PROM ($\overline{\text{IREQT}} = 1$ or $\overline{\text{DREQT}} = 0$ with $\text{OPT2} = 1$),

 Figure 6-3 State Machine Flow Diagram

then it is a two-cycle access. $\overline{\text{DREQ}}$ with $\text{OPT2} = 1$ is for the ADAPT29K to access PROM as data. PIN169 will be High for this type of load, but for other ADAPT29K loads and stores, PIN169 will be Low. Pin 169 is then used by the state machine to hold in the IDLE state.

CLKEN is the controlling term for the registering of data in the first half of a bus cycle, and it is also used as address bit A1 for all memory accesses. CLKEN is normally Low and then brought High during the CLK 1 and CLK 0 time period.

Decode PAL Device

The Decode PAL device is only used to generate the RAS, MUX, and CAS control signals for the DRAM array. Because this PAL device cycles CAS for page mode accesses on either instruction burst or data burst, this PAL device is in the critical path and needs to be fast; 10-ns propagation delay or less. The delay line on pin 1 and pin 2 form a time delay for the high time of CAS during page mode accesses. This delay line is used to squeeze a burst access cycle time within a single cycle of SYSCLK. Therefore, the CAS high time (precharge) must be as short as the specification will allow (20 ns) in order to provide enough time to access both halves of each memory word and then meet the Am29000 processor data set up requirement.

Refresh PAL Device

The Refresh PAL device is simply a counter requesting a refresh cycle from the bus arbiter at 12- μ s intervals. The refresh request (REFREQ) is reset when the REFRESH signal becomes true. No attempt is made to see if refresh requests are skipped since the Am29000 processor will not issue an instruction stream for more than 256 instructions in a row, allowing a single refresh to be missed at most. Most programs will take a branch on the average of every eight instructions, so missing an occasional refresh should not be a problem. Just to be safe, this design over-refreshes memory at 12 μ s rather than the usual 15.5 μ s requirement. This over-refreshing makes up for any misses.

Address MUX

Three 74F157 devices serve as the address multiplexer in this design. They multiplex the lower 18 address lines of the processor into the DRAMs. The MUX control is simply RAS delayed by one 32-MHz clock cycle. The Clock Enable (CLKEN) signal serves as the half-word address (A1) bit. During burst accesses, the lower address bits of the Am29000 processor serve as the DRAM column.

Data/Instruction Bus Register

Since the 16-bit memory is being double-cycled to construct 32-bit words, the first half of the data must be remembered while the second half is being retrieved. This is done with a pair of 29C823A devices for the instruction bus and another pair for the data bus. The reason that the second pair of 29C823A devices is chosen is because the Am29000 processor can write data immediately after reading an instruction. This would violate the memory output hold time of the memory (instruction access) bus, so there must be a buffer between the Am29000 processor data bus and the instruction bus.

The separate Data In (DI) pins of the DRAM are driven by a separate set of 74LS244s attached to the data bus.

CRITICAL TIMING PATHS

This design has two areas critical for worst-case analysis:


1. $\overline{\text{BINV}}$ setup for the state machine
2. Second CAS on a Data Read operation

All other areas have good timing margins. The two critical areas are as follows.

$\overline{\text{BINV}}$

$\overline{\text{BINV}}$ comes out late in the second half of the Am29000 processor clock, however, it is needed to start up the state machine by mid-cycle. The clock for the AmPAL22V10-15 comes from the 32-MHz clock as shown in the path in Figure 6-4.

Figure 6-4 BINV Critical Path Timing

 

Assume the buffer will only have a 2-ns skew.

CLK-Q (7-ns PAL device)	6.5 ns
Buffer Skew	2 ns
CLK—BINV	9 ns
Setup AmpAL22V10-15	12 ns
	29.5 ns

This total must be less than 31.25 ns.


CAS

Here an early SYSCLOCK and a 2XSYSCLOCK are used to generate an early lead on CAS going false at the end of the first cycle. Also, a full clock is used to generate CAS; therefore, the CAS false time must be shortened by using a delay line function. CAS precharge time is 20 ns so a 20-ns delay line is chosen.

Worst CAS path is when the top path is slow and the bottom path is fast. The bottom path subtracts from the top path for a time balance.

The paths for operation are in Figure 6-5 below.

Figure 6-5 CAS Critical Path Timing

 

Delay Function (20 + 3)	23.0 ns
CAS (DECODE PAL)	7.5 ns
RC = 20 ohms x16 parts x6pf.	1.0 ns
CAS Access	25.0 ns
244 Buffer	4.5 ns
29K Data Setup	8.0 ns
	69.0 ns
<hr/>	
HCT04 Buffer	-3.0 ns
<hr/>	
	66.0 ns

This total must be less than **62.5 ns**.

Although this is out by 3.5 ns, it is unlikely all parts would be in the wrong direction simultaneously. However, simply slowing the clock down to 7.9 MHz would solve this worst case path without great impact on the MIP rate.

The data hold is guaranteed because all those signals are in a chain and hold time cannot go below the 4-ns minimum required on the data bus.

BENCHMARK FIGURES

This design was simulated using the Am29000 processor architectural simulator with two-clock-cycle first access with single-cycle burst on both data and instruction accesses. It was configured to simulate the sharing of address and data busses. The two programs run were Dhrystone 2.0 and Pi. (Pi is a very bus-access-intensive program that calculates the value of Pi to as many decimal places as desired.)

The results are as follows:

- Dhrystone 2.0 at 5.24 MIPS
- Pi at 6.30 MIPS

SUMMARY

This design demonstrates the versatility of the Am29000 processor. Even though the processor has a very high-performance bus architecture, the system implementation can be scaled down very economically while retaining good performance. A system using a single 16-bit bus, together with clock signals derived from a 32-MHz oscillator, can provide very respectable performance. This design approach may be suitable for embedded processor applications requiring a relatively small amount of memory.

Figure 6-6 Low-Cost Am29000 Processor Design (continued)

 


Figure 6-6 Low-Cost Am29000 Processor Design (continued)

 


Figure 6-6 Low-Cost Am29000 Processor Design (continued)

 


Figure 6-6 Low-Cost Am29000 Processor Design (continued)

 


Figure 6-6 Low-Cost Am29000 Processor Design (continued)

 


Figure 6-6 Low-Cost Am29000 Processor Design (continued)

 


Figure 6-6 Low-Cost Am29000 Processor Design (continued)

 


Figure 6-7 Clock Generator for Low-Cost Am29000 Processor Design Pattern

```

CHIP UXX PAL16R4
32CLK  $\overline{\text{RESETIN}}$  NC NC NC NC NC NC NC GND
OE NC NC NC 29KCLK SYSCLK 2XSYSCLK NRESET PRESET VCC

PRESET =  $\overline{\text{RESETIN}}$ 

NRESET.TRST = RESETIN

NRESET = VCC

2XSYSCLK :=  $\overline{2XSYSCLK}$ 

SYSCLK :=  $\overline{2XSYSCLK} \cdot \text{SYSCLK}$ 
          +  $\text{SYSCLK} \cdot 2XSYSCLK$ 

29KCLK :=  $\overline{2XSYSCLK} \cdot \text{SYSCLK}$ 

```

Figure 6-8 Bus Controller for Low-Cost Am29000 Processor Design

```

CHIP UXX AmPAL22V10
32CLK 2XSYSCLK SYSCLK  $\overline{\text{DREQ}}$  DREQT0  $\overline{\text{IREQ}}$  REQ  $\overline{\text{BINV}}$   $\overline{\text{DBREQ}}$   $\overline{\text{IBREQ}}$ 
PIN169 GND

 $\overline{\text{BGRT}}$   $\overline{\text{REFREQ}}$  OPT2 CLKEN  $\overline{\text{DRDY}}$   $\overline{\text{IRDY}}$  2NDCYCLE IDLE  $\overline{\text{REFRESH}}$   $\overline{\text{DACCESS}}$ 
 $\overline{\text{IACCESS}}$  VCC GLOBAL

STRING CLK3 '(SYSCLK • 2XSYSCLK)'
STRING CLK2 '(SYSCLK •  $\overline{2XSYSCLK}$ )'
STRING CLK1 '( $\overline{\text{SYSCLK}}$  • 2XSYSCLK)'
STRING CLK0 '( $\overline{\text{SYSCLK}}$  •  $\overline{2XSYSCLK}$ )'

IDLE := IDLE •  $\overline{\text{CLK2}}$  +  $\overline{\text{REFREQ}}$  •  $\overline{\text{DREQ}}$  •  $\overline{\text{IREQ}}$  •  $\overline{\text{BGRT}}$  •  $\overline{\text{PIN169}}$  • CLK2
      + PIN169 • IDLE + BINV • CLK2 • IDLE • DREQ + BINV • CLK2
      • IDLE • IREQ
      + BGRT •  $\overline{\text{IACCESS}}$  •  $\overline{\text{DACCESS}}$  • CLK0 • IDLE
      + IACCESS •  $\overline{\text{IBREQ}}$  • CLK1 • 2NDCYCLE • IDLE
      + DACCESS •  $\overline{\text{DBREQ}}$  • CLK1 • 2NDCYCLE • IDLE
      + REFRESH • 2NDCYCLE • CLK0 • IDLE

IACCESS := IDLE • IREQ •  $\overline{\text{DREQ}}$  •  $\overline{\text{REFREQ}}$  •  $\overline{\text{BINV}}$  • CLK2
          + IACCESS • 2NDCYCLE
          + IACCESS • 2NDCYCLE •  $\overline{\text{CLK1}}$ 
          + IACCESS • 2NDCYCLE • CLK1 • IBREQ

DACCESS := IDLE • DREQ •  $\overline{\text{DREQT0}}$  •  $\overline{\text{REFREQ}}$  •  $\overline{\text{PIN169}}$  •  $\overline{\text{BINV}}$  • CLK2
          + DACCESS • 2NDCYCLE
          + DACCESS • 2NDCYCLE •  $\overline{\text{CLK1}}$ 
          + DACCESS • 2NDCYCLE • CLK1 • DBREQ

```

Figure 6-8 Bus Controller for Low-Cost Am29000 Processor Design (continued)

$$\begin{aligned}
 \text{REFRESH} &: = \overline{\text{IDLE}} \cdot \overline{\text{REFREQ}} \cdot \overline{\text{PIN169}} \cdot \overline{\text{CLK2}} \cdot \overline{\text{BGRT}} \\
 &+ \overline{\text{REFRESH}} \cdot \overline{2\text{NDCYCLE}} \\
 &+ \overline{\text{REFRESH}} \cdot \overline{2\text{NDCYCLE}} \cdot \overline{\text{CLK0}} \\
 \\
 \text{IRDY} &: = \overline{\text{IRDY}} \cdot \overline{\text{IACCESS}} \cdot \overline{\text{IREQT}} \cdot \overline{2\text{NDCYCLE}} \cdot \overline{\text{CLK0}} \\
 &+ \overline{\text{IRDY}} \cdot \overline{\text{IACCESS}} \cdot \overline{\text{IREQT}} \\
 &+ \overline{\text{IRDY}} \cdot \overline{\text{IACCESS}} \cdot \overline{\text{IREQT}} \cdot \overline{\text{CLK0}} \\
 &+ \overline{\text{IRDY}} \cdot \overline{\text{CLK0}} \cdot \overline{\text{IREQT}} \\
 \\
 \text{DRDY} &: = \overline{\text{DRDY}} \cdot \overline{\text{DACCESS}} \cdot \overline{\text{OPT2}} \cdot \overline{2\text{NDCYCLE}} \cdot \overline{\text{CLK0}} \\
 &+ \overline{\text{DRDY}} \cdot \overline{\text{DACCESS}} \cdot \overline{\text{OPT2}} \\
 &+ \overline{\text{DRDY}} \cdot \overline{\text{DACCESS}} \cdot \overline{\text{OPT2}} \\
 &+ \overline{\text{DRDY}} \cdot \overline{\text{CLK0}} \cdot \overline{\text{DACCESS}} \cdot \overline{\text{OPT2}} \\
 \\
 2\text{NDCYCLE} &: = (\overline{\text{DACCESS}} + \overline{\text{IACCESS}} + \overline{\text{REFRESH}}) \cdot \overline{2\text{NDCYCLE}} \cdot \overline{\text{CLK0}} \\
 &+ \overline{2\text{NDCYCLE}} \cdot (\overline{\text{DACCESS}} + \overline{\text{IACCESS}} + \overline{\text{REFRESH}}) \cdot \overline{\text{CLK0}} \\
 \\
 \text{CLKEN} &: = (\overline{\text{DACCESS}} \cdot \overline{\text{OPT2}} + \overline{\text{IACCESS}} \cdot \overline{\text{IREQT}}) \cdot \overline{2\text{NDCYCLE}} \cdot \overline{\text{CLK2}} \\
 &+ (\overline{\text{DACCESS}} \cdot \overline{\text{OPT2}} + \overline{\text{IACCESS}} \cdot \overline{\text{IREQT}}) \cdot \overline{2\text{NDCYCLE}} \cdot \overline{\text{CLK1}} \cdot \overline{\text{CLKEN}} \\
 &+ \overline{\text{IACCESS}} \cdot \overline{\text{IREQT}} \cdot \overline{\text{CLKEN}} \cdot \overline{\text{CLK0}} \\
 &+ \overline{\text{IACCESS}} \cdot \overline{\text{IREQT}} \cdot \overline{\text{CLKEN}} \cdot \overline{\text{CLK0}} \\
 &+ \overline{\text{DACCESS}} \cdot \overline{\text{OPT2}} \cdot \overline{\text{CLKEN}} \cdot \overline{\text{CLK0}} \\
 &+ \overline{\text{DACCESS}} \cdot \overline{\text{OPT2}} \cdot \overline{\text{CLKEN}} \cdot \overline{\text{CLK0}}
 \end{aligned}$$

Figure 6-9 RAS and CAS Decoder for Low-Cost Am29000 Processor Design

CHIP UXX PAL16L8

$\overline{D2X}$ $\overline{2XSYSCLK}$ \overline{SYSCLK} $\overline{IACCESS}$ $\overline{DACCESS}$ $\overline{REFRESH}$ \overline{IREQT} \overline{SIPW} $\overline{2NDCYCLE}$
 GND OPT2 NC NC \overline{DATAE} \overline{PROME} \overline{WE} \overline{CAS} $\overline{DRAMACCESS}$ \overline{RAS} VCC

STRING CLK3 '($\overline{2XSYSCLK} \bullet \overline{SYSCLK}$)'

STRING CLK2 '($\overline{SYSCLK} \bullet \overline{2XSYSCLK}$)'

STRING CLK1 '($\overline{SYSCLK} \bullet \overline{2XSYSCLK}$)'

STRING CLK0 '($\overline{SYSCLK} \bullet \overline{2XSYSCLK}$)'

PROME = $\overline{IREQT} \bullet \overline{IACCESS} + \overline{DACCESS} \bullet \overline{OPT2} + \overline{PROME} \bullet \overline{CLK3}$

WE = $\overline{SIPW} \bullet \overline{DACCESS} + \overline{WE} \bullet \overline{CLK3}$

DATAE = $\overline{DACCESS} \bullet \overline{SIPW} \bullet \overline{OPT2} + \overline{DATAE} \bullet \overline{CLK3}$

RAS = $\overline{IACCESS} \bullet \overline{IREQT} + \overline{DACCESS}$
 + $\overline{REFRESH} \bullet (\overline{2NDCYCLE} \bullet \overline{CLK0} + \overline{2NDCYCLE} \bullet (\overline{CLK3} + \overline{CLK2}))$

CAS = $\overline{REFRESH} \bullet (\overline{2NDCYCLE} + \overline{2NDCYCLE} \bullet (\overline{CLK3} + \overline{CLK2}))$
 + $\overline{DRAMACCESS} \bullet \overline{2NDCYCLE} \bullet (\overline{2XSYSCLK} \bullet \overline{D2X} + \overline{D2X}$
 + $\overline{2XSYSCLK})$

DRAMACCESS = $\overline{DACCESS} + \overline{IACCESS} \bullet \overline{IREQT} + \overline{DRAMACCESS} \bullet \overline{CLK3}$

Figure 6-10 Refresh Controller Pattern

CHIP U23 PAL16U8

SYSCLK $\overline{\text{REFRESH}}$ NC NC NC NC NC NC NC NC GND
 NC Q6 Q5 Q4 Q3 Q2 Q1 Q0 $\overline{\text{REFREQ}}$ VCC

STRING TIME 'Q6 • Q5 • $\overline{\text{Q4}}$ • $\overline{\text{Q3}}$ • $\overline{\text{Q2}}$ • $\overline{\text{Q1}}$ • $\overline{\text{Q0}}$ '

Q0 := $\overline{\text{Q0}}$ + TIME

Q1 := Q0 :+: Q1 + TIME

Q2 := Q2 :+: (Q1 • Q0) + TIME

Q3 := Q3 :+: (Q2 • Q1 • Q0) + TIME

Q4 := Q4 :+: (Q3 • Q2 • Q1 • Q0) + TIME

Q5 := Q5 :+: (Q4 • Q3 • Q2 • Q1 • Q0) + TIME

Q6 := Q6 :+: (Q5 • Q4 • Q3 • Q2 • Q1 • Q0) + TIME

REFREQ := REFREQ • $\overline{\text{REFRESH}}$ + TIME • $\overline{\text{REFREQ}}$

TIMING DIAGRAMS

Figure 6-11 Instruction or Data Access


 


Figure 6-12 Refresh Cycle

 

PARTS LIST

Table 6-1 16-Bit Architecture Parts List

Item No.	Quantity	Device Description
OSC1	1	32 MHz
U1	1	74AC04
D1	1	1N4148
R1	1	100K
C1	1	4.7 μ F
R2, R4	2	1K
R3, R5, R6, R7	4	10K
U2	1	16R4-7
U3	1	Am29000
R8	1	33K
R9, R10	2	47
U4	1	16L8-7
U5	1	22V10-15
U6	1	18U8-35
U7	1	20 ns
U8, U9, U10	3	74F157
U11	1	74F74
R11–R19	9	20
U12, U13, U14, U15, U21, U22	6	74LS244
U16	1	74LS04
U17–U20	4	29C823A
U23, U24	2	27512
SW1	1	PROM CONFIG
U25–U40	16	21256

71 packages



INTERLEAVED SCDRAM

A Static Column DRAM (SCDRAM) memory design offers cache-like performance, but at a far lower cost and complexity than an SRAM memory. The static column capability means that once a row is addressed for the first time, all subsequent accesses within that row can be made by changing the column address without changing the row address, thereby avoiding the timing overhead of multiplexed row/column addressing. In effect, the SCDRAM memory has a built-in cache consisting of one row of words.

MEMORY STRUCTURE

The memory design described in this chapter has separate blocks of memory for instruction and data. Within each memory block, there are two banks of memory interleaved as odd and even words.

Each bank is 1M words deep with each word being 32-bits wide. The total for the instruction memory block is then 2M words (8M bytes). The same is true for the data memory.

SCDRAM memories with 85-ns access times are used for all memory banks. A non-sequential access requires one cycle for address decode and three cycles for the first word accessed. The low $\overline{\text{RAS}}$ access time allows a four-cycle initial access time for the memory system; 100-ns $\overline{\text{RAS}}$ access time memories may be used if the initial access time is extended to five cycles. Essentially the burst access timing is the same as for the medium-speed SRAM of Chapter 3; each burst access is two cycles long. Overlapping the memory bank access time allows this longer access time to be hidden from the system viewpoint, except on the first word of a non-sequential access. The result is a memory that provides four-cycle access time for the first word of a non-sequential access and single-cycle access for subsequent words in a burst transfer.

The instruction memory bank has a read-only port for sending instructions to the Am29000 processor and a read/write port tied to the Am29000 processor data bus. This port provides access via the data bus for instruction loading and memory diagnostics. The data memory has a single read/write port connection to the Am29000 processor data bus.

INSTRUCTION MEMORY

Refer to the block diagram in Figure 7-1.

The Memory

The memories are 1M x 1-bit SCDRAMs with separate data in and out lines. The access time is 85 ns. Thirty-two devices are required in each bank to form the 32-bit wide instruction word for the Am29000 processor. These are shown as devices U21 through U85. SCDRAMs are used to provide for access to sequential words within two clock cycles at 25 MHz and to simplify the required logic design. SCDRAMs have an advantage over standard DRAMs in that once a row is accessed, additional accesses within

the same row can be done simply by changing the column address and waiting the access time delay of 45 ns. Standard DRAMs with page mode access ability require that the Column Address Strobe ($\overline{\text{CAS}}$) be cycled for each new word accessed. Eliminating the need to cycle $\overline{\text{CAS}}$ simplifies the logic design and most SCDRAMs have faster access cycle times in static column mode than do equivalent DRAMs in page mode.

One additional "potential" advantage for either page mode or SCDRAMs is that the access time to words within an already selected row is much less than that required if the needed word lies in a different row. It is possible to reduce the initial access time of the memory whenever a non-sequential access begins in a row already being accessed. This is done by comparing all addresses from the processor with any currently active row address. If a match is identified, the memory control logic can simply access the needed word rather than precharging the memory and giving a new row address. This can reduce the initial access time from five to three cycles (precharge time between row addresses adds one clock cycle to the basic four-cycle initial access time).

This advantage is described above as "potential" because in the interest of keeping the design simple, this memory design does not implement the comparators or control logic needed to utilize the possible improvements from page or static column modes.

Data Bus Output Buffers

The memory data outputs are connected to the data bus lines via high-speed buffers. These buffers are required to isolate the memory outputs from the data bus whenever the memory is accessing instruction words. This isolation allows another data memory block to use the data lines at the same time instructions are being fetched from this memory block. These are shown as devices U95 through U102.

Data Bus Input Latches

The memory data inputs are connected to the data bus lines via Am29C843A latches. These are shown as devices U86 through U94.

Latches are used for the following reasons:

1. $\overline{\text{CAS}}$ (sometimes called Chip Select on SCDRAMs) is used as the write-enable qualifier.
2. The $\overline{\text{CAS}}$ signal is a registered output of the memory control logic and therefore its edge transitions occur one clock-to-output delay of a PAL device after the system clock time (3 to 8 ns plus memory loading delay).
3. Write data to the memories must be valid at or before the falling edge of the $\overline{\text{CAS}}$ signal.
4. Write data must be held valid for at least 20 ns after the falling edge of the $\overline{\text{CAS}}$ signal.
5. The $\overline{\text{CAS}}$ signal minimum pulse width is 25 ns.
6. The data output valid delay from the Am29000 processor is 18 ns.

Due to the reasons above, it is not possible to write data directly from the processor data bus since the data may not be valid until after the falling edge of the $\overline{\text{CAS}}$ signal during burst write cycles where new data is placed on the bus in each cycle (as a result of items 2, 3, and 6 above).

A register clocked by the rising edge of system clock would not have a clock-to-output delay fast enough to ensure meeting the data setup time to the $\overline{\text{CAS}}$ signal (Item 2).

A register clocked by the falling edge of system clock may not satisfy the required hold time relative to the $\overline{\text{CAS}}$ signal, assuming a single register set is used and is simply clocked on each falling edge of system clock (Items 2 and 4).

Dual register sets, one for each bank, clocked on every other falling edge of system clock could work. However, the worst-case timing margin for data setup time to the $\overline{\text{CAS}}$ signal is very small, due to clock-gating logic plus clock-to-output time of a register.

Dual latch sets, one for each bank, latch enabled every other cycle by the active bank indicator (Q02E) and a delayed system clock, will also work. Latches allow data to flow through to the memory inputs prior to the falling edge of the $\overline{\text{CAS}}$ signal. The latches also hold the data valid for the required time after the $\overline{\text{CAS}}$ signal. Both functions are accomplished with reasonable timing margins.

So with all the above in mind, data latches were chosen for use in the input data path to the memories. Using this data latching approach means data is removed from the bus one cycle earlier than would be the case if simple buffers could be used; this makes a write operation one cycle faster than an equivalent read operation.

Instruction Bus Buffers

The memory data outputs are also connected to the instruction bus lines via buffers. These buffers serve to isolate the data outputs of this memory block from those outputs of other memory blocks which may also drive the instruction bus. Also, the buffers serve to isolate the even and odd banks of this memory block from each other so simultaneous data access can occur in each bank independently. These buffers are shown as devices U103 through U110.

Address Registers and Counters

To support burst accesses, the lower seven address bits to each memory bank come from a loadable counter. An 8-bit counter is used to provide the address so the least significant bit of the counter can be used to track which memory bank is connected to the data or instruction bus on each cycle. The upper seven bits of the counter are used as the least significant address bits to each memory bank.

Each 8-bit counter is built from one PAL16R4 device and one PAL16R6 D-speed PAL device. The counters for both banks are shown as devices U6, U7, U9, and U10. The D-speed PAL devices are used because their clock-to-output delay is significantly faster than standard MSI 8-bit counters. Also, the use of PAL devices allow additional functions to be integrated into the same packages used for the counter function.

The upper 14 bits of memory address need not come from a counter since the Am29000 processor will always output a new address when a 256 word boundary is crossed. The upper 14 bits of address are simply latched. A latch is used so the address can flow through to the memories during the decode cycle and be setup before the falling edge of Row Address Strobe (RAS).

Address bits 10 through 12 are latched within the PAL devices which are used to implement the lower half of each bank address counter.

The upper 10 address bits (address bits 13 through 22) are latched in a pair of PAL16L8D PAL devices which also generate the needed latch-enable term. These are shown as devices U8 and U11.

A separate set of address counter logic is used to address each memory bank. This is done because when one bank is connected to the data or instruction bus, the other bank will be accessing the next word in sequence. This requires that the two banks have independently incremented addresses. The address for each bank will increment on different cycles.

Memory Address Multiplexers

The upper and lower ten bits of memory address must be multiplexed into the address inputs of the memories. Discrete multiplexers are used rather than simply controlling the output enables of the address counters and latches to form a three-state multiplexer. This was done to provide tighter control over the timing of the multiplexer switching between sources. The input switching delay of the multiplexer is no worse than what the three-state enable delays would be if the three-state multiplexer approach was used, although they do add undesired delay in the burst access address to data timing in read operations. Multiplexing is done via 74F158 multiplexers shown as devices U12–U14 and U114–U116.

Note: The outputs of the counter PAL devices are inverted as are the outputs of the 74F158; thus, the memory address lines are active High and the counters, in effect, count up.

Registered Control Signals

As noted earlier, the timing of the Instruction Burst REQuest ($\overline{\text{IBREQ}}$), Data Burst REQuest ($\overline{\text{DBREQ}}$), and Bus Invalid ($\overline{\text{BINV}}$) control signals require they be registered by a low setup time register. A 74F175 register, U3 shown in Figure 7-1, is used as a low setup time register.

Interface Control Logic

This logic must generate the memory response signals, manage the loading and counting of memory addresses, generate $\overline{\text{RAS}}$ and the $\overline{\text{CAS}}$ signals, control the data buffer output enables, and perform memory refresh. The logic functions needed for this require 11 PAL devices: two PAL20L8-B, two PAL16R4-D, four PAL16R6-D, one PAL16L8-B, one PAL16R8-D, and one AmPAL22V10-25.

In Figure 7-1, device U1, a PAL16L8-B produces the load and count enable signals for the address counters.


Device U2, an AmPAL22V10-25, provides a refresh interval counter and refresh request logic.

Devices U4 and U5, PAL20L8-B PAL devices perform address decode for instruction and data accesses. Their outputs indicate when this memory block has been addressed, when an access is to begin, and when an access is terminated.

Devices U15 through U20, four PAL16R6-D and two PAL16R4-D PAL devices, form a complex state machine controlling the $\overline{\text{RAS}}$, $\overline{\text{CAS}}$, output buffer enables, and memory response signals.

Device U112 generates byte-specific write enables.

Figure 7-1 Interface Logic Block Diagram

 


are not valid until the same cycle in which the outputs are required to effect control of the memory.

As shown in Figure 7-2, this state machine can be described as having 15 states. These states control the enabling of activity on the memory \overline{RAS} , \overline{CAS} , burst acknowledge, output buffer enable, and ready lines.

IDLE is the default state of the interface state machine. It is characterized by Instruction Burst ACKnowledge (\overline{IBACK}) and Data Burst ACKnowledge (\overline{DBACK}) both being inactive and no refresh activity in progress. This state serves as a way of identifying when the memory is not being accessed and could be placed into a low power mode. This state also serves as a precharge cycle for the memory when a transition is made between instruction, data, and refresh sequences. A transition to either the Instruction \overline{RAS} (IRAS) or Data \overline{RAS} (DRAS) states occurs when an address selecting this memory block is placed on the address bus. A transition to the Refresh Request 1 (RQ1) state occurs when a refresh request is active. Refresh will take priority over any pending instruction or data access request.

The IRAS state occurs during the first cycle of memory access following a new instruction address being presented on the address bus. During this state the instruction output buffer enables and Ready response lines are held inactive and the \overline{IBACK} and \overline{RAS} lines go active. The address latches are closed to hold the memory address. \overline{RAS} is

Figure 7-2 SCDRAM Memory State Diagram

 

10623C-044

used as the input to a delay line whose output will switch the address mux to the column address after the row address hold time is satisfied. The transition to the Instruction Column Address Strobe (ICAS) state is unconditional.

During the ICAS state the memory $\overline{\text{CAS}}$ signal goes active to start the first access cycle. Since the $\overline{\text{CAS}}$ access time for the memories used is 45 ns, it will take two cycles to access the memory, propagate data through the data buffers, and meet the setup time of the processor. Therefore, the transition to the Instruction ACCESS (IACCESS) state is unconditional.

The IACCESS state is used during the third cycle of a new address access and during all subsequent burst access cycles, whether active or suspended. In this state the instruction output buffer enable and ready lines are allowed to be active as required by the active or suspended status of an instruction burst request. When a new instruction address appears on the bus, a transition to the PreCharge (PC) state will occur. Also, if a data address selecting this memory block appears, there will be a transition to the PC state to force a preemption of the current instruction access. The same is true when a refresh request is pending. The state machine remains in the IACCESS state as the default if no other state transition condition appears.

During the PC state, both burst acknowledge signals will go inactive along with $\overline{\text{RAS}}$. The PC state will preempt any burst access and begin the $\overline{\text{RAS}}$ precharge required before any new row address is applied to the memory. The precharge period for the memory used is 80 ns so a second cycle of precharge will be done during the IDLE cycle which unconditionally follows the PC cycle. Another important use of the PC state is as a delay cycle in the transition between an active instruction burst access being preempted and the start of the preempting data access. The delay is needed to allow the completion of the final instruction access in the cycle that $\overline{\text{IBACK}}$ is deasserted and the instruction burst access is preempted.

There are two data access sequences, one for read, and another for write accesses.

During a read access the sequence is the same as for an instruction access except that during the Data ACCESS (DACCESS) cycles the $\overline{\text{DRDY}}$ and Data Output Enable ($\overline{\text{DOE}}$) signals are allowed to be active instead of the instruction related control signals. The read DACCESS state is exited when a refresh is pending, or when a data access is suspended. The exit transition is to the PC state.

A data write access is a little different in that during a write, the $\overline{\text{CAS}}$ signal is cycled to act as the write enable gate to the memories. This means that data to be written is latched from the bus in the cycle prior to $\overline{\text{CAS}}$ being made active. Therefore, the $\overline{\text{DRDY}}$ signal will go active one cycle before the $\overline{\text{CAS}}$ goes active. This creates a problem that is solved by the Write Burst Preempt (WBP1 and WBP2) states.

It is important to note that when the $\overline{\text{RRQ1}}$ signal is active, it will preempt a DACCESS and that a write operation is, in effect, pipelined. Data to be written is removed from the bus in the cycle before the write operation is enabled. So in the cycle that $\overline{\text{DBACK}}$ is made inactive to preempt the access, there may be one last data word being accepted from the bus. This word must be written in the following cycle. Also, at the point a refresh request goes active, $\overline{\text{DBACK}}$ will still be active and will not be made inactive until the beginning of the next cycle. So, from the time refresh request goes active until the last write cycle in memory is done, two cycles will occur. These cycles are labeled WBP1 and WBP2. During WBP1 the $\overline{\text{DBACK}}$ signal is made inactive to preempt the access, and data from the previous bus cycle is written. During WBP2 the last data word accepted from the bus is written, at which point the exit to the PC state is made.

Finally, there is the refresh sequence. Once the IDLE state is reached and a refresh is pending, the refresh sequence will start as the highest priority task of the memory. In fact, during the IDLE cycle, $\overline{\text{CAS}}$ will go active to setup for a $\overline{\text{CAS}}$ -before- $\overline{\text{RAS}}$ refresh cycle. This type of refresh cycle makes use of the SCDRAM internal refresh counters to supply the refresh address. During RQ1, $\overline{\text{RAS}}$ is made active as during IRAS and DRAS cycles. The RQ2 and RQ3 cycles are used to supply two additional wait states to make up the three cycles needed to satisfy the minimum $\overline{\text{RAS}}$ active time of 85 ns.

LOGIC DETAILS—SIGNAL BY SIGNAL

All signals are described in active High terms so the design is a little easier to follow. The signals, as implemented in the final Programmable Array Logic (PAL) outputs, will often be active Low as required by the actual circuit design. The actual PAL Definition files are included in Figures 7-3 through 7-19 at the end of this chapter.

NOTE: All PAL equations in this handbook use the following convention:

1. Where a PAL equation uses a colon followed by an equals sign ($:=$), the equation signals are registered PAL device outputs.
2. Where a PAL equation uses only an equals sign ($=$), the equation signals are combinatorial PAL device outputs

RFREQ (Refresh Request)

Dynamic memories are very forgetful and need to be completely refreshed every 4 ms, which translates into at least one row refreshed every 15.6 μs on average. A counter is used to keep track of this time. Once a refresh interval has passed, a latch is used to remember that a refresh is requested while the counter continues to count the next interval. Once the refresh has been performed, the latch is cleared.

The counter and refresh request latch is implemented in an AmPAL22V10-25. Nine of the outputs form the counter, which is incremented by the system clock at 25 MHz and which produces up to $512 \times 40 \text{ ns} = 20.48 \mu\text{s}$ refresh periods. The synchronous preset term for all the output registers is programmed to go active on a count value of 389, which sets all the outputs active on the 390th clock cycle. Afterwards, the counter will roll over to zero. This produces a refresh interval of 390 cycles \times 40 ns = 15.6 μs . The one remaining output is used to implement the refresh request function. That signal (the RFRQ1 registered output) is also set by the synchronous preset term. Thus, the refresh request is set on the last cycle of each refresh interval along with all the other outputs.

The equations for the counter are shown in Figure 7-3. Below are the preset and refresh request equations:

$$\text{SYNCHRONOUS PRESET} = \frac{\text{RFQ2} \cdot \overline{\text{RFQ3}} \cdot \text{RFQ4} \cdot \overline{\text{RFQ5}} \cdot \overline{\text{RFQ6}} \cdot \overline{\text{RFQ7}}}{\text{RFQ8} \cdot \text{RFQ9} \cdot \text{RFQ10}}$$

$$\text{RFRQ1} := \text{RFRQ1} \cdot \overline{(\text{RFACK} \cdot \text{RQ1})}$$

REFRESH SEQUENCE EQUATIONS

A refresh of the memory requires multiple clocks so the minimum $\overline{\text{RAS}}$ active time of 100 ns can be satisfied. To manage this the following equations are used.

RFACK

The Refresh Acknowledge (RFACK) is used to begin a refresh sequence and to clear the pending refresh request. A refresh may begin when the state machine has returned

to the IDLE state indicated by $\overline{\text{IBACK}}$ and DBACKI inactive. The DBACKI signal is an internal version of DBACK which is active until all data write cycles are completed. RFAACK is held active until the end of the sequence, indicated by $\text{RFRQ1} \bullet \text{RQ3}$.

$$\begin{aligned} \text{RFAACK} &:= \overline{\text{DBACKI}} \bullet \overline{\text{IBACK}} \bullet \text{RFRQ1} \\ &+ \text{RFAACK} \bullet (\overline{\text{RFRQ1}} \bullet \overline{\text{RQ3}}) \end{aligned}$$

RQ1, RQ2, RQ3

The three cycles needed for a refresh are tracked by RQ1, RQ2, and RQ3. RQ1 will not go active until the cycle following the IDLE state. This is controlled by $\text{RQ1} \bullet \text{PC1} \bullet \overline{\text{RFAACK}}$ which is only true during IDLE. The RQ1 signal is held active for all three refresh cycles to provide a single signal to identify when a refresh is in progress. the RQ2 and RQ3 signals simply follow RQ1 with RQ3 signaling the last cycle of the refresh sequence.

$$\begin{aligned} \text{RQ1} &:= \overline{\text{RQ1}} \bullet \overline{\text{PC1}} \bullet \text{RFAACK} \\ &+ \text{RQ1} \bullet \text{RQ3} \end{aligned}$$

$$\text{RQ2} := \text{RQ1} \bullet \overline{\text{RQ3}}$$

$$\text{RQ3} := \text{RQ2} \bullet \overline{\text{RQ3}}$$

REXIT

The Refresh EXIT (REXIT) signal is used to switch off the $\overline{\text{RAS}}$ signal at the end of a refresh sequence. RQ3 causes an exit and the $\overline{\text{RFAACK}}$ term causes REXIT to be active outside of a refresh sequence to disable other equation terms using REXIT as a holding input during a refresh sequence.

$$\begin{aligned} \text{REXIT} &= \overline{\text{RFAACK}} \\ &+ \text{RQ3} \end{aligned}$$

IME

The use of the Instruction for ME (IME) signal is based on the assumption that other blocks of instruction or data memory may be added later and that there may be valid addresses in address spaces other than instruction/data space.

This means this memory will only respond with $\overline{\text{IBACK}}$ or $\overline{\text{DBACK}}$ active when this block has been selected by valid addresses in the instruction/data space. This requires that at least some of the more significant address lines above the address range of this memory block be monitored to determine when this memory block is addressed. Also, it means the Instruction Request Type (IREQT) and Pin 169 lines must be monitored to determine that an address is valid and lies in the instruction/data space. Further, when a refresh request is pending, the memory will not recognize its address. This will ensure refresh has the highest priority during the IDLE state.

IME is the indication the address of this memory block is present on the upper address lines, an instruction request is active, Pin 169 is inactive (test hardware has not taken control), no refresh is pending, and instruction/data address space is indicated. In other words, this memory block is receiving a valid instruction access request. This example design will assume the address of this memory block is equal to $\text{A31} \bullet \text{A30} \bullet \text{A29} \bullet \text{A28} \bullet \text{A27}$. The equation for this signal is:

$$\text{IME} = \text{IREQ} \bullet \overline{\text{IREQT}} \bullet \overline{\text{A31}} \bullet \overline{\text{A30}} \bullet \overline{\text{A29}} \bullet \overline{\text{A28}} \bullet \overline{\text{A27}} \bullet \overline{\text{Pin169}} \bullet \overline{\text{RFRQ1}}$$

Note that IME is not directly implemented as a PAL device output in this design. The terms are used in the generation of the ISTART and IEXIT terms.

DME

The Data ME (DME) signal is the indication the address of this memory block is present on the upper address lines, a data request is active, Pin 169 is inactive, refresh is not active, and instruction/data address space is indicated. In other words, this memory block is receiving a valid data access request. This example design will assume the address of this memory block is equal to $A_{31} \cdot A_{30} \cdot A_{29} \cdot A_{28} \cdot A_{27}$. Note that for instruction accesses the memory address for this block had $A_{31} = \text{zero}$ where the data accesses to this block are valid for $A_{31} = \text{one}$. This allows instruction memory for instruction accesses to be located at address zero while having the window for data bus access to the instruction memory located at a different base address. This allows the separate data memory block used in this design to have its base address also at zero. Thus, both the instruction and data memories are located at address zero in their respective address spaces.

The equation for this signal is:

$$\text{DME} = \text{DREQ} \cdot \text{DREQT0} \cdot \text{DREQT1} \cdot A_{31} \cdot A_{30} \cdot A_{29} \cdot A_{28} \cdot A_{27} \cdot \text{Pin169} \cdot \text{REFRQ1}$$

As with IME, this term is not directly implemented.

ISTART

The Instruction START (ISTART) signal causes the transition from IDLE to IRAS states. It is valid only in the IDLE or IACCESS state with no refresh sequence starting, identified by not being in any other state via $\overline{\text{DBACKI}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}}$. So when in the IDLE or IACCESS state and IME is active, ISTART is active.

$$\text{ISTART} = \overline{\text{DBACKI}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}} \cdot \text{IME}$$

DSTART

The Data START (DSTART) signal is similar to ISTART except with DME as the qualifier.

$$\text{DSTART} = \overline{\text{IBACK}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}} \cdot \text{DME}$$

START

The START signal is used to restart $\overline{\text{RAS}}$ following precharge when there is still an active access in progress. This condition occurs when an instruction or data access is suspended and a new instruction or data access is started. In that situation the memory must be precharged before the new address is presented along with $\overline{\text{RAS}}$. During this PC time, the appropriate burst acknowledge signal is held active so as not to preempt the new access.

$$\begin{aligned} \text{START} &= \overline{\text{PC1}} \cdot \text{PC2} \cdot \overline{\text{IBACK}} \\ &+ \overline{\text{PC1}} \cdot \text{PC2} \cdot \overline{\text{DBACKI}} \\ &+ \overline{\text{PC1}} \cdot \overline{\text{RFACK}} \end{aligned}$$

IEXIT

The Instruction EXIT (IEXIT) equation identifies when it is time to leave the IACCESS state. IEXIT is true if no instruction access is in progress. The $\overline{\text{IBACK}}$ input causes this

so other equations using IEXIT to hold a term active will have that holding term made invalid when the IEXIT equation has no valid meaning, (i.e., when no instruction access is active).

IEXIT is also active when a data access, a refresh, or an instruction access not addressing this memory is pending. Any subsequent access is held off while $\overline{\text{IBACK}}$ remains active during the access of the first new instruction. As noted before, the DME term is a documentation convenience. In the IEXIT equation this term is directly expanded so all inputs of DME are inputs to IEXIT. This eliminates a level of logic delay that would be needed if DME were implemented as the output of another PAL device.

The IEXIT equation is:

$$\begin{aligned} \text{IEXIT} = & \overline{\text{DME}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \\ & + \overline{\text{IREQ}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \\ & + \overline{\text{RFRQ1}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \\ & + \overline{\text{IBACK}} \end{aligned}$$

A data request to this memory block for instruction data space takes priority over an instruction fetch in progress. Also, if a new instruction fetch stream is started, this memory interface can return to the idle state.

DEXIT

The description of IEXIT applies directly to the Data EXIT (DEXIT) signal; the logic is the same with data respective signals substituted for instruction terms. The only difference is the first exit term is a little different. A data access terminates when there is no further data burst requested. This approach is an optimization for use with the Am29000 processor. It makes use of the fact that the Am29000 processor will never suspend a data transfer and burst data transfers will always go to completion in a single contiguous burst access. When a burst, simple, or pipelined access ends, the memory immediately goes into precharge so the memory will be ready for subsequent accesses with a minimum initial access delay.

$$\begin{aligned} \text{DEXIT} = & \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{IME}} \\ & + \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{RFRQ1}} \\ & + \overline{\text{DBACKI}} \end{aligned}$$

IBACK

The instruction burst acknowledge ($\overline{\text{IBACK}}$) signal is applied to the Am29000 processor and is in effect the indication that the interface state machine is in an active or suspended instruction access. The equation is:

$$\begin{aligned} \overline{\text{IBACK}} := & \overline{\text{BINV}} \cdot \text{ISTART} \\ & + \overline{\text{IEXIT}} \end{aligned}$$

The $\overline{\text{IBACK}}$ active state is entered when ISTART is active and the bus state is valid on the same cycle. Note here that the $\overline{\text{BINV}}$ input is used directly rather than the registered form of $\overline{\text{BINV.D}}$. The timing of $\overline{\text{BINV}}$ is such that it will just meet the setup time of a PAL device input. The $\overline{\text{BINV}}$ signal is required as the qualifier since ISTART is a combinatorial signal. $\overline{\text{IBACK}}$ will remain active until one of the IEXIT conditions is active.

There is one special situation when $\overline{\text{IBACK}}$ remains active even after IEXIT goes active. When an instruction access is suspended and a new instruction access begins, $\overline{\text{IBACK}}$ is already active in the first cycle of the new instruction. The $\overline{\text{IBACK}}$ signal being active

tells the processor the address has been captured by the memory and a new address may be placed on the bus, perhaps one for a data access.

So, the memory is committed to accessing at least one instruction word for the new instruction access even though the address for the new access may change to begin yet another access.

Therefore, $\overline{\text{IBACK}}$ must remain active and any subsequent data access or refresh of this memory block must be held off until at least one word of the new instruction access can be read. Note that this can take several cycles since, when a new instruction access starts after a previously suspended one, the memory must be precharged followed by the normal sequence of $\overline{\text{RAS}}$ and $\overline{\text{CAS}}$ signals before the new instruction access is complete.

This is accomplished by holding $\overline{\text{IBACK}}$ active during the one cycle that $\overline{\text{IEXIT}}$ is active. The $\overline{\text{Istart}}$ input is active with $\overline{\text{IEXIT}}$ and is used to hold $\overline{\text{IBACK}}$ active.

$\overline{\text{IBACK.D}}$

The $\overline{\text{IBACK}}$ Delayed ($\overline{\text{IBACK.D}}$) signal is simply a one-cycle delayed version of $\overline{\text{IBACK}}$.

$$\overline{\text{IBACK.D}} := \overline{\text{IBACK}}$$

It is used in the generation of $\overline{\text{IRDY}}$, Instruction Output Enable (IOE)0, and IOE1.

$\overline{\text{DBACK}}$

The Data Burst Acknowledge ($\overline{\text{DBACK}}$) signal is applied to the Am29000 processor and is in effect the indication to the processor that a burst access is allowed. $\overline{\text{DBACK}}$ is essentially the same as $\overline{\text{IBACK}}$ but with data respective terms substituted.

$$\overline{\text{DBACK}} := \overline{\text{BINV}} \cdot \overline{\text{DSTART}} + \overline{\text{DEXIT}}$$

$\overline{\text{DBACK.D}}$

The $\overline{\text{DBACK}}$ Delayed ($\overline{\text{DBACK.D}}$) signal is simply a one-cycle delayed version of $\overline{\text{DBACK}}$.

$$\overline{\text{DBACK.D}} := \overline{\text{DBACK}}$$

It is used in the generation of $\overline{\text{DRDY}}$.

$\overline{\text{DBACKI}}$

The $\overline{\text{DBACK}}$ Internal ($\overline{\text{DBACKI}}$) signal is a memory interface internal version of $\overline{\text{DBACK}}$ to the Am29000 processor and is in effect the indication that the interface state machine is in an active or suspended data access. This signal will stay active during the DWBP states after $\overline{\text{DBACK}}$ has gone inactive to preempt a data burst write operation. The equation is:

$$\overline{\text{DBACKI}} := \overline{\text{BINV}} \cdot \overline{\text{DSTART}} + \overline{\text{DEXIT}} + \overline{\text{DWBP}}$$

Instruction Initial Access States

Signals IQ1, IQ2, and IQ3 are used to control the state transitions from IRAS to IACCESS during the first instruction access. IQ1 goes active during IRAS and remains active for two additional cycles. IQ1 will go active when there is a valid ISTART or when there was a previously suspended instruction access and a new instruction access was accepted; indicated by $\overline{PC1} \cdot PC2 \cdot IBACK$. IQ2 and IQ3 follow IQ1 with IQ3 indicating the last cycle of the initial access.

$$IQ1 := \overline{BINV} \cdot \overline{IQ1} \cdot ISTART \cdot \overline{IBACK} \\ + \overline{IQ1} \cdot \overline{PC1} \cdot PC2 \cdot IBACK \\ + IQ1 \cdot \overline{IQ3}$$

$$IQ2 := IQ1 \cdot \overline{IQ3}$$

$$IQ3 = IQ2 \cdot \overline{IQ3}$$

Data Initial Access States

These equations are the same as for IQ3–IQ1 with data respective inputs.

$$DQ1 := \overline{BINV} \cdot \overline{DQ1} \cdot DSTART \cdot \overline{DBACK} \\ + DQ1 \cdot \overline{PC1} \cdot PC2 \cdot DBACK \\ + DQ1 \cdot \overline{DQ3}$$

$$DQ2 := DQ1 \cdot \overline{DQ3}$$

$$DQ3 := DQ2 \cdot \overline{DQ3}$$

Data Write Burst Preempt States

When a data write operation is forced to preempt by a refresh request there are two additional write cycles that must be completed before PC is started. These states are tracked by the Data Write Burst Preempt (DWBP), DWBP1, and DWBP2 signals. DWBP starts the sequence when a data write is in progress, with burst request active, after the initial data write is completed, and a refresh is pending. DWBP1 and DWBP2 simply follow DWBP to indicate those states.

$$DWBP = DBACK1 \cdot \overline{RW} \cdot DBREQ.D \cdot RFRQ1 \cdot \overline{DQ1} \cdot \overline{DWBP2}$$

$$DWBP1 := DWBP1 \cdot DWBP$$

$$DWBP2 := \overline{DWBP2} \cdot DWBP1$$

Precharge States

At the end of any access, the \overline{RAS} lines must be made inactive to precharge internal memory buses before another access with a different row address may begin. Two cycles are needed and are indicated by the signals PC1 and PC2. PC1 is active during the PC state and PC2 is active during the first cycle of the IDLE state. PC1 goes active as the result of an IEXIT condition during instruction access, a DEXIT condition during data access following any Data Write Burst Preempt (DWBP) cycles, and at the end of a refresh sequence. PC2 simply follows PC1.

$$PC1 := \overline{PC1} \cdot IBACK \cdot IEXIT \\ + \overline{PC1} \cdot DBACK1 \cdot \overline{DWBP} \cdot DEXIT \\ + \overline{PC1} \cdot RQ3 \\ + DWBP2$$

$$PC2 := PC1 \cdot \overline{PC2}$$

LD

The Load (LD) signal enables the lower address bit counters and the upper address bit latches to load a new address on the next rising edge of System Clock (SYSCLK). The equation is:

$$LD = \overline{IQ1} \cdot PC1 \cdot \overline{DBACKI} \cdot IREQ \\ + \overline{DQ1} \cdot PC1 \cdot \overline{IBACK} \cdot DREQ$$

When an Instruction request (\overline{IREQ}) signal is active, load is prevented from being active while a data access is active or suspended. In other words, when the state machine is in a data access state a load that would result from an instruction request is suppressed. This prevents the changing of the address counter values until the data access ends. Similarly, for the case that Data Request (\overline{DREQ}) signal is active, load is prevented when \overline{IBACK} is active.

The LD signal is limited in length to one cycle by IQ1 or DQ1 during an initial access. It is limited to one cycle by PC1 when a new access begins during a previously suspended access. Limiting the LD signal to one cycle ensures the correct address is captured and that LD does not interfere with the incrementing of the counters. The LD signal is combinatorial so that it can be active during the first cycle of a new instruction or data request.

Address Counters

There is one address counter for each bank of memory. Each is implemented with one PAL16R4-D and one PAL16R6-D device. The counter function is split across two PAL devices due to the number of product terms required to implement the upper bits of the counter. The lower half of the counter produces a carry out to the upper counter half. The equations for both bank counters are the same. These equations are shown in Figures 7-13 through 7-16.

The LSB bit of each counter is used as the means to control the timing of when the upper seven bits of each counter will increment. Note that only the upper seven bits of the counter are used as the low seven bits of address to the memory in a bank. This is because, with two interleaved banks, the maximum length burst access is split between the banks so each bank counter will never increment more than 128 times.

The upper bits of each counter increment on every cycle that the count signal is active and the LSB is also active. The only exception to the latter condition is during a bus invalid cycle where \overline{BINV} signal is used to prevent counting when burst request may be invalid.

The value of the LSB bit in each counter is different in any given cycle, which causes the upper bits of the counters to increment on different cycles with regard to each other. In other words, the upper seven bits of the counters will be out of phase in terms of when they increment. This allows one bank of memory to start the access of the next word in sequence while the other bank completes the access of the current word.

Count Signals

There are two Count (CNT) signals defined in this design, CNT0 and CNT1, one for the even bank and one for the odd bank. This is because the even bank always increments one cycle earlier than the odd bank during the initial access of memory. Once the counting is started out of phase between banks, the bank counters are always incremented together to maintain the phase relationship. The CNT signals cause the address counters to increment on the next rising edge of SYSCLK.

The CNT0 controls the even bank counter. During either a data or instruction read operation, the first active cycle of CNT0 is during the DCAS or ICAS states indicated by the first cycle in which DQ2 or IQ2 is active. When the initial address selects an even word of memory, this first count cycle increments only the LSB of the even bank counter. This does not affect the memory address, but it makes the LSB high; this is used as an indication in other equations that data from the even bank is to be placed on the system bus. If the initial address selects an odd word, this first count cycle increments the whole even bank counter to point to the next even word in sequence after the initial odd word that will come from the odd memory bank. In this case, the LSB bit is Low and indicates that the word, ready to be placed on the system bus, comes from the odd bank.

In the following cycle, IQ2 or DQ2 is still active, which ensures one more cycle of count. Any further count cycles come from burst-request signals being active during IACCESS or DACCESS states.

Note that in case a burst access is suspended and a new access of the same type begins, the address of the new access is loaded into the counter and the memory precharges in preparation for a new $\overline{\text{RAS}}$ cycle. During the precharge cycles, the incrementing of the counter must be inhibited by PC1 and PC2 so as not to change the address stored in the counter before the RAS and the CAS signal cycles for the new access.

The CNT0 signal is handled differently during a data write in that any increment during IQ3 or DQ3 must be qualified by a burst request in the previous cycle. This is needed because in a write operation, the first Data Ready (DRDY) signal active cycle comes one cycle earlier than in a read operation.

$$\begin{aligned} \text{CNT0} = & \text{IBACK} \cdot \text{IQ2} \\ & + \text{IBACK} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IBREQ.D} \\ & + \text{DBACK1} \cdot \text{RW} \cdot \text{DQ2} \\ & + \text{DBACK1} \cdot \text{RW} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D} \\ & + \text{DBACK1} \cdot \overline{\text{RW}} \cdot \text{DQ2} \cdot \text{DQ3} \\ & + \text{DBACK1} \cdot \overline{\text{RW}} \cdot \text{DQ3} \cdot \text{DBREQ.D} \\ & + \text{DBACK1} \cdot \overline{\text{RW}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D} \end{aligned}$$

The CNT1 signal controls the odd bank counter. This equation is essentially the same as CNT0 except the first cycle in which CNT1 is active is always one later than it would have been in CNT0.

$$\begin{aligned} \text{CNT1} = & \text{IBACK} \cdot \text{IQ3} \\ & + \text{IBACK} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IBREQ.D} \\ & + \text{DBACK1} \cdot \text{RW} \cdot \text{DQ3} \\ & + \text{DBACK1} \cdot \text{RW} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D} \\ & + \text{DBACK1} \cdot \overline{\text{RW}} \cdot \text{DQ3} \cdot \text{DBREQ.D} \\ & + \text{DBACK1} \cdot \overline{\text{RW}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D} \end{aligned}$$

$\overline{\text{IRDY}}$

The Instruction Ready ($\overline{\text{IRDY}}$) signal indicates there is valid read data on the instruction bus.

$$\begin{aligned} \overline{\text{IRDY}} = & \text{IQ3} \\ & + \overline{\text{BINV.D}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IBREQ.D} \cdot \text{IBACK.D} \end{aligned}$$

This memory design is always ready with data in the IQ3 cycle.

The memory is also ready when $\overline{\text{IBREQ}}$ is active with $\overline{\text{IBACK}}$ in the previous cycle. But again, the special situation of a suspended burst operation followed by a new access of the same type is handled by adding $\text{IQ1} \cdot \text{PC1} \cdot \text{PC2}$ to the equation. This prevents $\overline{\text{IRDY}}$ from going active until the new access has had time to precharge and readdress the memory. The $\overline{\text{BINV.D}}$ input is used to prevent false ready indications due to signals on the bus being invalid.

$\overline{\text{IBACK.D}}$ is required as a qualifier so when an access is preempted, the continued presence of $\overline{\text{IBREQ}}$ will not cause a false ready indication. The $\overline{\text{BINV.D}}$ signal is used to prevent false ready indications if the bus was invalid in the previous cycle. Note that situations can occur during a suspended access when the processor grants the bus to another bus master.

The reason $\overline{\text{IRDY}}$ must be a combinatorial signal is that $\overline{\text{IBREQ}}$ comes very late in the previous cycle and must be registered. There is no time to perform logic on $\overline{\text{IBREQ}}$ in the previous cycle before SYSCLK rises. This means the information that $\overline{\text{IBREQ}}$ was active in the last cycle is not available until the cycle in which $\overline{\text{IRDY}}$ should go active for a resumption of a suspended burst access.

IOE0 and IOE1

The instruction output enable (IOE) signals are used to control which bank is allowed to drive the instruction bus during each cycle. The signals use essentially the same logic as $\overline{\text{IRDY}}$ except each signal is further qualified by the output of the LSB bit of the even bank counter (Q02E). This bit keeps track of which memory bank is ready to provide data to the instruction bus. The even bank is enabled when $\overline{\text{IRDY}}$ is active and the Q02E bit is active. The odd bank is enabled when $\overline{\text{IRDY}}$ is active and Q02E is inactive.

$$\begin{aligned} \text{IOE0} &= \text{Q02E} \cdot \text{IQ3} \\ &+ \overline{\text{BINV.D}} \cdot \text{Q02E} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IBREQ.D} \cdot \text{IBACK.D} \\ \text{IOE1} &= \overline{\text{Q02E}} \cdot \text{IQ3} \\ &+ \overline{\text{BINV.D}} \cdot \overline{\text{Q02E}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IBREQ.D} \cdot \text{IBACK.D} \end{aligned}$$

DRDY

The Data Ready ($\overline{\text{DRDY}}$) is the equivalent of $\overline{\text{IRDY}}$ for data accesses and therefore uses the same equation with data respective terms substituted for instruction terms. The one additional change is that a term is added to cause $\overline{\text{DRDY}}$ to occur one cycle early during write operations. This is done because the data to be written is taken from the data bus into a latch before actually being stored in the memory. This maintains the same memory timing used during read operations but write data is removed from the bus one cycle earlier than when $\overline{\text{DRDY}}$ would normally go active during a data read operation.

$$\begin{aligned} \overline{\text{DRDY}} &= \text{RW} \cdot \text{DQ3} \\ &+ \overline{\text{BINV.D}} \cdot \text{RW} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D} \cdot \text{DBACK.D} \\ &+ \text{RW} \cdot \text{DQ2} \cdot \text{DQ3} \\ &+ \overline{\text{BINV.D}} \cdot \text{RW} \cdot \text{DQ3} \cdot \text{DBREQ.D} \cdot \text{DBACK.D} \\ &+ \overline{\text{BINV.D}} \cdot \overline{\text{RW}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D} \cdot \text{DBACK.D} \end{aligned}$$

DOE0 and DOE1

The data output enable (DOE) signals serve the same function for $\overline{\text{DRDY}}$ as the IOE0 and IOE1 signals serve for $\overline{\text{IRDY}}$. Their signal descriptions are the same as for the IOE signals. The only difference is the DOE signals are active only during read operations.

$$\begin{aligned} \text{DOE0} &= \text{RW} \cdot \text{Q02E} \cdot \text{DQ3} \\ &+ \overline{\text{BINV.D}} \cdot \text{RW} \cdot \text{Q02E} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D} \cdot \text{DBACK.D} \\ \text{DOE1} &= \text{RW} \cdot \overline{\text{Q02E}} \cdot \text{DQ3} \\ &+ \text{BINV.D} \cdot \text{RW} \cdot \overline{\text{Q02E}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D} \cdot \text{DBACK.D} \end{aligned}$$

WE

The Write enables (WE) are registered signals that go active during the first DQ2 active cycle. They stay active throughout the data-write operation. The $\overline{\text{CAS}}$ signal is used in this design as the actual write-gating signal. This was done to reduce the number of write signal outputs. Address, $\overline{\text{RAS}}$, and the $\overline{\text{CAS}}$ lines have been duplicated in this design so only half of each memory bank is driven by a given output. This reduces the capacitive and inductive loading on each output so as to improve signal speed. Since the $\overline{\text{CAS}}$ signal lines have already been doubled they are used as the write gate. The write enable line can thus be made active early in the cycle to have additional time to drive a heavier load.

$$\text{WE0} := \text{DBACKI} \cdot \overline{\text{RW}}$$

$$\text{WE1} := \text{DBACKI} \cdot \overline{\text{RW}}$$

Separate WE lines are provided for each byte position in the memory. These are controlled by the two least significant address lines (A1, A0), the Option bits 0–2, and a Byte Order (BO) input. The BO input determines the byte order assumed by the memory and should be tied High or Low, or driven from a loadable register, to match the value of the byte order maintained in the Am29000 processor internal configuration register. The Option bits express codes are defined to select full-word, half-word, and byte-wide memory accesses. Used in combination with the least significant address bits, the Option bits give the processor the ability to specify partial-word Write operations.

When a full-word Write operation is specified, all WE lines go active. A half-word Write only selects either the upper or lower two WE lines to go active, thus preventing a Write operation in the two byte positions not selected. The two unselected byte positions perform a Read operation instead. The resulting Read Access of data is prevented from reaching the data bus by the data read buffers U95–102 since these buffers are not enabled during a Write operation. This prevents contention on the data bus with the processor since the processor actively drives all 32 data lines. There is also no contention at the SCDRAM outputs since the data inputs and outputs are separate. Byte-Write operations operate in a fashion similar to half-word Writes. A duplicate set of WE signals is provided for each bank of memory to help limit the loading on these lines.

A sample of the WE equations is shown below; the full set of equations are shown in Figure 7-19. The DSTART input is used to indicate when the Address, R/W, and Option signals are valid. The DBACKI input is used to hold the appropriate state of the WE lines after the Address, R/W, and Option lines go invalid.

$$\begin{aligned} \text{WE031} &= \overline{\text{OPT2}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{RW}} \cdot \text{DSTART} && ;\text{Word} \\ &+ \overline{\text{OPT2}} \cdot \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \overline{\text{BO}} \cdot \overline{\text{A1}} \cdot \overline{\text{A0}} \cdot \overline{\text{RW}} \cdot \text{DSTART} && ;\text{Byte, Big} \\ &+ \overline{\text{OPT2}} \cdot \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \text{BO} \cdot \overline{\text{A1}} \cdot \overline{\text{A0}} \cdot \overline{\text{RW}} \cdot \text{DSTART} && ;\text{Byte, Little} \\ &+ \overline{\text{OPT2}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{BO}} \cdot \overline{\text{A1}} \cdot \overline{\text{RW}} \cdot \text{DSTART} && ;\text{HW, Big} \\ &+ \overline{\text{OPT2}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \text{BO} \cdot \overline{\text{A1}} \cdot \overline{\text{RW}} \cdot \text{DSTART} && ;\text{HW, Little} \\ &+ \text{WE031} \cdot \text{DBACKI} \end{aligned}$$

Data Latch Enables

Data Latch Enable 0 and 1 (DLE0 and DLE1) are the signals enabling the write data latches on the D input of each memory bank to load new data.

The latches are enabled on every other cycle so data is held valid long enough to satisfy the hold time after the $\overline{\text{CAS}}$ signal goes active. The Q02E counter output is used to control which latch is enabled on a given cycle. A delayed version of the system clock is used to further place a window on the latch enable. This is an 8-ns delay generated in U111. Only during the high time of the delayed clock signal will the data be allowed through the latch. This is done to ensure that data is latched before the end of the system clock cycle when the processor begins changing the data value for the next write cycle. That could not be guaranteed by Q02E alone since it is a registered output with a clock-to-output delay. This is also the reason the clock used is a delayed version of the system clock. This clock is delayed long enough to ensure the worst-case clock-to-output time on Q02E has passed before enabling the latch. This ensures that no data is lost by having the latch enabled during the switching transition of Q02E as might happen if simply the system clock were used instead of the delayed clock.

$$\overline{\text{DLE0}} = \text{Q02E} \cdot \text{CLKD}$$

$$\overline{\text{DLE1}} = \overline{\text{Q02E}} \cdot \text{CLKD}$$

Row Address Strobes

There are five duplicated Row Address Strobe ($\overline{\text{RAS}}$) lines. Four are used to drive the memories and one drives the delay line used to switch the address mux at the appropriate time. Multiple lines are used to split the capacitive and inductive load of the memory array to improve signal speed.

$\overline{\text{RAS}}$ is made active by a valid ISTART, DSTART, or START condition. $\overline{\text{RAS}}$ is held active until an exit condition exists for the type of access in progress.

$$\begin{aligned} \text{RAS0H} := & \overline{\text{BINV}} \cdot \overline{\text{RAS0H}} \cdot \text{ISTART} \\ & + \overline{\text{BINV}} \cdot \overline{\text{RAS0H}} \cdot \text{DSTART} \\ & + \overline{\text{BINV}} \cdot \overline{\text{RAS0H}} \cdot \text{START} \\ & + \text{RAS0H} \cdot \overline{\text{EXIT}} \\ & + \text{RAS0H} \cdot \overline{\text{DEXIT}} \\ & + \text{RAS0H} \cdot \overline{\text{REXIT}} \\ & + \text{RAS0H} \cdot \text{DWBP} \end{aligned}$$

$\overline{\text{CAS}}$

As with the $\overline{\text{RAS}}$ lines, the $\overline{\text{CAS}}$ lines are duplicated to split the memory load.

The $\overline{\text{CAS}}$ signal goes active in the cycle after $\overline{\text{RAS}}$ during instruction or data accesses. During a data write access the $\overline{\text{CAS}}$ signal is enabled only when the appropriate bank is written with data. This is controlled with the Q02E line from the even bank address counter. $\overline{\text{CAS}}$ signal during write is further gated by $\overline{\text{DRDY}}$ being active on the previous cycle which ensures that a write only occurs when valid data was taken from the bus. Only in the case of a refresh sequence will $\overline{\text{CAS}}$ signal be made active prior to $\overline{\text{RAS}}$. This will initiate a $\overline{\text{CAS}}$ before $\overline{\text{RAS}}$ refresh cycle in the memories. In this case the $\overline{\text{CAS}}$ signal is made active during the IDLE state.

$$\begin{aligned} \text{CAS0H} := & \text{RAS} \cdot \text{IBACK} \\ & + \text{RAS} \cdot \text{DBACKI} \cdot \text{RW} \\ & + \text{RAS} \cdot \text{DBACKI} \cdot \overline{\text{RW}} \cdot \overline{\text{Q02E}} \cdot \text{DRDY} \\ & + \overline{\text{RAS}} \cdot \overline{\text{IBACK}} \cdot \overline{\text{DBACKI}} \cdot \text{RFRQ1} \end{aligned}$$

$$\begin{aligned}
 \text{CAS1H} &:= \text{RAS} \cdot \text{IBACK} \\
 &+ \text{RAS} \cdot \text{DBACKI} \cdot \text{RW} \\
 &+ \text{RAS} \cdot \text{DBACKI} \cdot \overline{\text{RW}} \cdot \text{Q02E} \cdot \text{DRDY} \\
 &+ \overline{\text{RAS}} \cdot \overline{\text{IBACK}} \cdot \overline{\text{DBACKI}} \cdot \text{RFRQ1}
 \end{aligned}$$

Upper Address Bits Latch

The address bits 13 through 22 are latched by two D-speed PAL devices. All the bit equations are the same. Data flows through when the Address Latch Enable (ALE) term is active, and latched when ALE is inactive. An additional product term combines the data input and output to prevent any possible loss of data during the ALE transition that might be caused by timing skew on ALE within the PAL device (note the ALE term is a documentation convenience only; where ALE is shown, the actual logic definition of ALE is substituted). The ALE term is made active each cycle by a delayed version of the system clock. The delayed clock is used for the same reasons described for the DLE signals. During the initial access of an instruction or data word, ALE is prevented from going active by the IQ1 and DQ1 terms. ALE is also held inactive during PC1 and PC2. This is done to preserve the address when a suspended access is followed by another access of the same type. In this case, the address must be held while the memory is precharged and during the $\overline{\text{RAS}}$ cycle of the new access.

$$\begin{aligned}
 \text{LA22} &= \text{ALE} \cdot \text{A22} \\
 &+ \overline{\text{ALE}} \cdot \text{LA22} \\
 &+ \text{A22} \cdot \text{LA22}
 \end{aligned}$$

$$\text{ALE} = \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{CLKD}$$

PAL Definition Files

The PAL definition files are provided in Figures 7-3 through 7-19.

NOTE: All PAL equations in this Application Note use the following convention:

1. Where a PAL equation uses a colon followed by an equals sign (:=), the equation signals are registered PAL outputs.
2. Where a PAL equation uses only an equals sign (=), the equation signals are combinatorial PAL outputs.
3. The device pin list is shown near the top of each figure as two lines of signal names. The names occur in pin order, numbered from left to right, 1 through 20. The polarity of each name indicates the actual input or output signal polarity. Signals within the equations are shown as active High (e.g., where signal names in the pin list are A B C, the equation is $C = A \cdot B$; when the inputs are A = Low, B = Low, then the C output will be Low).

Figure 7-3 AmPAL22V10-25 SCDRAM Refresh Counter/Request Generator Device U2

CLK $\overline{\text{RFACK}}$ $\overline{\text{RQ1}}$ $\overline{\text{RQ2}}$ $\overline{\text{RQ3}}$ NC6 NC7 NC8 NC9 NC10 NC11 GND
 NC13 $\overline{\text{RFRQ1}}$ $\overline{\text{RFQ2}}$ $\overline{\text{RFQ3}}$ $\overline{\text{RFQ4}}$ $\overline{\text{RFQ5}}$ $\overline{\text{RFQ6}}$ $\overline{\text{RFQ7}}$ $\overline{\text{RFQ8}}$ $\overline{\text{RFQ10}}$ $\overline{\text{RFQ9}}$ VCC

$$\text{RFQ2} := \overline{\text{RFQ2}}$$

$$\text{RFQ3} := \overline{\text{RFQ2}} \cdot \overline{\text{RFQ3}} + \overline{\text{RFQ2}} \cdot \text{RFQ3}$$

$$\text{RFQ4} := \text{RFQ2} \cdot \text{RFQ3} \cdot \overline{\text{RFQ4}} + \overline{\text{RFQ2}} \cdot \text{RFQ4} + \overline{\text{RFQ3}} \cdot \text{RFQ4}$$

$$\text{RFQ5} := \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \overline{\text{RFQ5}} + \overline{\text{RFQ2}} \cdot \text{RFQ5} + \overline{\text{RFQ3}} \cdot \text{RFQ5} + \overline{\text{RFQ4}} \cdot \text{RFQ5}$$

$$\text{RFQ6} := \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \overline{\text{RFQ6}} + \overline{\text{RFQ2}} \cdot \text{RFQ6} + \overline{\text{RFQ3}} \cdot \text{RFQ6} + \overline{\text{RFQ4}} \cdot \text{RFQ6} + \overline{\text{RFQ5}} \cdot \text{RFQ6}$$

$$\text{RFQ7} := \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \overline{\text{RFQ7}} + \overline{\text{RFQ2}} \cdot \text{RFQ7} + \overline{\text{RFQ3}} \cdot \text{RFQ7} + \overline{\text{RFQ4}} \cdot \text{RFQ7} + \overline{\text{RFQ5}} \cdot \text{RFQ7} + \overline{\text{RFQ6}} \cdot \text{RFQ7}$$

$$\text{RFQ8} := \overline{\text{RFQ2}} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \overline{\text{RFQ8}} + \overline{\text{RFQ2}} \cdot \text{RFQ8} + \overline{\text{RFQ3}} \cdot \text{RFQ8} + \overline{\text{RFQ4}} \cdot \text{RFQ8} + \overline{\text{RFQ5}} \cdot \text{RFQ8} + \overline{\text{RFQ6}} \cdot \text{RFQ8} + \overline{\text{RFQ7}} \cdot \text{RFQ8}$$

$$\text{RFQ9} := \overline{\text{RFQ2}} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \text{RFQ8} \cdot \overline{\text{RFQ9}} + \overline{\text{RFQ2}} \cdot \text{RFQ9} + \overline{\text{RFQ3}} \cdot \text{RFQ9} + \overline{\text{RFQ4}} \cdot \text{RFQ9} + \overline{\text{RFQ5}} \cdot \text{RFQ9} + \overline{\text{RFQ6}} \cdot \text{RFQ9} + \overline{\text{RFQ7}} \cdot \text{RFQ9} + \overline{\text{RFQ8}} \cdot \text{RFQ9}$$

10623C-045

Figure 7-3 AmPAL22V10-25 SCDRAM Refresh Counter/Request Generator Device U2 (continued)

$$\begin{aligned} \text{RFQ10} &:= \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \text{RFQ8} \cdot \text{RFQ9} \cdot \overline{\text{RFQ10}} \\ &+ \overline{\text{RFQ2}} \cdot \text{RFQ10} \\ &+ \overline{\text{RFQ3}} \cdot \text{RFQ10} \\ &+ \overline{\text{RFQ4}} \cdot \text{RFQ10} \\ &+ \overline{\text{RFQ5}} \cdot \text{RFQ10} \\ &+ \overline{\text{RFQ6}} \cdot \text{RFQ10} \\ &+ \overline{\text{RFQ7}} \cdot \text{RFQ10} \\ &+ \overline{\text{RFQ8}} \cdot \text{RFQ10} \\ &+ \overline{\text{RFQ9}} \cdot \text{RFQ10} \end{aligned}$$

$$\begin{aligned} \text{SYNCHRONOUS PRESET} &= \text{RFQ2} \cdot \overline{\text{RFQ3}} \cdot \text{RFQ4} \cdot \overline{\text{RFQ5}} \cdot \overline{\text{RFQ6}} \cdot \overline{\text{RFQ7}} \cdot \overline{\text{RFQ8}} \\ &\cdot \text{RFQ9} \cdot \text{RFQ10} \end{aligned}$$

$$\text{RFRQ1} := \text{RFRQ1} \cdot (\overline{\text{RFACK}} \cdot \overline{\text{RQ1}})$$

Figure 7-4 PAL16R6-D DRAM Refresh State Generator—Interleaved Device U15

CLK $\overline{\text{IBACK}}$ $\overline{\text{DBACK1}}$ $\overline{\text{RFRQ1}}$ $\overline{\text{DBREQ.D}}$ $\overline{\text{DQ1}}$ $\overline{\text{PC1}}$ RW NC9 GND
OE DWBP $\overline{\text{DWBP1}}$ $\overline{\text{DWBP2}}$ RFACK RQ1 RQ2 RQ3 REXIT VCC

$$\begin{aligned} \text{RFACK} &:= \overline{\text{DBACK1}} \cdot \overline{\text{IBACK}} \cdot \text{RFRQ1} \\ &+ \text{RFACK} \cdot (\overline{\text{RFRQ1}} \cdot \text{RQ3}) \end{aligned}$$

$$\begin{aligned} \text{RQ1} &:= \overline{\text{RQ1}} \cdot \overline{\text{PC1}} \cdot \text{RFACK} \\ &+ \text{RQ1} \cdot \overline{\text{RQ3}} \end{aligned}$$

$$\text{RQ2} := \text{RQ1} \cdot \overline{\text{RQ3}}$$

$$\text{RQ3} := \text{RQ2} \cdot \overline{\text{RQ3}}$$

$$\begin{aligned} \text{REXIT} &= \overline{\text{RFACK}} \\ &+ \text{RQ3} \end{aligned}$$

$$\text{DWBP} = \text{DBACK1} \cdot \overline{\text{RW}} \cdot \text{DBREQ.D} \cdot \text{RFRQ1} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DWBP2}}$$

$$\text{DWBP1} := \overline{\text{DWBP1}} \cdot \text{DWBP}$$

$$\text{DWBP2} := \overline{\text{DWBP2}} \cdot \text{DWBP1}$$

10623C-046

Figure 7-5 PAL16R6-D DRAM Precharge State Generator—Interleaved Device U16

CLK $\overline{\text{ISTART}}$ $\overline{\text{DSTART}}$ $\overline{\text{IEXIT}}$ NC5 $\overline{\text{DEXIT}}$ NC7 $\overline{\text{RQ3}}$ $\overline{\text{BINV}}$ GND
 OE $\overline{\text{DWBP}}$ $\overline{\text{IBACK}}$ $\overline{\text{DBACK}}$ $\overline{\text{DBACKI}}$ $\overline{\text{PC1}}$ $\overline{\text{PC2}}$ NC18 NC19 VCC

$$\text{IBACK} := \overline{\text{BINV}} \cdot \text{ISTART} + \overline{\text{IEXIT}}$$

$$\text{DBACK} := \overline{\text{BINV}} \cdot \text{DSTART} + \overline{\text{DEXIT}}$$

$$\text{DBACKI} := \overline{\text{BINV}} \cdot \text{DSTART} + \overline{\text{DEXIT}} + \overline{\text{DWBP}}$$

$$\text{PC1} := \overline{\text{PC1}} \cdot \text{IBACK} \cdot \text{IEXIT} + \overline{\text{PC1}} \cdot \text{DBACKI} \cdot \overline{\text{DWBP}} \cdot \text{DEXIT} + \overline{\text{PC1}} \cdot \text{RQ3}$$

$$\text{PC2} := \overline{\text{PC1}} \cdot \overline{\text{PC2}}$$

10623C-047

Figure 7-6 PAL20L8-B DRAM State Decoder—Interleaved Device U4

$\overline{\text{RFRQ1}}$ $\overline{\text{IREQ}}$ $\overline{\text{DREQT0}}$ $\overline{\text{DREQT1}}$ $\overline{\text{IREQT}}$ $\overline{\text{PIN169}}$ A31 A30 A29 A28 A27 GND
 $\overline{\text{RFACK}}$ $\overline{\text{DREQ}}$ $\overline{\text{ISTART}}$ $\overline{\text{IEXIT}}$ $\overline{\text{IBACK}}$ $\overline{\text{DBACKI}}$ $\overline{\text{PC1}}$ $\overline{\text{PC2}}$ $\overline{\text{START}}$ NC18 $\overline{\text{IQ1}}$ VCC

$$\text{ISTART} = \overline{\text{DBACKI}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}} \cdot \text{IME}$$

$$\text{START} = \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IBACK} + \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBACKI} + \overline{\text{PC1}} \cdot \text{RFACK}$$

$$\text{IEXIT} = \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DME} + \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IREQ} + \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{RFRQ1} + \overline{\text{IBACK}}$$

NOTE: In the above equations, IME and DME are used only for clarity. The actual input terms should be substituted when compiling this device.

$$\text{DME} = \overline{\text{DREQ}} \cdot \overline{\text{DREQT0}} \cdot \overline{\text{DREQT1}} \cdot \text{A31} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{PIN169}} \cdot \overline{\text{RFRQ1}}$$

$$\text{IME} = \overline{\text{IREQ}} \cdot \overline{\text{IREQT}} \cdot \overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{PIN169}} \cdot \overline{\text{RFRQ1}}$$

10623C-048

Figure 7-7 PAL20L8-B DRAM State Decoder—Interleaved Device U5

$\overline{\text{RFRQ1}}$ $\overline{\text{IREQ}}$ $\overline{\text{DREQT0}}$ $\overline{\text{DREQT1}}$ $\overline{\text{PIN169}}$ $\overline{\text{IREQT}}$ A31 A30 A29 A28 A27 GND
 $\overline{\text{RFACK}}$ $\overline{\text{DREQ}}$ $\overline{\text{DSTART}}$ $\overline{\text{DEXIT}}$ $\overline{\text{DBREQ.D}}$ $\overline{\text{IBACK}}$ $\overline{\text{DBACKI}}$ PC1 PC2 NC18 DQ1 VCC

$$\text{DSTART} = \overline{\text{IBACK}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}} \cdot \text{DME}$$

$$\begin{aligned} \text{DEXIT} &= \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IME} \cdot \overline{\text{DBREQ.D}} \\ &+ \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{RFRQ1}} \\ &+ \overline{\text{DBACKI}} \end{aligned}$$

NOTE: In the above equations, IME and DME are used only for clarity. The actual input terms should be substituted when compiling this device.

$$\text{IME} = \overline{\text{IREQ}} \cdot \overline{\text{IREQT}} \cdot \overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{PIN169}} \cdot \overline{\text{RFRQ1}}$$

$$\begin{aligned} \text{DME} &= \overline{\text{DREQ}} \cdot \overline{\text{DREQT0}} \cdot \overline{\text{DREQT1}} \cdot \overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{PIN169}} \\ &\cdot \overline{\text{RFRQ1}} \end{aligned}$$

10623C-049

Figure 7-8 PAL16R4-D DRAM Instruction State Generator—Interleaved Device U17

CLK $\overline{\text{IBACK}}$ $\overline{\text{ISTART}}$ $\overline{\text{PC1}}$ $\overline{\text{PC2}}$ $\overline{\text{Q02E}}$ $\overline{\text{IBREQ.D}}$ $\overline{\text{BINV.D}}$ $\overline{\text{BINV}}$ GND
 $\overline{\text{OE}}$ $\overline{\text{IOE0}}$ $\overline{\text{IOE1}}$ IQ1 $\overline{\text{IQ2}}$ $\overline{\text{IQ3}}$ $\overline{\text{IBACK.D}}$ $\overline{\text{IRDY}}$ NC19 VCC

$$\text{IBACK.D} := \text{IBACK}$$

$$\begin{aligned} \text{IQ1} &:= \overline{\text{BINV}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{ISTART}} \cdot \overline{\text{IBACK}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IBACK} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{IQ3}} \end{aligned}$$

$$\text{IQ2} := \overline{\text{IQ1}} \cdot \overline{\text{IQ3}}$$

$$\text{IQ3} := \overline{\text{IQ2}} \cdot \overline{\text{IQ3}}$$

$$\begin{aligned} \text{IRDY} &= \overline{\text{IQ3}} \\ &+ \overline{\text{BINV.D}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{IBREQ.D}} \cdot \overline{\text{IBACK.D}} \end{aligned}$$

$$\begin{aligned} \text{IOE0} &= \overline{\text{Q02E}} \cdot \overline{\text{IQ3}} \\ &+ \overline{\text{BINV.D}} \cdot \overline{\text{Q02E}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{IBREQ.D}} \cdot \overline{\text{IBACK.D}} \end{aligned}$$

$$\begin{aligned} \text{IOE1} &= \overline{\text{Q02E}} \cdot \overline{\text{IQ3}} \\ &+ \overline{\text{BINV.D}} \cdot \overline{\text{Q02E}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{IBREQ.D}} \cdot \overline{\text{IBACK.D}} \end{aligned}$$

10623C-050

Figure 7-9 PAL16R4-D DRAM Data State Generator—Interleaved Device U18

$\overline{\text{CLK}}$ $\overline{\text{DSTART}}$ $\overline{\text{DBACK}}$ $\overline{\text{PC1}}$ $\overline{\text{PC2}}$ $\overline{\text{Q02E}}$ $\overline{\text{DBREQ.D}}$ $\overline{\text{BINV}}$ $\overline{\text{RW}}$ $\overline{\text{GND}}$
 $\overline{\text{OE}}$ $\overline{\text{DOE0}}$ $\overline{\text{DOE1}}$ $\overline{\text{DQ1}}$ $\overline{\text{DQ2}}$ $\overline{\text{DQ3}}$ $\overline{\text{DBACK.D}}$ $\overline{\text{DRDY}}$ $\overline{\text{BINV.D}}$ $\overline{\text{VCC}}$

$\overline{\text{DBACK.D}} := \overline{\text{DBACK}}$

$\overline{\text{DQ1}} := \overline{\text{BINV}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DSTART}} \cdot \overline{\text{DBACK}}$
 $+ \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{DBACK}}$
 $+ \overline{\text{DQ1}} \cdot \overline{\text{DQ3}}$

$\overline{\text{DQ2}} := \overline{\text{DQ1}} \cdot \overline{\text{DQ3}}$

$\overline{\text{DQ3}} := \overline{\text{DQ2}} \cdot \overline{\text{DQ3}}$
 $+ \overline{\text{BINV.D}} \cdot \overline{\text{RW}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{DBREQ.D}} \cdot \overline{\text{DBACK.D}}$
 $+ \overline{\text{RW}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{DQ3}}$
 $+ \overline{\text{BINV.D}} \cdot \overline{\text{RW}} \cdot \overline{\text{DQ3}} \cdot \overline{\text{DBREQ.D}} \cdot \overline{\text{DBACK.D}}$
 $+ \overline{\text{BINV.D}} \cdot \overline{\text{RW}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{DBREQ.D}} \cdot \overline{\text{DBACK.D}}$

$\overline{\text{DOE0}} = \overline{\text{RW}} \cdot \overline{\text{Q02E}} \cdot \overline{\text{DQ3}}$
 $+ \overline{\text{BINV.D}} \cdot \overline{\text{RW}} \cdot \overline{\text{Q02E}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{DBREQ.D}} \cdot \overline{\text{DBACK.D}}$

$\overline{\text{DOE1}} = \overline{\text{RW}} \cdot \overline{\text{Q02E}} \cdot \overline{\text{DQ3}}$
 $+ \overline{\text{BINV.D}} \cdot \overline{\text{RW}} \cdot \overline{\text{Q02E}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \overline{\text{DBREQ.D}} \cdot \overline{\text{DBACK.D}}$

10623C-051

Figure 7-10 PAL16R6-D DRAM RAS Generator—Interleaved Device U19

CLK $\overline{\text{I}}\text{START}$ $\overline{\text{D}}\text{START}$ $\overline{\text{I}}\text{EXIT}$ NC5 $\overline{\text{D}}\text{EXIT}$ NC7 $\overline{\text{R}}\text{EXIT}$ $\overline{\text{B}}\text{INV}$ GND
 $\overline{\text{O}}\text{E}$ $\overline{\text{S}}\text{TART}$ $\overline{\text{R}}\text{AS0H}$ $\overline{\text{R}}\text{AS0L}$ $\overline{\text{R}}\text{AS1H}$ $\overline{\text{R}}\text{AS1L}$ $\overline{\text{R}}\text{AS}$ NC18 $\overline{\text{D}}\text{WBP}$ VCC

$$\begin{aligned} \text{RAS0H} &:= \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS0H} \cdot \text{I}\text{START} \\ &+ \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS0H} \cdot \text{D}\text{START} \\ &+ \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS0H} \cdot \text{S}\text{TART} \\ &+ \text{R}\text{AS0H} \cdot \overline{\text{I}}\text{EXIT} \\ &+ \text{R}\text{AS0H} \cdot \overline{\text{D}}\text{EXIT} \\ &+ \text{R}\text{AS0H} \cdot \overline{\text{R}}\text{EXIT} \\ &+ \text{R}\text{AS0H} \cdot \overline{\text{D}}\text{WBP} \end{aligned}$$

$$\begin{aligned} \text{RAS0L} &:= \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS0L} \cdot \text{I}\text{START} \\ &+ \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS0L} \cdot \text{D}\text{START} \\ &+ \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS0L} \cdot \text{S}\text{TART} \\ &+ \text{R}\text{AS0L} \cdot \overline{\text{I}}\text{EXIT} \\ &+ \text{R}\text{AS0L} \cdot \overline{\text{D}}\text{EXIT} \\ &+ \text{R}\text{AS0L} \cdot \overline{\text{R}}\text{EXIT} \\ &+ \text{R}\text{AS0L} \cdot \overline{\text{D}}\text{WBP} \end{aligned}$$

$$\begin{aligned} \text{RAS1H} &:= \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS1H} \cdot \text{I}\text{START} \\ &+ \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS1H} \cdot \text{D}\text{START} \\ &+ \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS1H} \cdot \text{S}\text{TART} \\ &+ \text{R}\text{AS1H} \cdot \overline{\text{I}}\text{EXIT} \\ &+ \text{R}\text{AS1H} \cdot \overline{\text{D}}\text{EXIT} \\ &+ \text{R}\text{AS1H} \cdot \overline{\text{R}}\text{EXIT} \\ &+ \text{R}\text{AS1H} \cdot \overline{\text{D}}\text{WBP} \end{aligned}$$

$$\begin{aligned} \text{RAS1L} &:= \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS1L} \cdot \text{I}\text{START} \\ &+ \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS1L} \cdot \text{D}\text{START} \\ &+ \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS1L} \cdot \text{S}\text{TART} \\ &+ \text{R}\text{AS1L} \cdot \overline{\text{I}}\text{EXIT} \\ &+ \text{R}\text{AS1L} \cdot \overline{\text{D}}\text{EXIT} \\ &+ \text{R}\text{AS1L} \cdot \overline{\text{R}}\text{EXIT} \\ &+ \text{R}\text{AS1L} \cdot \overline{\text{D}}\text{WBP} \end{aligned}$$

$$\begin{aligned} \text{RAS} &:= \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS} \cdot \text{I}\text{START} \\ &+ \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS} \cdot \text{D}\text{START} \\ &+ \overline{\text{B}}\text{INV} \cdot \overline{\text{R}}\text{AS} \cdot \text{S}\text{TART} \\ &+ \text{R}\text{AS} \cdot \overline{\text{I}}\text{EXIT} \\ &+ \text{R}\text{AS} \cdot \overline{\text{D}}\text{EXIT} \\ &+ \text{R}\text{AS} \cdot \overline{\text{R}}\text{EXIT} \\ &+ \text{R}\text{AS} \cdot \overline{\text{D}}\text{WBP} \end{aligned}$$

10623C-052

Figure 7-11 PAL16R6-D DRAM CAS Generator—Interleaved Device U20

$\overline{\text{CLK}}$ $\overline{\text{Q02E}}$ $\overline{\text{IBACK}}$ $\overline{\text{DBACKI}}$ $\overline{\text{RBACK}}$ $\overline{\text{RAS}}$ $\overline{\text{RFRQ1}}$ $\overline{\text{RW}}$ $\overline{\text{DRDY}}$ $\overline{\text{GND}}$
 $\overline{\text{OE}}$ NC12 CAS0H CAS0L CAS1H CAS1L WE0 WE1 NC19 VCC

$\text{CAS0H} := \text{RAS} \cdot \text{IBACK}$
 $+ \text{RAS} \cdot \text{DBACKI} \cdot \text{RW}$
 $+ \text{RAS} \cdot \text{DBACKI} \cdot \overline{\text{RW}} \cdot \overline{\text{Q02E}} \cdot \text{DRDY}$
 $+ \text{RAS} \cdot \overline{\text{IBACK}} \cdot \overline{\text{DBACKI}} \cdot \text{RFRQ1}$

$\text{CAS0L} := \text{RAS} \cdot \text{IBACK}$
 $+ \text{RAS} \cdot \text{DBACKI} \cdot \text{RW}$
 $+ \text{RAS} \cdot \text{DBACKI} \cdot \overline{\text{RW}} \cdot \overline{\text{Q02E}} \cdot \text{DRDY}$
 $+ \text{RAS} \cdot \overline{\text{IBACK}} \cdot \overline{\text{DBACKI}} \cdot \text{RFRQ1}$

$\text{CAS1H} := \text{RAS} \cdot \text{IBACK}$
 $+ \text{RAS} \cdot \text{DBACKI} \cdot \text{RW}$
 $+ \text{RAS} \cdot \text{DBACKI} \cdot \overline{\text{RW}} \cdot \text{Q02E} \cdot \text{DRDY}$
 $+ \text{RAS} \cdot \overline{\text{IBACK}} \cdot \overline{\text{DBACKI}} \cdot \text{RFRQ1}$

$\text{CAS1L} := \text{RAS} \cdot \text{IBACK}$
 $+ \text{RAS} \cdot \text{DBACKI} \cdot \text{RW}$
 $+ \text{RAS} \cdot \text{DBACKI} \cdot \overline{\text{RW}} \cdot \text{Q02E} \cdot \text{DRDY}$
 $+ \text{RAS} \cdot \overline{\text{IBACK}} \cdot \overline{\text{DBACKI}} \cdot \text{RFRQ1}$

$\text{WE0} := \text{DBACKI} \cdot \overline{\text{RW}}$

$\text{WE1} := \text{DBACKI} \cdot \overline{\text{RW}}$

10623C-053

Figure 7-12 PAL16L8-B DRAM Counter Load—Interleaved Device U1

$\overline{\text{IBREQ.D}}$ $\overline{\text{DBREQ.D}}$ $\overline{\text{IBACK}}$ $\overline{\text{DBACKI}}$ $\overline{\text{IQ1}}$ $\overline{\text{IQ2}}$ $\overline{\text{IQ3}}$ $\overline{\text{IREQ}}$ $\overline{\text{DREQ}}$ $\overline{\text{GND}}$
 $\overline{\text{RW}}$ CNT0 LD DQ1 DQ2 DQ3 PC1 PC2 CNT1 VCC

$\text{LD} = \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{DBACKI}} \cdot \text{IREQ}$
 $+ \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{IBACK}} \cdot \text{DREQ}$

$\text{CNT0} = \text{IBACK} \cdot \text{IQ2}$
 $+ \text{IBACK} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IBREQ.D}$
 $+ \text{DBACKI} \cdot \text{RW} \cdot \text{DQ2}$
 $+ \text{DBACKI} \cdot \text{RW} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D}$
 $+ \text{DBACKI} \cdot \overline{\text{RW}} \cdot \text{DQ2} \cdot \text{DQ3}$
 $+ \text{DBACKI} \cdot \overline{\text{RW}} \cdot \text{DQ3} \cdot \text{DBREQ.D}$
 $+ \text{DBACKI} \cdot \overline{\text{RW}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D}$

$\text{CNT1} = \text{IBACK} \cdot \text{IQ3}$
 $+ \text{IBACK} \cdot \overline{\text{IQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{IBREQ.D}$
 $+ \text{DBACKI} \cdot \text{RW} \cdot \text{DQ3}$
 $+ \text{DBACKI} \cdot \text{RW} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D}$
 $+ \text{DBACKI} \cdot \overline{\text{RW}} \cdot \text{DQ3} \cdot \text{DBREQ.D}$
 $+ \text{DBACKI} \cdot \overline{\text{RW}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{PC2}} \cdot \text{DBREQ.D}$

10623C-054

Figure 7-13 PAL16R4-D DRAM Address Counter—Interleaved Section 0—Even Bank Device U6

CLK $\overline{\text{CNT0}}$ $\overline{\text{LD}}$ A02 A03 A04 A05 NC8 CLKD GND
 OE $\overline{\text{DLE0}}$ $\overline{\text{DLE1}}$ Q02E Q03E Q04E Q05E $\overline{\text{BINV}}$ $\overline{\text{COUT0}}$ VCC

$$\begin{aligned} \text{Q02E} &:= \overline{\text{LD}} \cdot \text{A02} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{Q02E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \overline{\text{Q02E}} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{BINV}} \cdot \text{Q02E} \end{aligned}$$

$$\begin{aligned} \text{Q03E} &:= \overline{\text{LD}} \cdot \text{A03} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{Q03E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{Q02E} \cdot \overline{\text{Q03E}} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \overline{\text{Q02E}} \cdot \text{Q03E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{BINV}} \cdot \text{Q03E} \end{aligned}$$

$$\begin{aligned} \text{Q04E} &:= \overline{\text{LD}} \cdot \text{A04} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{Q04E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{Q02E} \cdot \text{Q03E} \cdot \overline{\text{Q04E}} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \overline{\text{Q02E}} \cdot \text{Q04E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \overline{\text{Q03E}} \cdot \text{Q04E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{BINV}} \cdot \text{Q04E} \end{aligned}$$

$$\begin{aligned} \text{Q05E} &:= \overline{\text{LD}} \cdot \text{A05} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{Q05E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{Q02E} \cdot \text{Q03E} \cdot \text{Q04E} \cdot \overline{\text{Q05E}} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \overline{\text{Q02E}} \cdot \text{Q05E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \overline{\text{Q03E}} \cdot \text{Q05E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{Q04E} \cdot \text{Q05E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{BINV}} \cdot \text{Q05E} \end{aligned}$$

$$\overline{\text{COUT0}} = \text{Q02E} \cdot \text{Q03E} \cdot \text{Q04E} \cdot \text{Q05E}$$

$$\overline{\text{DLE0}} = \text{Q02E} + \overline{\text{CLKD}}$$

$$\overline{\text{DLE1}} = \overline{\text{Q02E}} + \overline{\text{CLKD}}$$

10623C-055

Figure 7-14 PAL16R6-D DRAM Address Counter—Interleaved Section 1—Even Bank Device U7

CLK $\overline{\text{CNT0}}$ $\overline{\text{LD}}$ A06 A07 A08 A09 A10 A11 GND
 OE $\overline{\text{CIN0}}$ Q06E Q07E Q08E Q09E Q10 Q11 $\overline{\text{BINV}}$ VCC

$$\begin{aligned} \text{Q06E} &:= \overline{\text{LD}} \cdot \text{A06} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \overline{\text{Q06E}} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \overline{\text{CIN0}} \cdot \text{Q06E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{CIN0} \cdot \overline{\text{Q06E}} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{BINV}} \cdot \text{Q06E} \end{aligned}$$

$$\begin{aligned} \text{Q07E} &:= \overline{\text{LD}} \cdot \text{A07} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{Q07E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \overline{\text{CIN0}} \cdot \text{Q06E} \cdot \overline{\text{Q07E}} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{CIN0} \cdot \overline{\text{Q07E}} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{LD}} \cdot \overline{\text{CNT0}} \cdot \text{Q06E} \cdot \text{Q07E} \cdot \overline{\text{BINV}} \\ &+ \overline{\text{BINV}} \cdot \text{Q07E} \end{aligned}$$

10623C-056

Figure 7-14 PAL16R6-D DRAM Address Counter—Interleaved Section 1—Even Bank Device U7 (continued)

$$\begin{aligned}
 Q08E &:= \overline{LD} \cdot A08 \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot \overline{CNT0} \cdot Q08E \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT0 \cdot \overline{CIN0} \cdot Q06E \cdot Q07E \cdot \overline{Q08E} \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT0 \cdot \overline{CIN0} \cdot Q08E \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT0 \cdot \overline{Q06E} \cdot Q08E \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT0 \cdot Q07E \cdot Q08E \cdot \overline{BINV} \\
 &+ \overline{BINV} \cdot Q08E \\
 \\
 Q09E &:= \overline{LD} \cdot A09 \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot \overline{CNT0} \cdot Q09E \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT0 \cdot \overline{CIN0} \cdot Q06E \cdot Q07E \cdot Q08E \cdot \overline{Q09E} \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT0 \cdot \overline{CIN0} \cdot Q09E \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT0 \cdot \overline{Q06E} \cdot Q09E \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT0 \cdot \overline{Q07E} \cdot Q09E \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT0 \cdot Q08E \cdot Q09E \cdot \overline{BINV} \\
 &+ \overline{BINV} \cdot Q09E
 \end{aligned}$$

NOTE: Even bank counter holds Q10 and Q11; odd bank counter holds Q12 and Q13.

$$Q10 := \overline{LD} \cdot A10 + \overline{LD} \cdot Q10$$

$$Q11 := \overline{LD} \cdot A11 + \overline{LD} \cdot Q11$$

Figure 7-15 PAL16R4-D DRAM Address Counter—Interleaved Section 0—Odd Bank Device U9

CLK $\overline{CNT1}$ \overline{LD} A02 A03 A04 A05 NC8 NC9 GND
 \overline{OE} NC12 NC13 $\overline{Q02O}$ $\overline{Q03O}$ $\overline{Q04O}$ $\overline{Q05O}$ \overline{BINV} $\overline{COUT1}$ VCC

$$\begin{aligned}
 Q02O &:= \overline{LD} \cdot A02 \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot \overline{CNT1} \cdot Q02O \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT1 \cdot Q02O \cdot \overline{BINV} \\
 &+ \overline{BINV} \cdot Q02O \\
 \\
 Q03O &:= \overline{LD} \cdot A03 \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot \overline{CNT1} \cdot Q03O \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT1 \cdot Q02O \cdot \overline{Q03O} \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT1 \cdot Q02O \cdot Q03O \cdot \overline{BINV} \\
 &+ \overline{BINV} \cdot Q03O \\
 \\
 Q04O &:= \overline{LD} \cdot A04 \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot \overline{CNT1} \cdot Q04O \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT1 \cdot Q02O \cdot Q03O \cdot \overline{Q04O} \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT1 \cdot \overline{Q02O} \cdot Q04O \cdot \overline{BINV} \\
 &+ \overline{LD} \cdot CNT1 \cdot Q03O \cdot Q04O \cdot \overline{BINV} \\
 &+ \overline{BINV} \cdot Q04O
 \end{aligned}$$

Figure 7-17 PAL16L8-D DRAM Row Address Latch—Interleaved Device U8

CLKD	$\overline{IQ1}$	A13	A14	A15	A16	A17	$\overline{PC1}$	$\overline{PC2}$	GND	
DQ1	NC12	LA13	LA14	LA15	LA16	LA17	LA17	NC18	NC19	VCC

$$\begin{aligned} \text{LA13} &= \overline{\text{ALE}} \cdot \text{A13} \\ &+ \overline{\text{ALE}} \cdot \text{LA13} \\ &+ \text{A13} \cdot \text{LA13} \end{aligned}$$

$$\begin{aligned} \text{LA14} &= \overline{\text{ALE}} \cdot \text{A14} \\ &+ \overline{\text{ALE}} \cdot \text{LA14} \\ &+ \text{A14} \cdot \text{LA14} \end{aligned}$$

$$\begin{aligned} \text{LA15} &= \overline{\text{ALE}} \cdot \text{A15} \\ &+ \overline{\text{ALE}} \cdot \text{LA15} \\ &+ \text{A15} \cdot \text{LA15} \end{aligned}$$

$$\begin{aligned} \text{LA16} &= \overline{\text{ALE}} \cdot \text{A16} \\ &+ \overline{\text{ALE}} \cdot \text{LA16} \\ &+ \text{A16} \cdot \text{LA16} \end{aligned}$$

$$\begin{aligned} \text{LA17} &= \overline{\text{ALE}} \cdot \text{A17} \\ &+ \overline{\text{ALE}} \cdot \text{LA17} \\ &+ \text{A17} \cdot \text{LA17} \end{aligned}$$

NOTE: The term ALE is used for clarity only. The true form of ALE is:

$$\text{ALE} = \overline{IQ1} \cdot \overline{DQ1} \cdot \overline{PC1} \cdot \overline{PC2} \cdot \text{CLKD}$$

Figure 7-18 PAL16L8-D DRAM Row Address Latch—Interleaved Device U11

CLKD	$\overline{IQ1}$	A18	A19	A20	A21	A22	$\overline{PC1}$	$\overline{PC2}$	GND	
DQ1	NC12	LA18	LA19	LA20	LA21	LA22	LA22	NC18	NC19	VCC

$$\begin{aligned} \text{LA18} &= \overline{\text{ALE}} \cdot \text{A18} \\ &+ \overline{\text{ALE}} \cdot \text{LA18} \\ &+ \text{A18} \cdot \text{LA18} \end{aligned}$$

$$\begin{aligned} \text{LA19} &= \overline{\text{ALE}} \cdot \text{A19} \\ &+ \overline{\text{ALE}} \cdot \text{LA19} \\ &+ \text{A19} \cdot \text{LA19} \end{aligned}$$

$$\begin{aligned} \text{LA20} &= \overline{\text{ALE}} \cdot \text{A20} \\ &+ \overline{\text{ALE}} \cdot \text{LA20} \\ &+ \text{A20} \cdot \text{LA20} \end{aligned}$$

$$\begin{aligned} \text{LA21} &= \overline{\text{ALE}} \cdot \text{A21} \\ &+ \overline{\text{ALE}} \cdot \text{LA21} \\ &+ \text{A21} \cdot \text{LA21} \end{aligned}$$

$$\begin{aligned} \text{LA22} &= \overline{\text{ALE}} \cdot \text{A22} \\ &+ \overline{\text{ALE}} \cdot \text{LA22} \\ &+ \text{A22} \cdot \text{LA22} \end{aligned}$$

NOTE: The term ALE is used for clarity only. The true form of the ALE signal is:

$$\text{ALE} = \overline{IQ1} \cdot \overline{DQ1} \cdot \overline{PC1} \cdot \overline{PC2} \cdot \text{CLKD}$$

10623C-060

Figure 7-19 PAL16R8-D DRAM Write Enable Controls Device U112 (continued)

$\begin{aligned} \text{WE107} & := \overline{\text{OPT2}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{RW}} \cdot \text{DSTART} \\ & + \overline{\text{OPT2}} \cdot \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \overline{\text{BO}} \cdot \overline{\text{A1}} \cdot \overline{\text{A0}} \cdot \overline{\text{RW}} \cdot \text{DSTART} \\ & + \overline{\text{OPT2}} \cdot \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \text{BO} \cdot \overline{\text{A1}} \cdot \overline{\text{A0}} \cdot \overline{\text{RW}} \cdot \text{DSTART} \\ & + \overline{\text{OPT2}} \cdot \text{OPT1} \cdot \overline{\text{OPT0}} \cdot \overline{\text{BO}} \cdot \overline{\text{A1}} \cdot \overline{\text{RW}} \cdot \text{DSTART} \\ & + \overline{\text{OPT2}} \cdot \text{OPT1} \cdot \overline{\text{OPT0}} \cdot \text{BO} \cdot \overline{\text{A1}} \cdot \overline{\text{RW}} \cdot \text{DSTART} \\ & + \text{WE107} \cdot \text{DBACKI} \end{aligned}$;Word ;Byte, Big ;Byte, Little ;HW, Big ;HW, Little
---	---

Intra-Cycle Timing

This memory architecture has three basic cycle timings. The first is a cycle used to decode the memory address and control signals from the processor. At the end of this decode cycle, the address is loaded into the address counter and the selected block of memory begins its initial access in the next clock cycle. Following the decode cycle is the row-address cycle in which the row address is made active at the beginning of the cycle, and in which the address multiplexer is later switched between the row address and the column address.

The third cycle timing is that of a burst access. The first burst access time is the time required to access one of the memory banks. This time is designed to fit within two clock cycles, so the initial burst-access time will be two cycles.

The combination of a decode cycle, followed by the row-address cycle, followed by the first burst-access time defines a four-cycle initial access time.

After the initial access, all burst accesses use the two-clock-cycle timing of the initial burst access. Because two memory banks are interleaved, the apparent access time from the viewpoint of the system bus is only one cycle per burst access following the initial access.

Decode Timing

Within the decode cycle the address timing path is made up of:

- The Am29000 processor clock to address and control valid delay of 14 ns
- Address decode logic PAL device delay of 10 ns (devices, U4 and U5)
- The setup time of the address counter PAL device, 10 ns (devices, U6-U11)


Assuming D-speed PAL devices, those times total 34 ns, as shown in Figure 7-20.

Also, within the decode cycle time is the control signal to response signal path. In fact, this timing path is present in every cycle in the sense that the memory response signals must be valid in every clock cycle. This delay path is made up of:

- Clock-to-output time of registers within the control logic state machine PAL device, 8 ns
- Propagation delay of the control logic PAL device, 10 ns
- Propagation delay of a logical OR gate on the response signals from each memory block, 10 ns
- Control signal setup time of the processor, 12 ns

Again, assuming D-speed PAL devices, these times total 40 ns, as shown in Figure 7-19.

Figure 7-20 SCDRAM Interleaved Bank Memory Decode Cycle

 

Row Address Timing

Within the row address cycle, the \overline{RAS} line goes Low which initiates a time delay signal which later causes the address multiplexer to change from the row to the column address as shown in Figure 7-21.

The \overline{RAS} delay path is made up of:

- Clock-to-output time of \overline{RAS} signal registers within the control logic state machine PAL device (8 ns) plus an added delay due to capacitive and inductive loading by the memory array of the PAL device outputs.

The Address path is made up of:

- Clock-to-output time of \overline{RAS} output not loaded by memory array, 8 ns
- Delay-line time, 16 ns
- Minimum and maximum switch time of the multiplexer, 4 ns to 9.5 ns
- Memory load delay of 6.5 ns

Figure 7-21 SCDRAM Interleaved Bank Memory \overline{RAS} Cycle


 


Figure 7-22 SCDRAM Interleaved Bank Memory Burst Access

 

This works out to satisfy the 15 ns of required hold time of address after RAS goes active. Also, the column address is settled by 40 ns into the cycle.

Burst Timing

Within the burst access cycle, the address to data path timing is determined by:

- The clock to output time of the address counter (8 ns for a D-speed PAL device)
- Memory access time in static column mode, 45 ns
- Data buffer delay (FCT244A = 4.3 ns)
- The processor set-up time (6 ns)

Those delays total 76.3-ns worst case as shown in Figure 7-22.

Parts List

The part list for the Am29000 Interleaved Dynamic RAM Interface is provided in Table 7-1.

Table 7-1 Am29000 Interleaved Dynamic RAM Interface Parts List

Item No.	Quantity	Device Description
U1	1	PAL16L8-B
U2	1	AmPAL22V10-25
U4, U5	2	PAL20L8-B
U6,U9,U17,U18	4	PAL16R4-D
U7,U10,U15,U16, U19, U20	6	PAL16R6-D
U8, U11	2	PAL16L8-B
U21-U85	64	TC511002-85
U3	1	74F175
U12-U14, U114-U116	6	74F158
U86-U94	8	Am29C843A
U95-U110	16	IDT74FCT244A
U111	1	MTTLDL-8
U112	1	PAL16R8-D

113 packages

DATA MEMORY

The instruction and data memories for the Am29000 processor are separate structures. The data memory can be an exact subset of the instruction memory design. In fact the exact same design can be used by tying the instruction-related control signals to the inactive state. But, since the data memory is a subset, it is also possible to save a few chips by eliminating the instruction-related control signals and rearranging the distribution of logic terms between PAL devices.

With reference to the instruction memory design defined in this chapter, the following changes may be made to convert it to a data memory:

- All instruction related inputs can be removed and all the affected equations simplified.
- U17, the instruction-state machine PAL device, can therefore be removed entirely.
- The START signal can be moved to U16; therefore U4 can be eliminated.
- The 74F175 from the instruction-memory can also be used to supply the delayed control signals to the data memory, thus eliminating the need for U3.
- The ALE function from U8 and U11 can be moved to U1. Therefore, U8 and U11 could be replaced by a single 10-bit latch such as the 29841A.
- The instruction-bus output buffers can be eliminated.

In total, the design can be reduced by 12 chips. The details of the logic equation simplifications will be left as an exercise for the reader. All other aspects of the design are the same as for the instruction memory described in the previous section.



SINGLE-BANK SCDRAM

A very low-cost memory system can be built using the Am29000 processor with a single bank of non-interleaved static column dynamic RAM (SCDRAM). This low-cost design approach reduces the component count and power consumption to a minimum, while maintaining the high performance of single-cycle burst access to memory.

The static column capability of SCDRAM means once a row is addressed for the first time, all subsequent accesses within that row can be made by simply changing the column address. In effect, the SCDRAM has a built-in cache with one row of words. The time required to do a complete cache re-load is the initial row access time.

The memory system described in this chapter meets the following design goals:

- Minimum component count
- Power consumption of no more than 6 W
- Processor clock speed in the range of 10 MHz
- Burst-mode access support for fast data movement (DMA function)

SYSTEM BLOCK DIAGRAM


A block diagram of the complete system is shown in Figure 8-1. The memory system uses buffers between the instruction and data buses of the Am29000 processor, provided by the Am29C983 Bus Interchange Buffers, with each device providing buffering for 16 data bits. Two address PAL devices are used: one is a counter for the column address when accessing the static column DRAM, and a second PAL device is a refresh counter.

CHIP COUNT AND POWER CONSUMPTION

The memory system requires 17 devices: eight DRAMs, two EPROMs, three PAL devices and three buffers. The power requirements of the devices are shown below.

Device	Max Icc, mA (per device)	Total, mA
1 Am29000 processor	250 @ 10 MHz	250
2 Am29C983	20	40
1 PALCE29M16	120	120
2 AmPALCE22V10	90	180
1 Am29C823	30	30
8 DRAM	50	400
2 27C1024	50	100
Total power consumption:		1120 mA

Figure 8-1 System Block Diagram

 

10623C-065

The worst-case current consumption is 1.12 A, giving a worst-case power consumption of $5.0 \text{ V} \cdot 1.12 \text{ A} = 5.6 \text{ W}$.

TYPES OF MEMORY ACCESS

In the system described above, there are seven specific types of memory access the processor can perform:

1. Instruction fetch from EPROM
2. Instruction fetch (simple) from DRAM
3. Instruction fetch (burst) from DRAM
4. Data load (simple) from DRAM
5. Data load (burst) from DRAM
6. Data store (simple) to DRAM
7. Data store (burst) to DRAM

Because the aim of the design was to produce a simple solution at a minimum cost, a simple state machine approach was chosen to perform the above functions. The following descriptions and timing diagrams explain the state sequences for each type of memory access.


Instruction Fetch from EPROM

In the first cycle, the processor puts out a valid address and Instruction Request ($\overline{\text{IREQ}}$). As this accesses the ROM address space of the processor, the IREQT signal (Instruction Request Type) is also valid. This latter signal is used to provide the chip select and output enable strobe to the EPROM devices. Although the processor may attempt to perform a burst-type access to the EPROMs, this is not supported by the EPROM subsystem, and thus the Instruction Burst Acknowledge ($\overline{\text{IBACK}}$) signal is inactive throughout the duration of the access. To lengthen the access, the state machine asserts the Ready ($\overline{\text{IRDY}}$) signal after two states, thus allowing EPROMs with access times of 250 ns to be used. See Figure 8-2.

Instruction Fetch (Simple) from DRAM

In the first cycle, the processor puts out a valid address and Instruction Request ($\overline{\text{IREQ}}$). The high-order element of this address is buffered and then fed into the DRAM array to form the ROW address. On the falling edge of the clock (in the first cycle), the state machine asserts the RAS strobe into the DRAMs, thus latching the address. On the next rising edge of the clock, the output MUX1 changes state. This is connected to the enable of the buffer, thus removing the ROW address from the DRAMs. On the next

Figure 8-2 EPROM Instruction Access

 


10623C-066

falling edge of the clock, the MUX2 signal becomes active, thus enabling the output of the column address counter. The half-clock delay between the MUX1 signal going inactive and the MUX2 signal going active removes any possibility of contention on the address bus. On the rising edge of the third clock cycle, CAS strobe goes active, thus latching the column address into the DRAM array. The IRDY signal is then de-asserted, allowing the access to complete in the next clock cycle. In the following clock cycle, accesses to the DRAMs are inhibited to allow to the RAS precharge time. See Figure 8-3.

Instruction Fetch (Burst) from DRAM


Instruction burst accesses are similar to the simple accesses except the processor asserts the Instruction Burst Request Signal ($\overline{\text{IBREQ}}$). The initial access is identical to the simple access, but then subsequent accesses are performed at a rate of one per cycle, with the column address counter incremented on each clock edge. The burst can be terminated by one of two means: either the processor terminates the burst by removing $\overline{\text{IBREQ}}$, or the memory system can terminate the burst by de-asserting $\overline{\text{IBACK}}$ and $\overline{\text{IRDY}}$. This latter case could arise when the memory system is needed for data accesses. See Figure 8-4.

Figure 8-3 Simple Instruction Access to DRAM

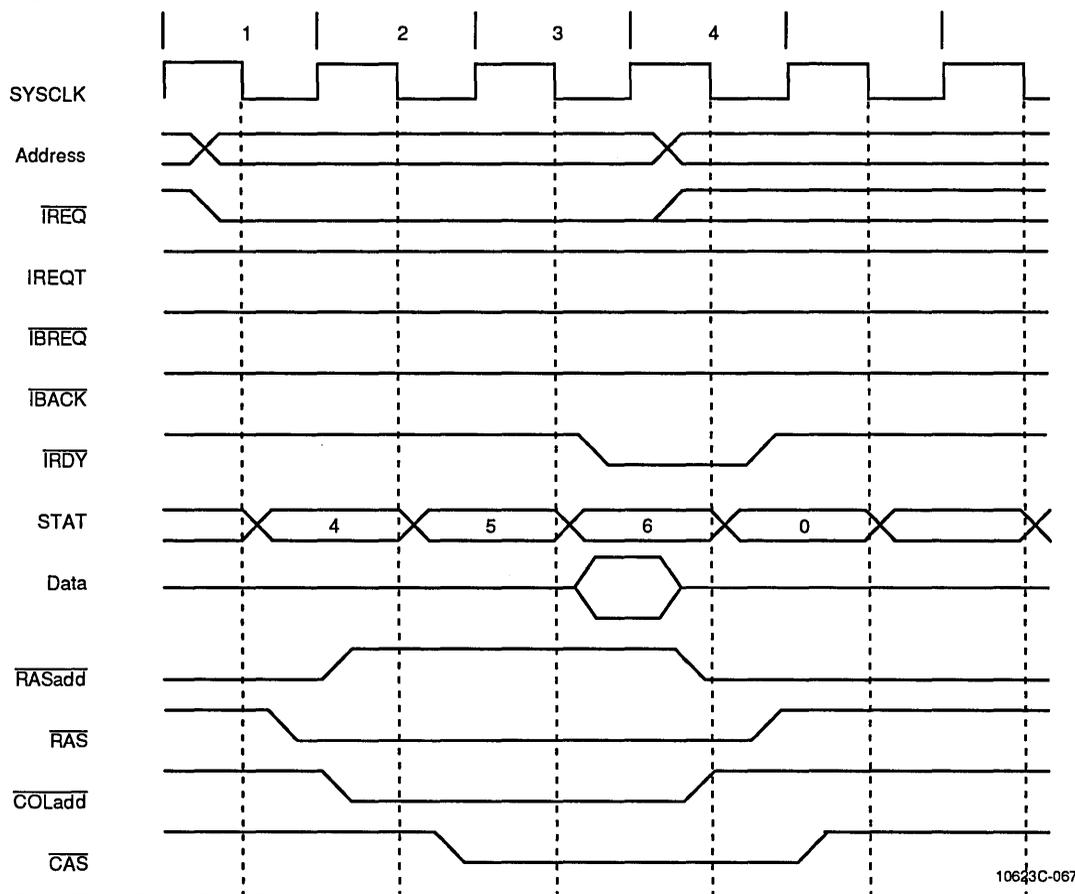

10623C-067

Figure 8-4 BURST Instruction Access to DRAM

 

Data Load Accesses from DRAM

The basic difference between data load accesses and instruction accesses is a delay imposed by the buffers connecting the data pins of the processor to the memory system.


Data Store Accesses to DRAM

When performing a store operation to the DRAM memory, a data write strobe must be generated to latch the data into the DRAM. Diagrams for both simple and burst data store accesses are shown in Figures 8-5 and 8-6.

Bus Preemption

One other requirement that must be observed is the preemption of an instruction burst due to a data access, as simultaneous instruction and data accesses are invalid with this memory model. Figure 8-7 shows the instruction accesses being preempted due to a data access. When the data access is completed, the Am29000 processor will restart the preempted instruction accesses by re-asserting the access as either a new simple or burst type access.

Figure 8-5 Simple Data Access to DRAM

 

10623C-069

Data Access Following Instruction Access

For the sake of completeness, Figure 8-8 shows a data access following an instruction access.


CONTROL PAL DEVICE DESCRIPTION

The main controlling PAL device is a PAL29M16. This device was chosen because it allows all the I/O pins to be utilized, while still allowing internal buried state registers for state information.

The state machine monitors the four request signals from the processor ($\overline{\text{IREQ}}$, $\overline{\text{DREQ}}$, $\overline{\text{IBREQ}}$, $\overline{\text{DBREQ}}$) to determine which type of access is being performed: ROM, instruction, data, or refresh.

When a ROM access is started (ROM input active), the state machine inhibits burst accesses by not asserting the Burst Acknowledge signal and counts a number of states until the $\overline{\text{IRDY}}$ signal goes active, thus terminating the access.

Figure 8-6 Burst Data Access to DRAM

 


An instruction access is similar to a ROM access, as the processor initially performs a simple read access. It is enhanced, however, by the assertion of the $\overline{\text{RAS}}$, $\overline{\text{CAS}}$, and the MUX signal. However, at possible completion of the simple access, if the processor requested an instruction burst sequence, then the Burst Acknowledge is asserted and the processor continues to receive instructions from the memory at the rate of one per clock cycle. This access can be terminated by one of two mechanisms: either the processor $\overline{\text{IBREQ}}$ signal goes inactive, indicating that the processor no longer needs to perform the burst access, or the processor asserts the $\overline{\text{DREQ}}$ signal, indicating either a LOAD or a STORE is being executed. As the memory system can only support either instruction or data accesses, but not both simultaneously, the state machine must preempt the instruction burst access and allow the data access to complete.

A data access is similar to an instruction access; however, the DRAM WR strobe must be toggled during write cycles.

When the internal processor counter reaches a pre-determined refresh value, the interrupt routine serving this condition must generate a read from a refresh address. This has the action of setting the state machine into the refresh mode, where a $\overline{\text{RAS}}$ -only refresh is performed, with the address generated by the refresh address counter.

Figure 8-7 Instruction Burst Pre-empted by a Data Access

 


10623C-071

CONCLUSION

This single-bank, static column DRAM memory system demonstrates one method of building a low-cost system with reasonably high performance. Tying the instruction and data buses together allows the memory system to be implemented with just eight DRAMs, combined with a few PAL devices, buffers, and EPROMs. The final result is low power consumption, low board space, and very reasonable cost.

Figure 8-8 Simple Instruction Access Followed by Data Access

 

10623C-072



INTERLEAVED VDRAM

VIDEO DRAM ADVANTAGES

Video Dynamic RAM (VDRAM) offers an excellent way to reduce the complexity and component count of the memory system. A VDRAM has a dual-ported internal memory array. The first port allows read and write random access to the memory array just as a standard DRAM does. The second port is a serial shift register which is loaded from (and in some cases may be written to) one row of the memory array in a single access cycle. Once the serial shift register is loaded, it may be shifted independently of the random-access port. In effect, a VDRAM provides independent and concurrent access to a common memory array via these two ports. A single address bus provides access to either port.

This memory architecture greatly simplifies the interface to the Am29000 processor. The shifter port can be connected to the instruction bus to provide sequential instruction streams. The random-access port can be connected to the data bus to provide read and write random access to data structures. Both ports are addressed via the Am29000 processor address bus.

This conveniently places both the instruction and data space in a common memory, thus significantly reducing the complexity of control logic and eliminating the need for many data buffers. Shared instruction and data space in a common memory also results in more efficient use of total memory space. This often results in a significant reduction in required memory size, and therefore a reduced component count. Due to its ability to concurrently access instructions and data, the VDRAM memory still provides performance near that of the SCDRAM design from Chapter 6.

The drawbacks to VDRAM are: a slower initial access time, lower density of currently available memories, and higher per-memory cost, although much of the higher cost is offset by the lower cost of control and buffer logic in the system. Some second generation 1-Mbit VDRAMs remove the density limitation as compared with first generation 1-Mbit DRAMs, although the initial cost is higher compared to the same density DRAMs.

Currently available VDRAMs are also unable to provide serial shifter ports fast enough to support a 40-ns instruction access time. To provide single-cycle burst instruction access speed, the current VDRAMs must be dual-bank interleaved. Again, future VDRAM may have the speed needed to eliminate dual-banking requirements. Where lower cost and simplicity is more important than a 20% clock-rate reduction, the system clock can be slowed to 20 MHz so a single bank of VDRAM can keep up with the demands of the instruction bus.

The Am29000 processor provides unique features allowing the use of slower memories, such as the VDRAM, without the severe performance reductions plaguing other high-performance microprocessors when using similar memory systems. As a result, VDRAM memories can significantly reduce system complexity and provide a fairly dense system memory, while also improving system performance-to-price ratio. The cost of the memory system drops while performance is reduced only slightly.

MEMORY FEATURES


The memory design described in this chapter has a single block of memory for instruction and data as shown in Figure 9-1. Within the memory block, there are two banks of memory, interleaved as odd and even words. For a general description of interleaved memory architecture, see Chapters 2 and 3.

Each bank is 64K words deep, with each word 32 bits wide. The total for the whole memory block is then 128K words (512K bytes). It is possible to use 120 ns access-time VDRAMs for both memory banks.

A non-sequential instruction access requires one cycle for address decode plus five additional cycles for the first word accessed. The burst access timing is similar to that used in previous chapters; each burst access is two cycles long. Overlapping the memory bank access time allows this longer access time to be hidden from the system viewpoint, except on the first word of a non-sequential instruction access. The end result is a memory providing six-cycle access time for the first word of a non-sequential instruction access and single-cycle access for subsequent words in a burst transfer. A data read access requires one cycle for address decode plus four additional cycles to complete the access.

A data write access requires one cycle for address decode plus two or three cycles (depending on the memory used) to take data from the bus. The write operation

Figure 9-1 Am29000 Processor with Interleaved VDRAM Memory

 

10623C-073

continues internal to the memory for one or two additional cycles, but the data bus is released after data is taken from the bus.


No burst accesses are supported for data. So all data read accesses are five cycles long and all write accesses are three or four cycles long, that is assuming the memory has internally completed a write operation and/or RAS precharge before the next access begins. If write completion time or RAS precharge time has not been satisfied, a subsequent data access can require up to eight cycles to complete. This is based on the worst case, a data read immediately following a data write operation.

The VDRAM random-access read/write port is connected to the Am29000 processor data bus. The serial-access shifter port is connected to the Am29000 processor instruction bus.

INTERFACE LOGIC BLOCK DIAGRAM

A block diagram of the interleaved VDRAM memory is shown in Figure 9-2. The various circuit blocks are described below.

Figure 9-2 Interleaved VDRAM Memory Block Diagram

 

10623D-074

The Memory

The memories are 64K x 4 bit VDRAMs supplied by either Fujitsu (MB81461-12) or NEC (PD41264-12). These memories have common data-in and data-out lines. Their access speed is 120 ns. Eight devices are required in each bank to form the 32-bit wide instruction word for the Am29000 processor. These are shown as devices U14 through U29.

VDRAM is used in this design to illustrate the savings in complexity, component count, and cost that the VDRAM architecture can provide. These savings come largely from the fact that the instruction and data words can reside in a common memory array still allowing concurrent dual-port access. Using one memory array instead of split instruction and data memories eliminates one entire set of memory control logic and data buffers. Also, the number of remaining control-logic and data-buffer circuits is reduced, since external buffers are no longer needed to support both data and instruction ports into the instruction memory.

Further, the VDRAM structure allows the boundary between instruction and data space to be flexible and dynamic, thereby providing for more efficient use of memory than a system that splits memory. This, in turn, may lead to reduced memory requirements in general.

Data Bus Connection

The memory random access data I/O ports of the two banks are directly connected to the Am29000 processor data bus lines. The $\overline{\text{CAS}}$ signals $\overline{\text{CAS0}}$ and $\overline{\text{CAS1}}$ control the three-state outputs of the appropriate banks, so no bus contention can occur.

If a system needs higher driving current, then buffers have to be added between the data outputs of the memory and the Am29000 processor data bus. This addition would result in another eight buffers for two banks.

Instruction Bus Multiplexers

In this design, the multiplexing and isolating of the DRAM outputs from the Instruction Bus is done with eight F157 multiplexers, but could also be done with eight buffers (like the F245). The only reason for choosing the multiplexer solution is that it solves an implementation problem for the PAL device U9.

The memory serial-data outputs are connected to the instruction bus lines via the above-mentioned multiplexers. These multiplexers serve to isolate the data outputs of the memory block from outputs of other memory blocks that may also drive the instruction bus. Also, the multiplexers serve to isolate the even and odd banks from each other, so simultaneous data accesses can occur in each bank independently. These multiplexers are shown as devices U30 through U37 in Figure 9-2.

Address Multiplexers

The upper and lower eight bits of memory address must be multiplexed into the address inputs of the memories. Discrete multiplexers are used to perform this function. These devices are shown as U5 through U8.

Note that in this design, the address is taken directly from the bus and through the multiplexers to the memories. No latching or registering of the address is done. This approach reduces the component count and complexity of the design, illustrating a lower-cost memory design. Doing this requires that the memory control logic force the

Am29000 processor to hold the address stable on the bus until after the $\overline{\text{RAS}}$ and Column Address Strobes $\overline{\text{CAS}}$ have gone active. This is done by delaying the assertion of $\overline{\text{IBACK}}$ or $\overline{\text{PEN}}$ during instruction or data accesses, respectively.

This approach reduces system performance somewhat, at least when compared with a split instruction and data memory system, or a system with multiple blocks of VDRAM in which one block could be addressed for an instruction fetch while another block is addressed for a data access. This is because the processor must, at times, hold an address on the bus when it might otherwise have been able to begin another access on an alternate memory block, assuming a memory that latches the address.

But in a system having a single block of VDRAM, there is no benefit to latching the address from the bus. This is because the memory cannot be ready to begin another access until the access in progress is completed, and the memory has completed the precharge cycles that must occur between all non-sequential accesses.

A word of warning: Do not use inverting buffers or multiplexers on VDRAM address lines. Inverted random access I/O (DQ) port addressing would conflict with the sequentially incremented addressing required by the design of the serial port.

Bank Selector

Since a VDRAM uses a shift mechanism to provide the serial output of instruction code, there is no need for an address counter. The initial address for an instruction burst request determines the starting location in the memory row to be shifted out. All subsequent instruction words are read by providing a shift clock to the VDRAM. Also, because the VDRAM shifter row is 256 words, the Am29000 processor always provides a new address at the right time when a row boundary is crossed. In addition, no address counter is required for data accesses, since no burst data accesses are supported in this memory design.

This design does, however, use bank interleaving to overcome the access delay of the VDRAM serial shifter port, so there must be a way to keep track of which bank should be output-enabled onto the instruction bus during any given cycle. Also, a way is needed to control the shift clock to each bank so the instruction accesses are overlapped properly.

This tracking function is provided by registering address line A02 at the beginning of an access and then toggling the registered bit for each completed instruction access. This registered output is called Q02E.

Registered Control Signals

As noted earlier, the timing of the $\overline{\text{BREQ}}$ control signal requires it be registered by a low-setup-time register; a F175 register is used (U4, shown in Figure 9-2).

Interface Control Logic

This logic must generate the memory response signals, manage the loading of memory addresses, generate $\overline{\text{RAS}}$ and $\overline{\text{CAS}}$ signals, control the data buffer output enables, and perform memory refresh. The logic functions needed for this require eight PAL devices: two PALCE16V8-D, one AmPAL22V10-25, one PAL20L8-B, one PAL16R4-D, one PAL20L8-D, one PAL20R8-D, and one PAL20R4-D.

Referring to Figure 9-2, device U1, a PAL16V8-B, serves to increment the memory address for the even bank when the initial address of an instruction access is odd. This causes the even bank to access the next even-bank word following the initial odd word.

Device U2, a PAL20L8-B, performs address decode for instruction and data accesses. Its outputs indicate when this memory block has been addressed and an access is to begin.

Device U3, an AmPAL22V10-25, acts as a refresh-interval counter and refresh-request logic.

Devices U9 through U13, one PAL16R4-D, one PAL20L8-D, one PAL20R8-D, one PAL20R4-D, and one PALCE16V8-D, form a state machine controlling the $\overline{\text{RAS}}$, $\overline{\text{CAS}}$, shift clock, transfer cycle enable, bank selector, write enables, and memory-response signals.

Response Signal Gating

The memory-response signals from all system bus devices are logically ORed together by a PAL device before being returned to the Am29000 processor. The gates in this PAL device are not included in the component count of this memory design since they are shared by all the bus devices in the system, and as such, are part of the overhead needed in any Am29000 processor system.

Byte Write Capability

The interface logic supports the byte-write capability of the Am29000 processor. It uses the signals OPT1, OPT0, A1, and A0 to generate the write enable signals $\overline{\text{WE0}}$ - $\overline{\text{WE3}}$. This design supports only big-endian byte ordering.

MEMORY INTERFACE LOGIC EQUATIONS

State Machine

The control logic for this memory can be thought of as a Mealy-type state machine in which the outputs are a function of the inputs and the present state of the machine. This structure is required because some of the output signals must be based on inputs which are not valid until the same cycle in which the outputs are required to take control of the memory. As shown in Figure 9-3, this state machine can be described as having 18 states. (Note: A timing diagram is provided at the end of this chapter.)

It is important to note that in this design, the instruction burst is never preempted by the slave. This is because VDRAMs are used; no contention between instruction bursts and data accesses can occur. Also, the length of the shifters is a minimum of 256 words. After 256 words, the Am29000 processor automatically preempts the burst by itself so it does not have to be preempted by the slave.


Therefore, in this design, no logic is needed to preempt an instruction burst.

IDLE is the default state of the interface state machine. It is characterized by the lack of any instruction access, data access, or refresh activity in progress. This state serves as a way of identifying when the memory is not being accessed and could be placed into a low-power mode. This state also serves as a precharge cycle for the memory when a transition is made between instruction, data, and refresh sequences.

A transition to either the IRAS or DRAS state occurs when an address selecting this memory block is placed on the address bus. These transitions are inhibited if the $\overline{\text{BINV}}$ signal is active. A transition to the RQ1 state occurs when a refresh request is active. Refresh takes priority over any pending instruction or data-access request.

There are five "Virtual States" shown in Figure 9-3: IQ1 through IQ4 and IACCESS. These states are needed because the serial data (SD) port of the VDRAM operates independently of the random access I/O (DQ) port after a row transfer cycle is completed. The states help illustrate what might be called the "split personality" of the state machine. Once a transfer cycle begins, there are in effect two active states in

Figure 9-3 VDRAM Memory State Diagram

 

10623C-075

this state machine. One state tracks the activity of the serial port control signals, and the other tracks the activity of signals associated with the random access I/O port.

The active states can be thought of as two tokens, labeled SD and DQ, being moved around a game board. The DQ token is never allowed to follow the dotted line to the virtual states. The SD token is always in one of the virtual states or the IDLE state; it never enters any of the other states. When the SD token enters the IDLE state, it cannot leave until the DQ token is also in IDLE and the ISTART condition is true.

When both tokens are in IDLE and ISTART is true, the SD token moves to the IQ1 state and the DQ token moves to the IRAS state. This would represent the beginning of a row transfer to the serial-shift port. The DQ token then tracks the progress of $\overline{\text{RAS}}$, $\overline{\text{CAS}}$, and address signals applied to the VDRAM. When the transfer sequence is finished, the DQ token goes through the precharge states and returns to IDLE. The SD token proceeds through the IQ states, counting off the delay needed until the first instruction is ready at the output of the SD port. In the IQ2 state, $\overline{\text{IBACK}}$ is made active to release the address bus. In IQ3 and IQ4, the shift clock and bank select signals begin operation to allow the access of the first instruction word. In IACCESS, $\overline{\text{IRDY}}$ is allowed to go active. During subsequent cycles of an instruction burst access, the active state remains IACCESS.

While the active state for instruction accessing is IACCESS, the DQ token is free to move through data-access states or refresh states completely independent of the instruction access in progress. When an instruction burst ends, the SD token returns to IDLE and must wait until the DQ token completes an access or refresh sequence followed by precharge before a new transfer cycle may begin.

The IRAS state occurs during the first cycle of a row transfer to the SD port following a new instruction address being presented on the address bus. During this state, the instruction output multiplexer is enabled, Ready response lines are held inactive, and the $\overline{\text{RAS}}$ lines go active. $\overline{\text{RAS}}$ is used as the input to a delay line whose output will switch the address mux to the column address after the row address hold time is satisfied. The transition to the ICAS state is unconditional.

During the ICAS state, $\overline{\text{CAS}}$ goes active to start the transfer cycle. Since the $\overline{\text{RAS}}$ minimum pulse width is 120 ns, and the minimum $\overline{\text{CAS}}$ pulse width is 60 ns, a WAIT state follows the ICAS state before the unconditional transition to the first precharge state.

During the precharge states, $\overline{\text{RAS}}$ goes inactive. The precharge period for the memory used is 100 ns, so a second and third precharge cycle is done during the PC2 and IDLE states, which unconditionally follow the PC1 cycle.

During a DQ port read sequence, the DRAS state generates $\overline{\text{RAS}}$ and the address-mux select signals. The DCAS state makes $\overline{\text{CAS}}$ active. Since the access time from $\overline{\text{CAS}}$ is 60 ns, the total of $\overline{\text{CAS}}$ -clock-to-output delay, plus access time, plus data-buffer delays, plus processor set-up time, is in excess of 95 ns, which will require a WAIT cycle, followed finally by the DACCESS cycle. During DACCESS, the $\overline{\text{DRDY}}$ signal is made active.

The DQ port write access is different only in that the $\overline{\text{DRDY}}$ signal may be made active during DCAS, since the data from the bus is written into the memory by the falling edge of the $\overline{\text{CAS}}$ signal. Doing this allows the processor to begin a new address cycle on the address bus during the WAIT cycle. This may help improve system performance if the new address is directed at a different memory block immediately beginning a new access. The WAIT cycle is used to fulfill the minimum $\overline{\text{CAS}}$ active time requirement. The DACCESS simplifies the design by allowing the logic controlling the state transitions to be the same for both read and write operations.

Finally, there is the refresh sequence. Once the IDLE state is reached and a refresh is pending, the refresh sequence starts as the highest priority task of the memory. In fact, during the IDLE cycle, $\overline{\text{CAS}}$ will go active to set up a $\overline{\text{CAS}}$ -before- $\overline{\text{RAS}}$ refresh cycle. This type of refresh cycle makes use of the VDRAM internal refresh counters to supply the refresh address. During RQ1, $\overline{\text{RAS}}$ is made active as in IRAS and DRAS cycles. The RQ2 and RQ3 cycles are used to supply two additional wait states to make up the three cycles needed to satisfy the minimum $\overline{\text{RAS}}$ active time of 120 ns.

Logic Details—Signal By Signal

The logic equations for the memory interface signals are described below. The signals as implemented in the final PAL device outputs are often active Low, as required by the actual circuit design. The signals are described in active High terms so the design is a little easier to follow. The PAL device definition files are shown in Figures 9-4 through 9-11; following the figures are descriptions of how the equations were derived.

NOTE: All PAL device equations use the following conventions:

- Where a PAL device equation uses a colon followed by an equals sign ($:=$), the equation signals are registered PAL device outputs.
- Where a PAL device equation uses only an equals sign ($=$), the equation signals are combinatorial PAL device outputs.
- The Device Pin list is shown near the top of each figure as two lines of signal names. The names occur in pin order, numbered from left to right 1 through 20. The polarity of each name indicates the actual input or output signal polarity. Signals within the equations are shown as active High (e.g., where signal names in the pin list are $\overline{\text{A}}$ B $\overline{\text{C}}$, the equation is $\text{C} = \text{A} \cdot \overline{\text{B}}$; when the inputs are $\overline{\text{A}} = \text{Low}$, $\text{B} = \text{High}$, then the $\overline{\text{C}}$ output will be Low).

Figure 9-4 AmPAL22V10-25 VRAM Refresh Counter/Request Generator Device U3

CLK $\overline{\text{RFAK}}$ $\overline{\text{RQ1}}$ $\overline{\text{RQ2}}$ $\overline{\text{RQ3}}$ NC6 NC7 NC8 NC9 NC10 NC11 GND
 NC13 RFRQ0 $\overline{\text{RFQ2}}$ $\overline{\text{RFQ3}}$ $\overline{\text{RFQ4}}$ $\overline{\text{RFQ5}}$ $\overline{\text{RFQ6}}$ $\overline{\text{RFQ7}}$ $\overline{\text{RFQ8}}$ $\overline{\text{RFQ9}}$ $\overline{\text{RFQ10}}$ $\overline{\text{RFQ9}}$ VCC

$$\text{RFQ2} := \overline{\text{RFQ2}}$$

$$\text{RFQ3} := \overline{\text{RFQ2}} \cdot \overline{\text{RFQ3}} + \overline{\text{RFQ2}} \cdot \text{RFQ3}$$

$$\text{RFQ4} := \overline{\text{RFQ2}} \cdot \overline{\text{RFQ3}} \cdot \overline{\text{RFQ4}} + \overline{\text{RFQ2}} \cdot \text{RFQ4} + \overline{\text{RFQ3}} \cdot \text{RFQ4}$$

$$\text{RFQ5} := \overline{\text{RFQ2}} \cdot \overline{\text{RFQ3}} \cdot \overline{\text{RFQ4}} \cdot \overline{\text{RFQ5}} + \overline{\text{RFQ2}} \cdot \text{RFQ5} + \overline{\text{RFQ3}} \cdot \text{RFQ5} + \overline{\text{RFQ4}} \cdot \text{RFQ5}$$

$$\text{RFQ6} := \overline{\text{RFQ2}} \cdot \overline{\text{RFQ3}} \cdot \overline{\text{RFQ4}} \cdot \overline{\text{RFQ5}} \cdot \overline{\text{RFQ6}} + \overline{\text{RFQ2}} \cdot \text{RFQ6} + \overline{\text{RFQ3}} \cdot \text{RFQ6} + \overline{\text{RFQ4}} \cdot \text{RFQ6} + \overline{\text{RFQ5}} \cdot \text{RFQ6}$$

Figure 9-4 AmPAL22V10-25 VRAM Refresh Counter/Request Generator Device U3 (continued)

$$\begin{aligned}
 \text{RFQ7} &:= \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \overline{\text{RFQ7}} \\
 &+ \overline{\text{RFQ2}} \cdot \text{RFQ7} \\
 &+ \text{RFQ3} \cdot \text{RFQ7} \\
 &+ \overline{\text{RFQ4}} \cdot \text{RFQ7} \\
 &+ \overline{\text{RFQ5}} \cdot \text{RFQ7} \\
 &+ \text{RFQ6} \cdot \text{RFQ7} \\
 \\
 \text{RFQ8} &:= \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \overline{\text{RFQ8}} \\
 &+ \overline{\text{RFQ2}} \cdot \text{RFQ8} \\
 &+ \text{RFQ3} \cdot \text{RFQ8} \\
 &+ \overline{\text{RFQ4}} \cdot \text{RFQ8} \\
 &+ \overline{\text{RFQ5}} \cdot \text{RFQ8} \\
 &+ \text{RFQ6} \cdot \text{RFQ8} \\
 &+ \overline{\text{RFQ7}} \cdot \text{RFQ8} \\
 \\
 \text{RFQ9} &:= \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \text{RFQ8} \cdot \overline{\text{RFQ9}} \\
 &+ \overline{\text{RFQ2}} \cdot \text{RFQ9} \\
 &+ \overline{\text{RFQ3}} \cdot \text{RFQ9} \\
 &+ \overline{\text{RFQ4}} \cdot \text{RFQ9} \\
 &+ \overline{\text{RFQ5}} \cdot \text{RFQ9} \\
 &+ \overline{\text{RFQ6}} \cdot \text{RFQ9} \\
 &+ \overline{\text{RFQ7}} \cdot \text{RFQ9} \\
 &+ \overline{\text{RFQ8}} \cdot \text{RFQ9} \\
 \\
 \text{RFQ10} &:= \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \text{RFQ8} \cdot \text{RFQ9} \cdot \overline{\text{RFQ10}} \\
 &+ \overline{\text{RFQ2}} \cdot \text{RFQ10} \\
 &+ \overline{\text{RFQ3}} \cdot \text{RFQ10} \\
 &+ \overline{\text{RFQ4}} \cdot \text{RFQ10} \\
 &+ \overline{\text{RFQ5}} \cdot \text{RFQ10} \\
 &+ \overline{\text{RFQ6}} \cdot \text{RFQ10} \\
 &+ \overline{\text{RFQ7}} \cdot \text{RFQ10} \\
 &+ \overline{\text{RFQ8}} \cdot \text{RFQ10} \\
 &+ \overline{\text{RFQ9}} \cdot \text{RFQ10} \\
 \\
 \text{SYNCHRONOUS PRESET} &= \text{RFQ2} \cdot \overline{\text{RFQ3}} \cdot \text{RFQ4} \cdot \overline{\text{RFQ5}} \cdot \overline{\text{RFQ6}} \cdot \overline{\text{RFQ7}} \cdot \overline{\text{RFQ8}} \\
 &\quad \cdot \text{RFQ9} \cdot \text{RFQ10} \\
 \\
 \text{RFRQ0} &:= \text{RFRQ0} \cdot (\overline{\text{RFACK}} \cdot \text{RQ1})
 \end{aligned}$$

Figure 9-5 PAL20L8-B VRAM State Decoder—Interleaved Device U2

$\overline{\text{IREQ}}$ DREQT0 IREQT A31 A30 A29 A28 A27 A26 A25 A24 GND
 DREQ DREQT1 ISTART RFRQ0 RFACK LD IQ1 DQ1 PC1 DSTART PIN169 VCC

$$\text{ISTART} = \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFRQ0}} \cdot \text{IME}$$

$$\text{DSTART} = \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFRQ0}} \cdot \text{DME}$$

NOTE: In the above equations, IME and DME are used only for clarity. The actual input terms should be substituted when compiling this device.

$$\begin{aligned}
 \text{IME} &= \text{IREQ} \cdot \overline{\text{IREQT}} \cdot \overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{A26}} \cdot \overline{\text{A25}} \cdot \overline{\text{A24}} \\
 &\quad \cdot \text{PIN169}
 \end{aligned}$$

$$\begin{aligned}
 \text{DME} &= \text{DREQ} \cdot \overline{\text{DREQT0}} \cdot \overline{\text{DREQT1}} \cdot \overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{A26}} \cdot \overline{\text{A25}} \\
 &\quad \cdot \text{A24} \cdot \text{PIN169}
 \end{aligned}$$

$$\text{LD} = \text{IREQ} \cdot \overline{\text{IQ1}}$$

Figure 9-6 PALCE16V8-D VRAM Instruction State Generator—Interleaved Device U9

CLK $\overline{\text{IREQ}}$ $\overline{\text{ISTART}}$ AX2 $\overline{\text{LD}}$ NC6 $\overline{\text{IBREQ.D}}$ $\overline{\text{BINV}}$ NC9 GND
 OE $\overline{\text{IOE}}$ CNT $\overline{\text{IQ1}}$ $\overline{\text{IQ2}}$ $\overline{\text{IQ3}}$ $\overline{\text{IQ4}}$ $\overline{\text{IRDY}}$ $\overline{\text{Q02E}}$ VCC

$$\text{IQ1} := \overline{\text{BINV}} \cdot \overline{\text{IQ1}} \cdot \text{ISTART} \\ + \text{IQ1} \cdot (\overline{\text{IQ3}} \cdot \text{IQ4})$$

$$\text{IQ2} := \text{IQ1} \cdot (\overline{\text{IQ3}} \cdot \text{IQ4})$$

$$\text{IQ3} := \text{IQ2} \cdot \overline{\text{IQ4}}$$

$$\text{IQ4} := \text{IQ3} \\ + \overline{\text{IQ4}} \cdot \text{IBREQ.D}$$

$$\text{Q02E} := \overline{\text{LD}} \cdot \text{AX2} \\ + \overline{\text{LD}} \cdot \text{CNT} \cdot \overline{\text{IQ3}} \cdot \overline{\text{IQ4}} \cdot \text{Q02E} \\ + \overline{\text{LD}} \cdot \text{IQ3} \cdot \overline{\text{Q02E}} \\ + \overline{\text{LD}} \cdot \text{IQ4} \cdot \overline{\text{Q02E}} \\ + \overline{\text{LD}} \cdot \text{CNT} \cdot \overline{\text{Q02E}}$$

$$\text{IRDY} = \overline{\text{IQ3}} \cdot \text{IQ4} \\ + \overline{\text{IQ1}} \cdot \text{IBREQ.D}$$

$$\text{IOE} = \overline{\text{IQ3}} \cdot \text{IQ4} \\ + \overline{\text{IQ1}} \cdot \text{IBREQ.D}$$

10623C-078

Figure 9-7 PAL16R4-D VRAM Data State Generator—Interleaved Device U10

CLK $\overline{\text{DSTART}}$ AX2 $\overline{\text{WE0}}$ $\overline{\text{NEC}}$ NC6 NC7 $\overline{\text{BINV}}$ NC9 GND
 OE $\overline{\text{DOE0}}$ $\overline{\text{DOE1}}$ $\overline{\text{DQ1}}$ $\overline{\text{DQ2}}$ $\overline{\text{DQ3}}$ $\overline{\text{DQ4}}$ $\overline{\text{DRDY}}$ $\overline{\text{PEN}}$ VCC

$$\text{DQ1} := \overline{\text{BINV}} \cdot \overline{\text{DQ1}} \cdot \text{DSTART} \\ + \text{DQ1} \cdot \overline{\text{DQ4}}$$

$$\text{DQ2} := \text{DQ1} \cdot \overline{\text{DQ4}}$$

$$\text{DQ3} := \text{DQ2} \cdot \overline{\text{DQ4}}$$

$$\text{DQ4} := \text{DQ3} \cdot \overline{\text{DQ4}}$$

$$\text{DRDY} = \overline{\text{WE}} \cdot \text{DQ4} \\ + \text{WE} \cdot \text{DQ2} \cdot \overline{\text{DQ3}} \cdot \overline{\text{NEC}} \\ + \text{WE} \cdot \text{DQ3} \cdot \overline{\text{DQ4}} \cdot \overline{\text{NEC}}$$

$$\text{PEN} = \text{DQ2} \cdot \overline{\text{DQ3}}$$

10623C-079

Figure 9-8 PAL20L8-D VRAM Transfer Generator—Interleaved Device U13

$\overline{Q02E}$ $\overline{TEXT1}$ $\overline{TEXT2}$ $\overline{DQ1}$ $\overline{DQ2}$ \overline{IREQ} $\overline{WE1}$ \overline{NEC} \overline{RESET} \overline{RW} $\overline{NC11}$ \overline{GND}
 \overline{SYSCLK} $\overline{NC14}$ $\overline{SAS0}$ $\overline{TR0}$ \overline{WE} $\overline{IQ1}$ $\overline{IQ4}$ $\overline{NC20}$ $\overline{TR1}$ $\overline{SAS1}$ $\overline{NC23}$ \overline{VCC}

$$\begin{aligned} \overline{SAS0} &= \overline{RESET} \cdot \overline{SYSCLK} \\ &+ \overline{RESET} \cdot \overline{IQ1} \cdot \overline{IQ4} \\ &+ \overline{RESET} \cdot \overline{IQ4} \cdot \overline{Q02E} \\ &+ \overline{RESET} \cdot \overline{IQ1} \cdot \overline{Q02E} \end{aligned}$$

$$\begin{aligned} \overline{SAS1} &= \overline{RESET} \cdot \overline{SYSCLK} \\ &+ \overline{RESET} \cdot \overline{IQ1} \cdot \overline{IQ4} \\ &+ \overline{RESET} \cdot \overline{IQ4} \cdot \overline{Q02E} \\ &+ \overline{RESET} \cdot \overline{IQ1} \cdot \overline{Q02E} \end{aligned}$$

$$\begin{aligned} \overline{TR0} &= \overline{DQ1} \cdot \overline{IREQ} \\ &+ \overline{DQ1} \cdot \overline{TR0} \cdot \overline{NEC} \cdot \overline{TEXT1} \\ &+ \overline{DQ1} \cdot \overline{TR0} \cdot \overline{NEC} \cdot \overline{TEXT2} \\ &+ \overline{DQ2} \cdot \overline{WE} \end{aligned}$$

$$\begin{aligned} \overline{TR1} &= \overline{DQ1} \cdot \overline{IREQ} \\ &+ \overline{DQ1} \cdot \overline{TR1} \cdot \overline{NEC} \cdot \overline{TEXT1} \\ &+ \overline{DQ1} \cdot \overline{TR1} \cdot \overline{NEC} \cdot \overline{TEXT2} \\ &+ \overline{DQ2} \cdot \overline{WE} \end{aligned}$$

$$\begin{aligned} \overline{WE} &= \overline{IQ1} \cdot \overline{DQ1} \cdot \overline{DQ2} \cdot \overline{RW} \\ &+ \overline{IQ1} \cdot \overline{DQ1} \cdot \overline{DQ2} \cdot \overline{WE} \end{aligned}$$

10623C-080

Figure 9-9 PAL20R8-D VRAM RAS-CAS Generator—Interleaved Device U11

$\overline{\text{CLK}}$ $\overline{\text{ISTART}}$ $\overline{\text{DSTART}}$ $\overline{\text{IQ1}}$ $\overline{\text{DQ1}}$ $\overline{\text{IQ3}}$ $\overline{\text{DQ3}}$ $\overline{\text{RQ3}}$ $\overline{\text{BINV}}$ $\overline{\text{AX2}}$ $\overline{\text{RFRQ0}}$ $\overline{\text{GND}}$
 $\overline{\text{OE}}$ $\overline{\text{RFACK}}$ $\overline{\text{RAS0}}$ $\overline{\text{RAS1}}$ $\overline{\text{RAS}}$ $\overline{\text{PC1}}$ $\overline{\text{PC2}}$ $\overline{\text{CAS0}}$ $\overline{\text{CAS1}}$ $\overline{\text{NC22}}$ $\overline{\text{NC23}}$ $\overline{\text{VCC}}$

$$\begin{aligned} \overline{\text{RAS0}} &:= \overline{\text{BINV}} \cdot \overline{\text{RAS0}} \cdot \overline{\text{ISTART}} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS0}} \cdot \overline{\text{DSTART}} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS0}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFACK}} \\ &+ \overline{\text{RAS0}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{IQ3}} \\ &+ \overline{\text{RAS0}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ3}} \\ &+ \overline{\text{RAS0}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{RQ3}} \end{aligned}$$

$$\begin{aligned} \overline{\text{RAS1}} &:= \overline{\text{BINV}} \cdot \overline{\text{RAS1}} \cdot \overline{\text{ISTART}} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS1}} \cdot \overline{\text{DSTART}} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS1}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFACK}} \\ &+ \overline{\text{RAS1}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{IQ3}} \\ &+ \overline{\text{RAS1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ3}} \\ &+ \overline{\text{RAS1}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{RQ3}} \end{aligned}$$

$$\begin{aligned} \overline{\text{RAS}} &:= \overline{\text{BINV}} \cdot \overline{\text{RAS}} \cdot \overline{\text{ISTART}} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS}} \cdot \overline{\text{DSTART}} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFACK}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{IQ3}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ3}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{RQ3}} \end{aligned}$$

$$\begin{aligned} \overline{\text{PC1}} &:= \overline{\text{PC1}} \cdot \overline{\text{IQ3}} \\ &+ \overline{\text{PC1}} \cdot \overline{\text{DQ3}} \\ &+ \overline{\text{PC1}} \cdot \overline{\text{RQ3}} \\ &+ \overline{\text{PC1}} \cdot \overline{\text{PC2}} \end{aligned}$$

$$\overline{\text{PC2}} := \overline{\text{PC1}}$$

$$\begin{aligned} \overline{\text{CAS0}} &= \overline{\text{RAS}} \cdot \overline{\text{IQ1}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{AX2}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{RFRQ0}} \end{aligned}$$

$$\begin{aligned} \overline{\text{CAS1}} &= \overline{\text{RAS}} \cdot \overline{\text{IQ1}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{AX2}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{RFRQ0}} \end{aligned}$$

10623C-081

Figure 9-10 PAL20R4-D Byte Write Enable Generator—Interleaved Device U12

$\overline{\text{CLK}}$ $\overline{\text{PC1}}$ $\overline{\text{IQ1}}$ $\overline{\text{DQ1}}$ $\overline{\text{DQ2}}$ $\overline{\text{RAS}}$ $\overline{\text{RFRQ0}}$ $\overline{\text{RW}}$ OPT1 OPT0 A1 GND
 OE A0 WE0 WE1 RFACK RQ1 RQ2 RQ3 WE2 WE3 NC23 VCC

$$\begin{aligned}
 \text{WE0} &:= \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \text{A1} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \text{A1} \cdot \overline{\text{A0}} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \text{WE0}
 \end{aligned}$$

$$\begin{aligned}
 \text{WE1} &:= \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \text{A1} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \text{A1} \cdot \text{A0} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \text{WE1}
 \end{aligned}$$

$$\begin{aligned}
 \text{WE2} &:= \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \text{A1} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \text{A1} \cdot \overline{\text{A0}} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \text{WE2}
 \end{aligned}$$

$$\begin{aligned}
 \text{WE3} &:= \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \text{A1} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \text{A1} \cdot \text{A0} \\
 &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \text{WE3}
 \end{aligned}$$

$$\begin{aligned}
 \text{RFACK} &:= \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \text{RFRQ0} \\
 &+ \text{RFACK} \cdot (\overline{\text{RFRQ0}} \cdot \text{RQ3})
 \end{aligned}$$

$$\begin{aligned}
 \text{RQ1} &:= \overline{\text{RQ1}} \cdot \overline{\text{PC1}} \cdot \text{RFACK} \\
 &+ \text{RQ1} \cdot \overline{\text{RQ3}}
 \end{aligned}$$

$$\text{RQ2} := \text{RQ1} \cdot \overline{\text{RQ3}}$$

$$\text{RQ3} := \text{RQ2} \cdot \overline{\text{RQ3}}$$

10623C-082

Figure 9-11 PALCE16V8-D VRAM Address Incrementer Device U1

$\overline{DQ1}$ A02 A03 A04 A05 A06 A07 A08 A09 GND
 NC11 AX9 AX8 AX7 AX6 AX5 AX4 AX2 AX3 VCC

$$\overline{AX2} = \overline{DQ1} \cdot \overline{A02} + DQ1 \cdot \overline{AX2}$$

$$\overline{AX3} = \overline{A02} \cdot \overline{A03} + A02 \cdot A03$$

$$\overline{AX4} = \overline{A02} \cdot \overline{A04} + A02 \cdot \overline{A03} \cdot \overline{A04} + A02 \cdot A03 \cdot A04$$

$$\overline{AX5} = \overline{A02} \cdot \overline{A05} + A02 \cdot A03 \cdot A04 \cdot A05 + A02 \cdot \overline{A03} \cdot \overline{A05} + A02 \cdot A04 \cdot A05$$

$$\overline{AX6} = \overline{A02} \cdot \overline{A06} + A02 \cdot A03 \cdot A04 \cdot A05 \cdot A06 + A02 \cdot \overline{A03} \cdot \overline{A06} + A02 \cdot A04 \cdot \overline{A06} + A02 \cdot \overline{A05} \cdot \overline{A06}$$

$$\overline{AX7} = \overline{A02} \cdot \overline{A07} + A02 \cdot \overline{A03} \cdot \overline{A04} \cdot A05 \cdot A06 \cdot A07 + A02 \cdot \overline{A03} \cdot \overline{A07} + A02 \cdot \overline{A04} \cdot \overline{A07} + A02 \cdot A05 \cdot \overline{A07} + A02 \cdot A06 \cdot \overline{A07}$$

$$\overline{AX8} = \overline{A02} \cdot \overline{A08} + A02 \cdot A03 \cdot A04 \cdot A05 \cdot A06 \cdot A07 \cdot A08 + A02 \cdot \overline{A03} \cdot \overline{A08} + A02 \cdot \overline{A04} \cdot \overline{A08} + A02 \cdot A05 \cdot \overline{A08} + A02 \cdot A06 \cdot \overline{A08} + A02 \cdot A07 \cdot \overline{A08}$$

$$\overline{AX9} = \overline{A02} \cdot \overline{A09} + A02 \cdot A03 \cdot A04 \cdot A05 \cdot A06 \cdot A07 \cdot A08 \cdot A09 + A02 \cdot \overline{A03} \cdot \overline{A09} + A02 \cdot \overline{A04} \cdot \overline{A09} + A02 \cdot A05 \cdot \overline{A09} + A02 \cdot A06 \cdot \overline{A09} + A02 \cdot A07 \cdot \overline{A09} + A02 \cdot A08 \cdot \overline{A09}$$

RFQ (Refresh Request)

Dynamic memories need to be completely refreshed every 4 μs , which translates into at least one row refreshed every 15.6 μs on average. To keep track of this time, a counter is used. Once a refresh interval has passed, a latch is used to remember that a refresh is requested while the counter continues to count the next interval. Once the refresh has been performed, the latch is cleared.

The counter and refresh request latch is implemented in an AmPAL22V10-25. Nine of the outputs form the counter, which is incremented by the system clock at 25 MHz. This gives up to $512 \times 40 \text{ ns} = 20.48 \mu\text{s}$ refresh periods. The synchronous preset term for all the registers is programmed to go active on a count value of 389, which will produce a refresh interval of $390 \text{ cycles} \times 40 \text{ ns} = 15.6 \mu\text{s}$. The one remaining output is used to implement the refresh request latch. That latch function (registered output) is also set by the synchronous preset term.

The equations for the counter are shown in Figure 9-4. Below are the preset and refresh latch equations:

$$\text{SYNCHRONOUS PRESET} = \overline{\text{RFQ2}} \cdot \overline{\text{RFQ3}} \cdot \overline{\text{RFQ4}} \cdot \overline{\text{RFQ5}} \cdot \overline{\text{RFQ6}} \cdot \overline{\text{RFQ7}} \cdot \overline{\text{RFQ8}} \\ \cdot \overline{\text{RFQ9}} \cdot \overline{\text{RFQ10}}$$

$$\text{RFRQ0} := \overline{\text{RFRQ0}} \cdot (\overline{\text{RFAck}} \cdot \text{RQ1})$$

Refresh Sequence Equations

A refresh of the memory requires multiple clocks so the minimum RAS active time of 120 ns can be satisfied. To manage this, the following equations are used.

RFAck

The Refresh Acknowledge (RFAck) signal is used to begin a refresh sequence and to clear the pending refresh request. The RFAck signal goes active when the state machine (DQ token) re-enters the IDLE state controlled by $\overline{\text{IQ1}}$ and $\overline{\text{DQ1}}$. RFAck is held active until the refresh request is cleared, indicated by $\overline{\text{RFRQ0}} \cdot \text{RQ3}$.

$$\text{RFAck} := \overline{\text{DQ1}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{RFRQ0}} \\ + \text{RFAck} \cdot (\overline{\text{RFREQ0}} \cdot \text{RQ3})$$

RQ1, RQ2, RQ3

The three cycles needed for a refresh are tracked by RQ1, RQ2, and RQ3. RQ1 will not go active until the cycle following the IDLE state. This is controlled by $\overline{\text{RQ1}} \cdot \overline{\text{PC1}} \cdot \text{RFAck}$, which is only true during IDLE. RQ1 is held active for all three refresh cycles to provide a single signal to identify when a refresh is in progress. RQ2 and RQ3 simply follow RQ1 with RQ3, signaling the last cycle of the refresh sequence.

$$\text{RQ1} := \overline{\text{RQ1}} \cdot \overline{\text{PC1}} \cdot \text{RFAck} \\ + \text{RQ1} \cdot \overline{\text{RQ3}}$$

$$\text{RQ2} := \text{RQ1} \cdot \overline{\text{RQ3}}$$

$$\text{RQ3} := \text{RQ2} \cdot \overline{\text{RQ3}}$$

IME

The use of the Instruction for ME (IME) signal is based on the assumption that other blocks of instruction or data memory may be added later and there may be valid addresses in address spaces other than instruction/data space.

This means this memory will only respond with $\overline{\text{IBACK}}$ or $\overline{\text{DRDY}}$ active when this block has been selected by valid addresses in the instruction/data space. This requires at least some of the more significant address lines above the address range of this memory block be monitored to determine when this memory block is addressed. Also, it means the Instruction Request Type (IREQT), Data Request Type (DREQT 0, DREQT1), and Pin 169 lines must be monitored to determine that an address is valid and lies in the instruction/data space.

IME is the indication that the address of this memory block is present on the upper address lines, an instruction request is active, Pin 169 is inactive (test hardware has not taken control), and instruction/data address space is indicated. In other words, this memory block is receiving a valid instruction access request. This example design will assume the address of this memory block is equal to $\overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{A26}} \cdot \overline{\text{A25}} \cdot \overline{\text{A24}}$. The equation for this signal is:

$$\text{IME} = \text{IREQ} \cdot \overline{\text{IREQT}} \cdot \overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{A26}} \cdot \overline{\text{A25}} \cdot \overline{\text{A24}} \cdot \text{Pin169}$$

Note that IME is not directly implemented as a PAL device output in this design. The terms are used in the generation of the ISTART term.

DME

The Data for ME (DME) signal is the indication that the address of this memory block is present on the upper address lines, a data request is active, Pin 169 is inactive, and instruction/data address space is indicated. In other words, this memory block is receiving a valid data access request. This example design will assume the address of this memory block is equal to $\overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{A26}} \cdot \overline{\text{A25}} \cdot \overline{\text{A24}}$. Note that for this design, both the instruction and data blocks reside in the same address space. This is possible because of the common memory array of the VDRAM that is accessible to either the instruction serial port or the data I/O port.

The equation for this signal is:

$$\text{DME} = \overline{\text{DREQ}} \cdot \overline{\text{DREQT0}} \cdot \overline{\text{DREQT1}} \cdot \overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{A26}} \cdot \overline{\text{A25}} \cdot \overline{\text{A24}} \cdot \text{Pin169}$$

As with IME, this term is not directly implemented.

ISTART

The Instruction Start (ISTART) signal causes the transition from IDLE to IRAS and IQ1 states. It is valid only in the IDLE state with no refresh sequence starting, identified by not being in any other state via $\overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFRQ0}}$. So when in the IDLE state and IME is active, ISTART is active.

$$\text{ISTART} = \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFRQ0}} \cdot \text{IME}$$

DSTART

The Data Start (DSTART) signal is the same as ISTART except DME is the qualifier.

$$DSTART = \overline{IQ1} \cdot \overline{DQ1} \cdot \overline{RFA\overline{CK}} \cdot \overline{PC1} \cdot \overline{RFRQ0} \cdot DME$$

IBACK

The Instruction Burst Acknowledge (IBACK) signal is applied to the Am29000 processor and is, in effect, the indication that the interface state machine is in an active or suspended instruction access. The equation is:

$$IBACK = IQ2 + \overline{IREQ} \cdot IBACK$$

The IBACK active state is entered during the IQ2 state. IBACK is delayed until IQ2 in order to hold the instruction address active on the bus until the CAS signal has gone active, thus eliminating the need for address latches or registers.

IBACK remains active until a new instruction access begins. The IBACK signal is combinatorial so it will go inactive in the same cycle IREQ goes active. This is required to hold the address on the bus until a new row transfer sequence can begin. The address must be held because there are no address latches or registers in this design to take the address from the bus. Address latches or registers would be required if IBACK were left active throughout the IREQ cycle.

This places a timing constraint on the IBACK response signal path that is different from earlier memory designs. IREQ is a signal that will not be stable until 14 ns into a cycle. The D-speed PAL device logic implementing the IBACK logic has a propagation delay of 10 ns. The Am29000 processor has a response signal setup time of 12 ns. These delays total 36 ns, which means the logic OR gate used to combine all IBACK response signals in the system must have a worst-case propagation delay of 4 ns. That is not easy to achieve when several IBACK response lines in the system must be logically ORed.

A solution to this is to move a copy of the VDRAM-block IBACK logic down into the PAL device used to implement the IBACK response signal logical OR gate. That will eliminate one level of PAL device delay. The equation for the response OR-gate function would then become:

$$IBACK = IBACK0 \cdot IBREQ.D + IBACK1 \cdot IBREQ.D + IBACK2 \cdot IBREQ.D + IBACK3 \cdot IBREQ.D + IBACK4 \cdot IBREQ.D + IBACK5 \cdot IBREQ.D + IQ2 \cdot IBREQ.D + \overline{IREQ} \cdot IBACK$$

where the numbered IBACK inputs are the IBACK signals from other bus devices and the IQ2 + IREQ · IBACK inputs are from the VDRAM control logic.

The IBACK logic defined earlier remains to provide a version of IBACK local to the VDRAM control logic. That version of the IBACK is not as time critical because it will simply be registered. Only IBACK.D is needed by other parts of the VDRAM control logic.

IBACK.D

The IBACK Delayed (IBACK.D) signal is simply a one-cycle delayed version of IBACK. The logic for IBACK is implemented directly in the IBACK.D equation.

$$\text{IBACK.D} := \text{IQ2} \\ + \text{IREQ} \bullet \text{BACK}$$

It is used in the generation of $\overline{\text{IRDY}}$, IOE0, IOE1, and CNT.

Instruction Initial Access States

Signals IQ1, IQ2, IQ3, and IQ4 are used to control the state transitions from IQ1 to IACCESS and IRAS through WAIT during the first instruction access. The IQ1 signal goes active during the IQ1 and IRAS states, and remains active for four additional cycles. IQ1 will go active only when there is a valid ISTART.

$\overline{\text{BINV}}$ inhibits the transition to IQ1. $\overline{\text{BINV}}$ is used in this equation instead of $\overline{\text{ISTART}}$ because it only needs a 10-ns setup time for the PAL device. If it were used in the ISTART PAL device, an additional 10 ns combinatorial delay would be created, so the $\overline{\text{BINV}}$ signal could not be used correctly anymore.

The IQ2, IQ3, and IQ4 signals are used to count the five cycles during which IQ1 is active. IQ3 is inactive during the fifth cycle after IQ1 goes active. This is used as a way to identify the fifth cycle as the condition of $\overline{\text{IQ3}} \bullet \text{IQ4}$. This eliminates the need for an additional signal to directly indicate the fifth cycle.

$$\text{IQ1} := \overline{\text{BINV}} \bullet \overline{\text{IQ1}} \bullet \text{ISTART} \\ + \text{IQ1} \bullet (\overline{\text{IQ3}} \bullet \text{IQ4})$$

$$\text{IQ2} := \text{IQ1} \bullet (\overline{\text{IQ3}} \bullet \text{IQ4})$$

$$\text{IQ3} := \text{IQ2} \bullet \overline{\text{IQ4}}$$

$$\text{IQ4} := \text{IQ3}$$

Data Initial Access States

These equations are similar in function to the IQ1-IQ4 signals. They control state transitions during data accesses. DQ1 goes active during the DQ1 state as a result of a valid DSTART signal during the IDLE state. DQ2 through DQ4 simply count off the four DQ states. The reason for using $\overline{\text{BINV}}$ here is the same as for the instruction side.

$$\text{DQ1} := \overline{\text{BINV}} \bullet \overline{\text{DQ1}} \bullet \text{DSTART} \\ + \text{DQ1} \bullet \text{DQ4}$$

$$\text{DQ2} := \text{DQ1} \bullet \overline{\text{DQ4}}$$

$$\text{DQ3} := \text{DQ2} \bullet \overline{\text{DQ4}}$$

$$\text{DQ4} := \text{DQ3} \bullet \overline{\text{DQ4}}$$

Precharge States

At the end of any DQ port access, the $\overline{\text{RAS}}$ lines must be made inactive to precharge internal memory buses before another access with a different row address may begin. Three cycles are needed, indicated by the signals PC1 and PC2. The PC1 signal is

active during the PC1 state and the PC2 state. The PC2 signal is active during the PC2 state and the first IDLE state following the PC2 state. PC1 goes active following the third cycle of any instruction, data, or refresh sequence. In other words, once the minimum RAS pulse width requirement is satisfied, $\overline{\text{RAS}}$ is made inactive to begin precharging for the next access. In the case of a data read where the output data must be held valid after $\overline{\text{RAS}}$ goes inactive, the CAS signal is kept active to hold the data.

$$\begin{aligned} \text{PC1} &:= \overline{\text{PC1}} \cdot \text{IQ3} \\ &+ \overline{\text{PC1}} \cdot \text{DQ3} \\ &+ \overline{\text{PC1}} \cdot \text{RQ3} \\ &+ \text{PC1} \cdot \overline{\text{PC2}} \end{aligned}$$

$$\text{PC2} := \text{PC1}$$

LD

The Load (LD) signal enables address bit A02 to be loaded into the bank selection register (Q02E) on the next rising edge of SYSCLK. The equation is:

$$\text{LD} = \text{IREQ} \cdot \overline{\text{IQ1}}$$

In this design, bank selection is only meaningful for an instruction access because no burst data accesses are supported. LD is thus active as a result of $\overline{\text{IREQ}}$ except during the access time of the first instruction word. This limitation turns off LD after an instruction access begins so LD will not interfere with the bank selection bit toggling activity that must go on during the initial access.

The LD signal is combinatorial so it can be active during the first cycle of a new instruction request.

Bank Select Signal

The Q02E register bit is used to indicate which memory bank should provide valid instruction data to the instruction bus in any given cycle. Each time another instruction word is accessed, this bit is toggled. The bit is originally loaded from the address-bus bit A02.

$$\begin{aligned} \text{Q02E} &:= \text{LD} \cdot \text{AX2} && \text{;Load counter} \\ &+ \text{LD} \cdot \overline{\text{CNT}} \cdot \overline{\text{IQ3}} \cdot \overline{\text{IQ4}} \cdot \text{Q02E} && \text{;Hold counter} \\ &+ \overline{\text{LD}} \cdot \text{IQ3} \cdot \overline{\text{Q02E}} \\ &+ \overline{\text{LD}} \cdot \text{IQ4} \cdot \overline{\text{Q02E}} \\ &+ \overline{\text{LD}} \cdot \text{CNT} \cdot \overline{\text{Q02E}} && \text{;Counting} \end{aligned}$$

Q02E is used directly in the generation of the serial shift clock for the VDRAM. Before the first word in the serial shifter is available at the SD output of the VDRAM, one serial shift clock rising edge must occur. The IQ3 and IQ4 signals are used to force the first rising edges on the serial shift clock for each memory bank. After the IQ1 signal goes invalid, any further toggling of the bank select signal and the serial port shift clock will come as a result of valid $\overline{\text{IBREQ}}$ cycles.

Even Bank Address Incrementer and LSB Latch

In this design, the lack of address counters requires a new way of satisfying the need to increment the even bank address before the first word access, when the initial address is odd. To deal with this need, a PALCE16V8-D is used to build a flow-through

incrementer. The increment function is selective because when address bit A02 is Low, indicating an even-word initial address, no increment is done and the address passes through unchanged. When A02 is High, the memory address is incremented. The A02 bit is used to select which bank is read or written during a data access. Thus, the A02 bit is required to be stable throughout the entire access. So it may be held stable after the address bus is released, the A02 bit is latched within the incrementer by the DQ1 signal. The equations for the increment and latch functions are shown in Figure 9-11.

Count Signal

The count (CNT) signal in this design is reduced to being an enable on the toggling action of the Q02E bit. Following the initial instruction word access determined by IQ1, the CNT signal is active for each valid instruction burst request determined by IBREQ.D and IBACK.D.

$$\text{CNT} = \text{IQ4} + \overline{\text{IQ4}} \cdot \text{IBREQ.D}$$

Transfer Cycle Enable and DQ Port Output Enable

On a VDRAM, there is a dual function signal, called Transfer (TR), which controls when a row transfer cycle is performed and also when the random I/O data port is output enabled. When TR is active during the active edge of $\overline{\text{RAS}}$, a transfer cycle is performed.

The timing of TR is critical when performing this function. It must stay active for a minimum of 90 ns after $\overline{\text{RAS}}$ goes active when the Fujitsu VDRAM (MB81461-12) is used, or 100 ns after $\overline{\text{RAS}}$ goes active when the NEC VDRAM (PD41264-12) is used. The signal must also be inactive before the serial shift clock may go from Low to High, to clock out the first instruction word: 25 ns before for the Fujitsu VDRAM, or 10 ns before for the NEC VDRAM.

To make the above timing constraint fit within the six-cycle initial access time of this memory design, a delay line must be used to precisely set the duration of the TR signal. A separate RAS signal, which is not loaded by the capacitance of either memory bank, is the input to the delay line. The output for a 90-ns delay is TEXTIT1 and for a 100-ns delay is TEXTIT2. More details of this timing are provided in the intra-cycle timing section of this chapter.

TR goes active with IREQ, so TR is set up before $\overline{\text{RAS}}$ goes active. TR latches itself active until the appropriate TEXTIT signal goes active. The NEC input is strapped to Low when the NEC memory is used, or to High when the Fujitsu VDRAM is used.

Finally, when DQ2 is active during a non-transfer cycle of a read operation, the active TR signal enables the DQ port output.

$$\begin{aligned} \text{TR0} = & \overline{\text{DQ1}} \cdot \text{IREQ} \\ & + \overline{\text{DQ1}} \cdot \text{TR0} \cdot \overline{\text{NEC}} \cdot \overline{\text{TEXTIT1}} \\ & + \overline{\text{DQ1}} \cdot \text{TR0} \cdot \overline{\text{NEC}} \cdot \overline{\text{TEXTIT2}} \\ & + \text{DQ2} \cdot \overline{\text{WE}} \end{aligned}$$

Shift Clock

The signal clocking each new instruction out of the serial port is referred to as SAS. This signal must be Low at the time TR goes inactive and it must remain Low for the 25-ns or

10-ns period noted earlier. Once that timing constraint is satisfied, the next rising edge of SAS clocks the serial port output. SAS is held Low while IQ1 is active and IQ4 is inactive. After that time, SAS is controlled by the Q02E bank selection signal so a new instruction is clocked out every other system clock cycle when the CNT signal is active.

There is a special requirement on SAS immediately following system power-on time. The SAS signal must be cycled at least eight times before proper device operation is achieved following a power-on sequence. To ensure this is done, the system reset signal is used to connect the system clock to SAS. This ensures SAS is cycled during the system power-on reset time.

$$\begin{aligned} \overline{\text{SAS0}} &= \overline{\text{RESET}} \cdot \overline{\text{SYSCLK}} \\ &+ \overline{\text{RESET}} \cdot \text{IQ1} \cdot \overline{\text{IQ4}} \\ &+ \overline{\text{RESET}} \cdot \text{IQ4} \cdot \text{Q02E} \\ &+ \overline{\text{RESET}} \cdot \overline{\text{IQ1}} \cdot \text{Q02E} \end{aligned}$$

$$\begin{aligned} \text{SAS1} &= \overline{\text{RESET}} \cdot \overline{\text{SYSCLK}} \\ &+ \overline{\text{RESET}} \cdot \text{IQ1} \cdot \overline{\text{IQ4}} \\ &+ \overline{\text{RESET}} \cdot \text{IQ4} \cdot \overline{\text{Q02E}} \\ &+ \overline{\text{RESET}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{Q02E}} \end{aligned}$$

IRDY

The Instruction Ready ($\overline{\text{IRDY}}$) signal indicates there is valid read data on the instruction bus.

$$\begin{aligned} \overline{\text{IRDY}} &= \overline{\text{IQ3}} \cdot \text{IQ4} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{IBREQ.D}} \end{aligned}$$

This memory design is always ready with data in the IACCESS state indicated by $\overline{\text{IQ3}} \cdot \text{IQ4}$. The memory is also ready when $\overline{\text{IBREQ}}$ is active with $\overline{\text{IBACK}}$ in the previous cycle with no invalid bus condition, following the initial instruction word access.

The reason that $\overline{\text{IRDY}}$ must be a combinatorial signal is that $\overline{\text{IBREQ}}$ comes very late in the previous cycle and must be registered. There is no $\overline{\text{IBREQ}}$ qualifying time available in the previous cycle before SYSCLK rises. This means the information that $\overline{\text{IBREQ}}$ was active in the last cycle is not available until the cycle in which $\overline{\text{IRDY}}$ should go active for a resumption of a suspended burst access.

IOE

The instruction output enable signal (IOE) controls the output enable of the multiplexers. It is only needed if more than one memory section can drive the instruction bus, otherwise it can be omitted. The logic is the same as for $\overline{\text{IRDY}}$ generation. For an approach with buffers instead of multiplexers, the signals must be qualified with the bank select signal (Q02E). Therefore, this signal is implemented instead of using $\overline{\text{IRDY}}$ directly for control of the multiplexer output.

$$\begin{aligned} \text{IOE} &= \overline{\text{IQ3}} \cdot \text{IQ4} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{IBREQ.D}} \end{aligned}$$

DRDY

The Data Ready ($\overline{\text{DRDY}}$) signal is the equivalent of $\overline{\text{IRDY}}$, but for data accesses. The difference is that since no burst accesses are supported, $\overline{\text{DRDY}}$ will go active only once

in each simple access during the DACCESS state in a read, or during DCAS or WAIT in a write operation. Due to different data hold times for the Fujitsu and NEC VDRAMs, $\overline{\text{DRDY}}$ must be held until the WAIT state when using the NEC VDRAM.

$$\begin{aligned}\text{DRDY} &= \overline{\text{WE}} \cdot \text{DQ4} \\ &+ \text{WE} \cdot \text{DQ2} \cdot \overline{\text{DQ3}} \cdot \overline{\text{NEC}} \\ &+ \text{WE} \cdot \text{DQ3} \cdot \text{DQ4} \cdot \text{NEC}\end{aligned}$$

Pipeline Enable

During a read operation, the data address is no longer needed on the address bus following the DCAS state. So, to help improve system performance, the Pipeline ENable ($\overline{\text{PEN}}$) signal response is made active during the DCAS state. This active $\overline{\text{PEN}}$ signal tells the processor the address is no longer needed and it allows the processor to place a new address on the bus. In cases where the next address to be issued is for an instruction or data access from a different block of memory, the next access can begin while the current data access finishes.

$$\overline{\text{PEN}} = \text{DQ2} \cdot \overline{\text{DQ3}}$$

WE

Write Enable (WE) signal is not allowed to be active during the row transfer sequence beginning each non-sequential instruction access. This is because no write operations are supported for the serial port. During a data access, the read/write line is latched by the DQ2 signal at the end of the DCAS state.

WE shows that a write to the memory section is done regardless of the half-word or byte address.

$$\begin{aligned}\text{WE} &= \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \text{DQ2} \cdot \text{WE}\end{aligned}$$

To make use of the byte write capability of the Am29000 processor, the following signals are used. Please note this is true for big endian notation only.

$\overline{\text{WE0}}$ = Enable byte write for Bits 31–24

$\overline{\text{WE1}}$ = Enable byte write for Bits 23–16

$\overline{\text{WE2}}$ = Enable byte write for Bits 15–8

$\overline{\text{WE3}}$ = Enable byte write for Bits 7–0

The following signals are not real signals and are used only as macros for the $\overline{\text{WE0}}$ – $\overline{\text{WE3}}$ equations shown below.

$\text{WEN} = \overline{\text{OPT1}} \cdot \overline{\text{OPT0}}$;(32-bit Word Enable)
$\text{HEN0} = \text{OPT1} \cdot \overline{\text{OPT0}} \cdot \overline{\text{A1}}$;(Half-Word Enable, Bits 31–16)
$\text{HEN1} = \text{OPT1} \cdot \overline{\text{OPT0}} \cdot \text{A1}$;(Half-Word Enable, Bits 15–0)
$\text{BEN0} = \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \overline{\text{A1}} \cdot \overline{\text{A0}}$;(Byte Enable, Bits 31–24)
$\text{BEN1} = \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \overline{\text{A1}} \cdot \text{A0}$;(Byte Enable, Bits 23–16)
$\text{BEN2} = \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \text{A1} \cdot \overline{\text{A0}}$;(Byte Enable, Bits 15–8)
$\text{BEN3} = \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \text{A1} \cdot \text{A0}$;(Byte Enable, Bits 7–0)

The equations for WE0–WE3 are as follows:

$$\begin{aligned} WE0 = & \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot WEN \\ & + \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot HEN0 \\ & + \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot BEN0 \\ & + \overline{IQ1} \cdot DQ1 \cdot DQ2 \cdot WE0 \end{aligned}$$

$$\begin{aligned} WE1 = & \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot WEN \\ & + \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot HEN0 \\ & + \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot BEN1 \\ & + \overline{IQ1} \cdot DQ1 \cdot DQ2 \cdot WE1 \end{aligned}$$

$$\begin{aligned} WE2 = & \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot WEN \\ & + \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot HEN1 \\ & + \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot BEN2 \\ & + \overline{IQ1} \cdot DQ1 \cdot DQ2 \cdot WE2 \end{aligned}$$

$$\begin{aligned} WE3 = & \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot WEN \\ & + \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot HEN1 \\ & + \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \cdot BEN3 \\ & + \overline{IQ1} \cdot DQ1 \cdot DQ2 \cdot WE3 \end{aligned}$$

Row Address Strobes

There are three identical Row Address Strobe (\overline{RAS}) lines. Two are used to drive the memories and one drives the delay line used to switch the address mux at the appropriate time and to control the duration of the transfer signal. Multiple lines are used to split the capacitive and inductive load of the memory array to improve signal speed.

\overline{RAS} is made active by a valid ISTART, DSTART or refresh condition. \overline{RAS} is held active for three cycles to satisfy the minimum pulse-width requirement on \overline{RAS} .

$$\begin{aligned} RAS := & \overline{BINV} \cdot \overline{RAS} \cdot ISTART \\ & + \overline{BINV} \cdot \overline{RAS} \cdot DSTART \\ & + \overline{RAS} \cdot \overline{PC1} \cdot \overline{RFACK} \\ & + RAS \cdot IQ1 \cdot \overline{IQ3} \\ & + RAS \cdot DQ1 \cdot \overline{DQ3} \\ & + RAS \cdot \overline{RFACK} \cdot \overline{RQ3} \end{aligned}$$

Column Address Strobes

As with the \overline{RAS} lines, the \overline{CAS} lines are duplicated to split the memory load. \overline{CAS} becomes active in the cycle after \overline{RAS} during instruction or data accesses. During a data write access, \overline{CAS} is enabled only when the appropriate bank is written with data. This is controlled by the latched value of address bit 2 (AX2). Only in the case of a refresh sequence will \overline{CAS} be made active prior to \overline{RAS} . This will initiate a CAS-before-RAS refresh cycle in the memories. In this case, \overline{CAS} is made active during the IDLE state.

$$\begin{aligned} CAS0 := & RAS \cdot IQ1 \\ & + RAS \cdot DQ1 \cdot \overline{AX2} \\ & + \overline{RAS} \cdot \overline{IQ1} \cdot DQ1 \cdot \overline{RFRQ0} \end{aligned}$$

$$\begin{aligned} CAS1 := & RAS \cdot IQ1 + RAS \cdot DQ1 \cdot \overline{AX2} \\ & + \overline{RAS} \cdot \overline{IQ1} \cdot \overline{DQ1} \cdot \overline{RFRQ0} \end{aligned}$$

INTRA-CYCLE TIMING

This memory architecture has five timing sequences of interest. The first is a cycle used to decode the memory address and control signals from the processor. At the end of this decode cycle, the $\overline{\text{RAS}}$ registers are loaded to begin the initial access of memory if the address selects the memory block.

Following the decode cycle is the Row Address cycle, in which the row address strobe is made active at the beginning of the cycle, and the address multiplexer is later switched between the row address and the column address.

The third timing is a data access, where the $\overline{\text{CAS}}$ signal goes active to begin a read operation or perform a write operation.

The fourth is the critical timing sequence between $\overline{\text{RAS}}$ going active and the first shift clock (SAS) active edge which occurs in the row transfer of the initial access of an instruction burst.

The fifth timing is a burst access. This is the timing between SAS going High and a valid instruction being transferred to the processor. This time is designed to fit within two clock cycles.

The combination of a decode cycle followed by the row-address cycle and by a data-read access time defines a five-cycle read of data. Subsequent data-read operations may be six cycles long if the next data address appears during the PC2 precharge state.

For a data write, the access time is made up of a decode cycle followed by a data write, in which $\overline{\text{DRDY}}$ is active in the second or third cycle after decode. The write operation thus takes three to four cycles. Subsequent data-write cycles may take up to six cycles to complete if the next address appears during the data WAIT state (i.e., during the memory-precharge time). A read following a write could take up to eight cycles to complete if it started during the precharge time of the previous access.

The initial access time of an instruction access is made up of a decode cycle, plus a row transfer sequence, plus the first burst access. This totals six cycles. Again, this could be extended up to nine cycles if the instruction address were to appear during the precharge time following a data-write operation or up to seven cycles if following a data read.

After the initial access, all burst instruction accesses use a two-clock-cycle timing. Because two memory banks are interleaved, the apparent access time from the viewpoint of the system bus is only one cycle per burst access following the initial access.

Decode Timing

Within the decode cycle, the address timing path is made up of:

- The Am29000 processor clock to address and control valid delay of 14 ns
- Address decode logic PAL device delay of 10 ns
- The setup time of the $\overline{\text{RAS}}$ PAL device, 10 ns.

Assuming D-speed PAL devices, those times total 34 ns, as shown in Figure 9-12.

Also, within the decode cycle time is the control signal to response signal path. In fact, this timing path is present in every cycle in the sense that the memory response signals must be valid in every clock cycle. This delay path is made up of:


- Clock-to-output time of registers within the control logic state machine PAL device, 8 ns
- Propagation delay of the control logic PAL device, 10 ns
- Propagation delay of a logical OR gate on the response signals from each memory block, 10 ns
- Control signal set-up time of the processor, 12 ns

Again assuming D-speed PAL devices, these delay path times total 40 ns.

Row Address Timing


Referring to Figure 9-13, within the row-address cycle, the $\overline{\text{RAS}}$ line goes low, which initiates a time delay signal later causing the address multiplexer to change from the row to the column address.

Figure 9-12 VDRAM Interleaved Bank Memory Decode Cycle

 

10623C-084

Figure 9-13 Row Address Timing

 

10623C-085

This delay path is made up of:

- Clock-to-output time of $\overline{\text{RAS}}$ signal registers within the control-logic state machine PAL device (8 ns) plus an added delay due to capacitive and inductive loading by the memory array of the PAL device outputs. The estimated delay is 6.5 ns. This is added to the 8 ns delay of the $\overline{\text{RAS}}$ line (standard 50 pF load) for a total of 14.5 ns, worst case.
- Mux switch control signal delay path, which runs in parallel with the memory $\overline{\text{RAS}}$ delay just described. This mux signal delay is made up of the clock-to-output delay of a lightly loaded $\overline{\text{RAS}}$ signal (8 ns) plus the delay line time (20 ns).
- Minimum and maximum switching time of the address multiplexer, 4 ns to 9.5 ns, plus added delay for heavy loading (same as calculated above), 6.5 ns.

Thus, the memory $\overline{\text{RAS}}$ signals are stable no later than 14.5 ns into the cycle, and the address mux output can change no sooner than 32 ns (assuming $\overline{\text{RAS}}$ outputs from the same PAL device will always have similar delays). So the address hold time provided after $\overline{\text{RAS}}$ goes active is 17.5 ns. This works out to satisfy the 15 ns of required address hold time after $\overline{\text{RAS}}$ goes active. Also, the column address is settled by no later than 44 ns into the cycle. So the column address is set up prior the $\overline{\text{CAS}}$ going active in the next cycle.

$\overline{\text{CAS}}$ -to-Data Ready

In a data-read operation, the Column Address Strobe ($\overline{\text{CAS}}$) signal-to-end of $\overline{\text{DRDY}}$ cycle is made up of:


- $\overline{\text{CAS}}$ signal clock-to-output time, 8 ns, plus added delay for heavier-than-normal output loading, as determined above, 6.5 ns
- Memory access delay from $\overline{\text{CAS}}$, 60 ns
- Data bus transceiver propagation delay, 10 ns
- Processor set-up time, 6 ns

This totals 80.5 ns, which translates into just a little more than two cycles. Therefore, $\overline{\text{DRDY}}$ is not made active until the second cycle following the DCAS state.

In a data-write operation, the data is written by the falling edge of $\overline{\text{CAS}}$. But the data hold time relative to $\overline{\text{RAS}}$ going active may also have to be satisfied before $\overline{\text{DRDY}}$ is made active to free the address and data buses.

For the Fujitsu memory, only the data hold time relative to $\overline{\text{CAS}}$ is required; this is 30 ns after $\overline{\text{CAS}}$ active. The Am29000 processor will provide a minimum of 4 ns data hold time. The data transceiver will provide an additional minimum of 4 ns hold time beyond the end of the DCAS cycle. As shown in Figure 9-14, these will ensure meeting the hold time if $\overline{\text{DRDY}}$ is active in the DCAS cycle.


For the NEC memory, the hold time relative to $\overline{\text{RAS}}$ is the longer delay path; this is 95 ns from $\overline{\text{RAS}}$ going active. This implies the data must be held 29.5 ns into the WAIT state after DCAS. So in this case, $\overline{\text{DRDY}}$ must not go active until the WAIT state after DCAS as shown in Figure 9-15.

  Figure 9-14 $\overline{\text{CAS}}$ -to-Data Ready Timing


$\overline{\text{RAS}}$ -to-Shift Clock Timing

Referring to Figure 9-15, in order to maintain a six-cycle initial instruction access time, only three cycles can be used for the timing of signals between $\overline{\text{RAS}}$ and SAS. In that time, the TR signal must be active for 90 ns to 100 ns after $\overline{\text{RAS}}$, and it must be inactive 25 ns to 10 ns before SAS goes active, depending on the memory used. It is a tight fit. The timing is as follows:

- Clock-to-memory $\overline{\text{RAS}}$ delay, 8 ns, plus the added delay for heavy output loading of 6.5 ns, for a total of 14.5 ns
- In parallel with the memory $\overline{\text{RAS}}$, a separate copy of $\overline{\text{RAS}}$ not loaded by the memory array is used to drive the delay line determining the end of the TR signal. Its clock-to-output delay time is 8 ns
- Delay line time of 90 ns or 100 ns
- Propagation delay of the PAL device, which generates TR from the output of the delay line, is a minimum of 3 ns and a maximum of 10 ns, plus an output loading delay of 6.5 ns
- The SAS output is combinatorial and is dependent on registered input signals. Its minimum delay is the minimum clock-to-output delay plus the minimum propagation delay of a D-speed PAL device, plus the added delay for memory loading (3 ns + 3 ns + 6.5 ns = 12.5 ns). Its maximum delay consists of 8 ns of clock-to-output delay, 10 ns of propagation delay, and a loading delay of 6.5 ns for a total delay of 24.5 ns.

Figure 9-15 NEC Memory Write Data Hold Time

10623C-087

Assuming minimum delays in the TR and SAS signals and maximum delays in the \overline{RAS} signals, the hold time for TR will just be met for either the NEC or Fujitsu memories. For the Fujitsu memory, the TR setup time before SAS will also just be met as shown in Figure 9-16. For the NEC memory there is 5 ns of margin as shown in Figure 9-17.

The above relies on the fact that all \overline{RAS} outputs are implemented in the same PAL device and TR and SAS outputs reside in the same PAL device. The PAL device outputs for related signals will thus always track each other with respect to minimum or maximum delay times.

Burst Timing

Within the burst access cycle, the address to data path timing is determined by:

- The clock-to-output time of Q02E, 8 ns for a D-speed PAL device
- Propagation delay of SAS PAL, 10 ns, plus added delay for heavy capacitive and inductive load as was done for the \overline{RAS} line. The same derating delay of 6.5 ns applies.
- Memory access time for serial port, 40 ns
- F157 Multiplexer delay, 6.5 ns
- The processor set-up time, 6 ns.


Those delays produce a worst-case total of 77 ns as shown in Figure 9-18.

INTER-CYCLE TIMING

Inter-cycle timing for instruction, data-read, and data-write cycles are provided in Figures 9-19 through 9-21. In these timing diagrams, the horizontal time scale is 20 ns per division.

Figure 9-16 Fujitsu Transfer Enable Timing

Fujitsu Memory

 

10623C-088

Figure 9-17 NEC Transfer Enable Timing

NEC Memory

 


Figure 9-18 Burst Access Timing



 


Figure 9-19 VDRAM Instruction Burst Timing

 

10623C-093


Figure 9-20 VDRAM Data Read Timing

 

New access can start in parallel to precharge

10623C-092

Figure 9-21 VDRAM Data Write Timing

 

Early write due to \overline{WE} going active before \overline{CAS} active. Also at \overline{WE} is active, DATA is valid.

10623C-093

PARTS LIST

The parts list for the Am29000 Processor Interleaved VRAM Interface is provided in Table 9-1.

Table 9-1 Interleaved VRAM Interface Parts List

Item No.	Quantity	Device Description
U1	1	PALCE16V8-D
U2	1	PAL20L8-B
U3	1	AmPAL22V10-25
U4	1	74F175
U5-U8	4	74F157
U9	1	PALCE16V8-D
U10	1	PAL16R4-D
U11	1	PAL20R8-D
U12	1	PAL20R4-D
U13	1	PAL20L8-D
U14-U29	16	MB81461-12 or PD41264
U30-U37	8	74F157
U38	1	XTTLDM-100
38 packages		

FINAL DISCUSSION

Looking at the design, there may be concerns about the size of the design, whether it is compact or large. For an objective analysis, first look at the design from a theoretical standpoint, without considering the type of processor being used.

To perform single-cycle bursts with DRAM at clock speeds up to 33 MHz, you must use two banks of interleaved DRAMs. Because of the 32-bit wide architecture, you need a minimum of 16 DRAMs (64K x 4-bit devices), eight DRAMs per bank.

You also need multiplexers and drivers for interleaving, which adds another 16 parts to the design. In this design, only the multiplexers are needed, so only eight parts are added. For a burst start on an odd address, you need one incrementer PAL device in any case.

For DRAMs, the address lines must be multiplexed. This implies the addition of four multiplexers.

A refresh counter must be implemented. This implies the addition of one PAL device.

In any case, you need either a delay line or a high-speed clocked state machine for fast generation of $\overline{\text{RAS}}$ and $\overline{\text{CAS}}$ signals.

In summary, the raw logic, which does not depend on the type of processor used, requires 31 devices. Only seven PAL devices are used for all the rest of the design, including the state machines, the generation of the $\overline{\text{RAS}}$ and $\overline{\text{CAS}}$ signals, and the interface to the Am29000 processor. By using higher-integrated PAL devices or higher-density logic, this number could be reduced further.



SINGLE-BANK VDRAM

OVERVIEW

For an overview of the relative advantages and disadvantages of VDRAM, see the first section of the previous chapter.

Currently available VDRAMs are able to support a 30-ns serial shift rate, so a single bank VDRAM system can support an Am29000 processor system running at 20 MHz.

MEMORY FEATURES

The VDRAM memory design described in this chapter is a reduced version of the dual-bank design in the previous chapter. The major difference is only one bank of VDRAM is used. You will find many similarities between this design and the one in the previous chapter.

Figure 10-1 is a high-level block diagram of a single-bank VDRAM memory. The bank is a minimum of 64K words deep (32 bits per word).

A non-sequential instruction access requires one cycle for address decoding plus five additional cycles for the first word accessed. The burst access timing is similar to that used in the previous chapter; each burst access is one cycle long. The end result is a memory providing a six-cycle access time for the first word of a non-sequential instruction access, and single-cycle access for subsequent words in a burst transfer. A data-read access requires one cycle for address decoding plus four additional cycles to complete the access.


A data write access requires one cycle for address decode plus two cycles or three cycles (depending on the memory used) to take data from the bus. The write operation continues internal to the memory for one or two additional cycles, but the data bus is released after data is taken from the bus.

No burst accesses are supported for data. All data read accesses are five cycles long and all write accesses are three or four cycles long. That is assuming the memory has internally completed a write operation and/or $\overline{\text{RAS}}$ precharge before the next access begins. If write completion time or $\overline{\text{RAS}}$ precharge time has not been satisfied, a subsequent data access can require up to eight cycles to complete. This is based on the worst case, a data read immediately following a data write operation.

INTERFACE LOGIC BLOCK DIAGRAM

A block diagram of the interleaved VDRAM memory is shown in Figure 10-2. The various circuit blocks are described below.

Figure 10-1 Am29000 Processor with VDRAM Memory

 

10623C-094


The Memory

The memories are 64K x 4 bit VDRAMs supplied by either Fujitsu (MB81461-12) or NEC (PD41264-12). These memories have common data-in and data-out lines. Their access speed is 120 ns. Eight devices are required to form the 32-bit wide instruction word for the Am29000 processor. These are shown as devices U10 through U17.

VDRAM is used in this design to illustrate the savings in complexity, component count, and cost that the VDRAM architecture can provide. These savings come largely from the fact that the instruction and data words can reside in a common memory array still allowing concurrent dual-port access. Using one memory array, instead of split instruction and data memories, eliminates one entire set of memory control logic and data buffers. Also, the number of remaining control-logic and data-buffer circuits is reduced, since external buffers are no longer needed to support both data and instruction ports into the instruction memory.

The VDRAM structure allows the boundary between instruction and data space to be flexible and dynamic, thereby providing for more efficient use of memory than a system that splits memory. This, in turn, may lead to reduced memory requirements in general.

Figure 10-2 Single-Bank VDRAM Memory Block Diagram

 

Data Bus Connection

The memory random access data I/O port is connected directly to the Am29000 processor data bus lines. Isolating transceivers are not necessary so they are not used. This eliminates transceiver delays.

If higher driver currents were necessary, transceivers could be inserted between the data outputs of the VDRAMs and the Am29000 processor data bus lines.

Instruction Bus Connection

Because only one bank is used, the memory serial data outputs are also connected directly to the instruction bus of the Am29000 processor. This eliminates the buffer delays present in the dual-bank design.

Address Multiplexers

The upper and lower eight bits of memory address must be multiplexed into the address inputs of the memories. Discrete multiplexers are used to perform this function. These devices are shown as U5 through U8.

Note that in this design, the address is taken directly from the bus and through the multiplexers to the memories. No latching or registering of the address is done. This approach reduces the component count and complexity of the design, illustrating a lower-cost memory design. Doing this requires the memory control logic to force the Am29000 processor to hold the address stable on the bus until after the $\overline{\text{RAS}}$ and Column Address Strobe ($\overline{\text{CAS}}$) have gone active. This is done by delaying the assertion of $\overline{\text{IBACK}}$ or $\overline{\text{PEN}}$ during instruction or data accesses, respectively.

This approach reduces system performance somewhat, at least when compared with a split instruction and data memory system, or a system with multiple blocks of VDRAM in which one block could be addressed for an instruction fetch while another block is addressed for a data access. This is because the processor must, at times, hold an address on the bus when it might otherwise have been able to begin another access on an alternate memory block, assuming a memory that latches the address.

But in a system having a single block of VDRAM, there is no benefit to latching the address from the bus. This is because the memory cannot be ready to begin another access until the access in progress is completed, and the memory has completed the precharge cycles that must occur between all non-sequential accesses.

A word of warning: Do not use inverting buffers or multiplexers on VDRAM address lines. Inverted random access I/O (DQ) port addressing would conflict with the sequentially incremented addressing required by the design of the serial port.

VDRAM Shifter

Since a VDRAM uses a shift mechanism to provide the serial output of instruction code, there is no need for an address counter. The initial address for an instruction burst request determines the starting location in the memory row to be shifted out. All subsequent instruction words are read by providing a shift clock to the VDRAM. Also, because the VDRAM shifter row is 256 words, the Am29000 processor always provides a new address at the right time when a row boundary is crossed. In addition, no address counter is required for data accesses, since no burst data accesses are supported in this memory design.

Registered Control Signals

As noted earlier, the timing of the $\overline{\text{IBREQ}}$ control signal requires it be registered by a low-setup-time register; a F175 register is used (U3, shown in Figure 10-2).

Interface Control Logic

This logic must generate the memory response signals, manage the loading of memory addresses, generate $\overline{\text{RAS}}$ and $\overline{\text{CAS}}$ signals, and perform memory refresh. The logic functions needed for this require six PAL devices: one PAL20L8-B, one AmPAL22V10-25, one AmPAL22V10-15, one PAL20L8-D, one PAL20R8-B, and one PAL20R4-B.

Device U1, a PAL20L8-B, performs address decode for instruction and data accesses. Its outputs indicate when the memory block has been addressed and an access is to begin.

Device U2, an AmPAL22V10-25, acts as a refresh-interval counter and refresh-request logic.



Devices U6-U9, one AmPAL22V10-15, one PAL20L8-D, one PAL20R8-B, and one PAL20R4-B, form a state machine controlling the \overline{RAS} , \overline{CAS} , shift clock, transfer cycle enables, and memory-response signals.

Response Signal Gating

The memory-response signals from all system bus devices are logically ORed together by a PAL device before being returned to the Am29000 processor. The gates in this PAL device are not included in the component count of this memory design since they are shared by all the bus devices in the system, and as such, are part of the overhead needed in any Am29000 processor system.

Byte Write Capability

The interface logic supports the byte write capability of the Am29000 processor. It uses the signals OPT1, OPT0, A1, and A0 to generate the write enable signals WE0–WE3. This design supports only big endian byte ordering.

MEMORY INTERFACE LOGIC EQUATIONS

State Machine

The control logic for this memory can be thought of as a Mealy-type state machine in which the outputs are a function of the inputs and the present state of the machine. This structure is required because some of the output signals must be based on inputs which are not valid until the same cycle in which the outputs are required to take control of the memory. As shown in Figure 10-3, this state machine can be described as having 18 states. (Note: A timing diagram is provided at the end of this chapter.)

It is important to note that in this design, the instruction burst is never preempted by the slave. The reason for this is that VDRAMs are used; no contention between instruction bursts and data accesses can occur. Also, the length of the shifters is a minimum of 256 words. After 256 words, the Am29000 processor automatically preempts the burst by itself so it does not have to be preempted by the slave.


Therefore, in this design, no logic is needed to preempt an instruction burst.

IDLE is the default state of the interface state machine. It is characterized by the lack of any instruction access, data access, or refresh activity in progress. This state serves as a way of identifying when the memory is not being accessed and could be placed into a low-power mode. This state also serves as a precharge cycle for the memory when a transition is made between instruction, data, and refresh sequences.

A transition to either the IRAS or DRAS state occurs when an address selecting this memory block is placed on the address bus. These transitions are inhibited if the \overline{BINV} signal is active. A transition to the RQ1 state occurs when a refresh request is active. Refresh takes priority over any pending instruction or data-access request.

There are five Virtual States shown in Figure 10-3; they are IQ1 through IQ4 and IACCESS. These states are needed because the serial data (SD) port of the VDRAM operates independently of the random access I/O (DQ) port after a row transfer cycle is completed. The states help illustrate what might be called the “split personality” of the state machine. Once a transfer cycle begins, there are in effect two active states in this state machine. One state tracks the activity of the serial port control signals, and the other tracks the activity of signals associated with the random access I/O port.

Figure 10-3 VDRAM Memory State Diagram

 

10623C-096

The active states can be thought of as two tokens, labeled SD and DQ, being moved around a game board. The DQ token is never allowed to follow the dotted line to the virtual states. The SD token is always in one of the virtual states or the IDLE state; it never enters any of the other states. When the SD token enters the IDLE state, it cannot leave until the DQ token is also in IDLE and the ISTART condition is true.

When both tokens are in IDLE and ISTART is true, the SD token moves to the IQ1 state and the DQ token moves to the IRAS state. This would represent the beginning of a row transfer to the serial-shift port. The DQ token then tracks the progress of \overline{RAS} , \overline{CAS} , and address signals applied to the VDRAM. When the transfer sequence is finished, the DQ token goes through the precharge states and returns to IDLE. The SD token proceeds

through the IQ states, counting off the delay needed until the first instruction is ready at the output of the SD port. In the IQ2 state, $\overline{\text{IBACK}}$ is made active to release the address bus. In IQ3 and IQ4, the shift clock and bank select signals begin operation to allow the access of the first instruction word. In IACCESS, $\overline{\text{IRDY}}$ is allowed to go active. During subsequent cycles of an instruction burst access, the active state remains IACCESS.

While the active state for instruction accessing is IACCESS, the DQ token is free to move through data access states or refresh states completely independent of the instruction access in progress. When an instruction burst ends, the SD token returns to IDLE and must wait until the DQ token completes an access or refresh sequence followed by precharge before a new transfer cycle may begin.

The IRAS state occurs during the first cycle of a row transfer to the SD port following a new instruction address being presented on the address bus. During this state, the instruction output multiplexer is enabled, Ready response lines are held inactive and the $\overline{\text{RAS}}$ lines go active. $\overline{\text{RAS}}$ is used as the input to a delay line whose output will switch the address mux to the column address after the row address hold time is satisfied. The transition to the ICAS state is unconditional.

During the ICAS state, $\overline{\text{CAS}}$ goes active to start the transfer cycle. Since the $\overline{\text{RAS}}$ minimum pulse width is 120 ns, and the minimum $\overline{\text{CAS}}$ pulse width is 60 ns, a WAIT state follows the ICAS state before the unconditional transition to the first precharge state.

During the precharge states, $\overline{\text{RAS}}$ goes inactive. The precharge period for the memory used is 100 ns, so a second and third precharge cycle is done during the PC2 and IDLE states, which unconditionally follow the PC1 cycle.

During a DQ port read sequence, the DRAS state generates $\overline{\text{RAS}}$ and the address-mux select signals. The DCAS state makes $\overline{\text{CAS}}$ active. Since the access time from $\overline{\text{CAS}}$ is 60 ns, the total of $\overline{\text{CAS}}$ -clock-to-output delay, plus access time, plus processor setup time is in excess of 95 ns. This timing will require a WAIT cycle for future upgrades, finally followed by the DACCESS cycle. During DACCESS, the $\overline{\text{DRDY}}$ signal is made active.

The DQ port write access is different only in that the $\overline{\text{DRDY}}$ signal may be made active during DCAS, since the data from the bus is written into the memory by the falling edge of the $\overline{\text{CAS}}$ signal. This is done by using the early write cycle timing of the VDRAM. Doing this allows the processor to begin a new address cycle on the address bus during the WAIT cycle. This may help improve system performance if the new address is directed at a different memory block that can immediately begin a new access. The WAIT cycle is used to fulfill the minimum $\overline{\text{CAS}}$ active time requirement. The DACCESS simplifies the design by allowing the logic controlling the state transitions to be the same for both read and write operations.

Finally, there is the refresh sequence. Once the IDLE state is reached and a refresh is pending, the refresh sequence starts as the highest priority task of the memory. In fact, during the IDLE cycle, $\overline{\text{CAS}}$ will go active to set up a $\overline{\text{CAS}}$ -before- $\overline{\text{RAS}}$ refresh cycle. This type of refresh cycle makes use of the VDRAM internal refresh counters to supply the refresh address. During RQ1, $\overline{\text{RAS}}$ is made active as in IRAS and DRAS cycles. The RQ2 and RQ3 cycles are used to supply two additional wait states to make up the three cycles needed to satisfy the minimum $\overline{\text{RAS}}$ active time of 120 ns.

Logic Details—Signal By Signal

The logic equations for the memory interface signals are described below. The signals, as implemented in the final PAL device outputs, are often active Low, as required by the actual circuit design. The signals are described in active High terms so the design is a little easier to follow. The PAL device definition files are shown in Figures 10-4 through 10-9; the figures are followed by descriptions of how the equations were derived.

NOTE: All PAL device equations use the following conventions:

- Where a PAL device equation uses a colon followed by an equals sign (:=), the equation signals are registered PAL device outputs.
- Where a PAL device equation uses only an equals sign (=), the equation signals are combinatorial PAL device outputs.
- The Device Pin list is shown near the top of each figure as two lines of signal names. The names occur in pin order, numbered from left to right, 1 through 20. The polarity of each name indicates the actual input or output signal polarity. Signals within the equations are shown as active High (e.g., where signal names in the pin list are: A B C; the equation is $C = A \cdot B$; the inputs are A = Low, B = Low; then the C output will be Low).

Figure 10-4 AmPAL22V10-25 VRAM Refresh Counter/Request Generator Device U2

CLK $\overline{\text{RFACK}}$ $\overline{\text{RQ1}}$ $\overline{\text{RQ2}}$ $\overline{\text{RQ3}}$ NC6 NC7 NC8 NC9 NC10 NC11 GND
 NC13 $\overline{\text{RFRQ0}}$ $\overline{\text{RFQ2}}$ $\overline{\text{RFQ3}}$ $\overline{\text{RFQ4}}$ $\overline{\text{RFQ5}}$ $\overline{\text{RFQ6}}$ $\overline{\text{RFQ7}}$ $\overline{\text{RFQ8}}$ $\overline{\text{RFQ10}}$ $\overline{\text{RFQ9}}$ VCC

$$\text{RFQ2} := \overline{\text{RFQ2}}$$

$$\text{RFQ3} := \overline{\text{RFQ2}} \cdot \overline{\text{RFQ3}} + \overline{\text{RFQ2}} \cdot \text{RFQ3}$$

$$\text{RFQ4} := \overline{\text{RFQ2}} \cdot \text{RFQ3} \cdot \overline{\text{RFQ4}} + \overline{\text{RFQ2}} \cdot \text{RFQ4} + \text{RFQ3} \cdot \text{RFQ4}$$

$$\text{RFQ5} := \overline{\text{RFQ2}} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \overline{\text{RFQ5}} + \overline{\text{RFQ2}} \cdot \text{RFQ5} + \overline{\text{RFQ3}} \cdot \text{RFQ5} + \overline{\text{RFQ4}} \cdot \text{RFQ5}$$

$$\text{RFQ6} := \overline{\text{RFQ2}} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \overline{\text{RFQ6}} + \overline{\text{RFQ2}} \cdot \text{RFQ6} + \overline{\text{RFQ3}} \cdot \text{RFQ6} + \overline{\text{RFQ4}} \cdot \text{RFQ6} + \overline{\text{RFQ5}} \cdot \text{RFQ6}$$

$$\text{RFQ7} := \overline{\text{RFQ2}} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \overline{\text{RFQ7}} + \overline{\text{RFQ2}} \cdot \text{RFQ7} + \overline{\text{RFQ3}} \cdot \text{RFQ7} + \overline{\text{RFQ4}} \cdot \text{RFQ7} + \overline{\text{RFQ5}} \cdot \text{RFQ7} + \overline{\text{RFQ6}} \cdot \text{RFQ7}$$

10623C-097

Figure 10-4 AmPAL22V10-25 VRAM Refresh Counter/Request Generator Device U2 (continued)

$$\begin{aligned} \text{RFQ8} := & \overline{\text{RFQ2}} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \overline{\text{RFQ8}} \\ & + \overline{\text{RFQ2}} \cdot \text{RFQ8} \\ & + \overline{\text{RFQ3}} \cdot \text{RFQ8} \\ & + \overline{\text{RFQ4}} \cdot \text{RFQ8} \\ & + \overline{\text{RFQ5}} \cdot \text{RFQ8} \\ & + \overline{\text{RFQ6}} \cdot \text{RFQ8} \\ & + \overline{\text{RFQ7}} \cdot \text{RFQ8} \end{aligned}$$

$$\begin{aligned} \text{RFQ9} := & \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \text{RFQ8} \cdot \overline{\text{RFQ9}} \\ & + \overline{\text{RFQ2}} \cdot \text{RFQ9} \\ & + \overline{\text{RFQ3}} \cdot \text{RFQ9} \\ & + \overline{\text{RFQ4}} \cdot \text{RFQ9} \\ & + \overline{\text{RFQ5}} \cdot \text{RFQ9} \\ & + \overline{\text{RFQ6}} \cdot \text{RFQ9} \\ & + \overline{\text{RFQ7}} \cdot \text{RFQ9} \\ & + \overline{\text{RFQ8}} \cdot \text{RFQ9} \end{aligned}$$

$$\begin{aligned} \text{RFQ10} := & \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \text{RFQ5} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \text{RFQ8} \cdot \text{RFQ9} \cdot \overline{\text{RFQ10}} \\ & + \overline{\text{RFQ2}} \cdot \text{RFQ10} \\ & + \overline{\text{RFQ3}} \cdot \text{RFQ10} \\ & + \overline{\text{RFQ4}} \cdot \text{RFQ10} \\ & + \overline{\text{RFQ5}} \cdot \text{RFQ10} \\ & + \overline{\text{RFQ6}} \cdot \text{RFQ10} \\ & + \overline{\text{RFQ7}} \cdot \text{RFQ10} \\ & + \overline{\text{RFQ8}} \cdot \text{RFQ10} \\ & + \overline{\text{RFQ9}} \cdot \text{RFQ10} \end{aligned}$$

$$\begin{aligned} \text{SYNCHRONOUS PRESET} = & \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \overline{\text{RFQ5}} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \overline{\text{RFQ8}} \\ & \cdot \text{RFQ9} \cdot \text{RFQ10} \end{aligned}$$

$$\text{RFRQ0} := \text{RFRQ0} \cdot (\overline{\text{RFACK}} \cdot \text{RQ1})$$

Figure 10-5 PAL20L8-B VRAM State Decoder Device U1

$\overline{\text{IREQ}}$ DREQT0 IREQT A31 A30 A29 A28 A27 A26 A25 A24 GND
DREQ DREQT1 ISTART RFRQ0 RFACK PIN 169 IQ1 DQ1 PC1 DSTART NC23 VCC

$$\text{ISTART} = \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFRQ0}} \cdot \text{IME}$$

$$\text{DSTART} = \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFRQ0}} \cdot \text{DME}$$

NOTE: In the above equations, IME and DME are used only for clarity. The actual input terms should be substituted when compiling this device.

$$\text{IME} = \text{IREQ} \cdot \overline{\text{IREQT}} \cdot \overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{A26}} \cdot \overline{\text{A25}} \cdot \overline{\text{A24}} \cdot \text{PIN169}$$

$$\begin{aligned} \text{DME} = & \text{DREQ} \cdot \overline{\text{DREQT0}} \cdot \overline{\text{DREQT1}} \cdot \overline{\text{A31}} \cdot \overline{\text{A30}} \cdot \overline{\text{A29}} \cdot \overline{\text{A28}} \cdot \overline{\text{A27}} \cdot \overline{\text{A26}} \cdot \overline{\text{A25}} \cdot \overline{\text{A24}} \\ & \cdot \text{PIN169} \end{aligned}$$

10623C-098

Figure 10-6 AmPAL22V10-15 VRAM Instruction State Generator—Single Bank Device U6

CLK IREQ ISTART DSTART WE NC6 IBREQ.D BINV NC9 GND
 OE DQ1 DQ2 DQ3 DQ4 IQ1 IQ2 IQ3 IQ4 IRDY DRDY VCC

$$IQ1 := \overline{BINV} \cdot \overline{IQ1} \cdot ISTART \\ + IQ1 \cdot (\overline{IQ3} \cdot \overline{IQ4})$$

$$IQ2 := IQ1 \cdot (\overline{IQ13} \cdot \overline{IQ4})$$

$$IQ3 := IQ2 \cdot \overline{IQ4}$$

$$IQ4 := IQ3$$

$$IRDY = \overline{IQ3} \cdot \overline{IQ4} \\ + IQ1 \cdot \overline{IBREQ.D}$$

$$DQ1 := \overline{BINV} \cdot \overline{DQ1} \cdot DSTART \\ + DQ1 \cdot \overline{DQ4}$$

$$DQ2 := DQ1 \cdot \overline{DQ4}$$

$$DQ3 := DQ2 \cdot \overline{DQ4}$$

$$DQ4 := DQ3 \cdot \overline{DQ4}$$

$$DRDY = \overline{WE} \cdot DQ4 \\ + WE \cdot DQ3 \cdot \overline{DQ4}$$

10623C-099

Figure 10-7 PAL20L8-D VRAM Transfer Generator—Single Bank Device U7

DQ3 TEXIT NC3 DQ1 DQ2 IREQ WE NC8 RESET RW IQ3 GND
 SYSCLK IBREQ SAS TR WE IQ1 IQ4 NC20 PEN NC22 NC23 VCC

$$\overline{SAS} = \overline{RESET} \cdot \overline{SYSCLK} \\ + \overline{RESET} \cdot \overline{IQ1} \cdot \overline{IQ4} \\ + \overline{RESET} \cdot \overline{IQ4} \cdot \overline{IQ3} \cdot \overline{SYSCLK} \\ + \overline{RESET} \cdot \overline{IQ1} \cdot \overline{SYSCLK} \cdot \overline{IBREQ} \cdot \overline{IREQ}$$

$$TR = \overline{DQ1} \cdot \overline{IREQ} \\ + \overline{DQ1} \cdot TR \cdot \overline{TEXIT} \\ + DQ2 \cdot WE$$

$$PEN = DQ2 \cdot \overline{DQ3}$$

$$WE = \overline{IQ1} \cdot DQ1 \cdot \overline{DQ2} \cdot \overline{RW} \\ + \overline{IQ1} \cdot DQ1 \cdot DQ2 \cdot WE$$

10623C-100

Figure 10-8 PAL20R8-B VRAM RAS-CAS Generator—Single Bank Device U8

CLK $\overline{\text{ISTART}}$ $\overline{\text{DSTART}}$ $\overline{\text{IQ1}}$ $\overline{\text{DQ1}}$ $\overline{\text{IQ3}}$ $\overline{\text{DQ3}}$ $\overline{\text{RQ3}}$ $\overline{\text{BINV}}$ NC10 $\overline{\text{RFRQ0}}$ GND
 $\overline{\text{OE}}$ $\overline{\text{RFACK}}$ $\overline{\text{RAS0}}$ NC16 $\overline{\text{RAS}}$ $\overline{\text{PC1}}$ $\overline{\text{PC2}}$ $\overline{\text{CAS}}$ NC21 NC22 NC23 VCC

$$\begin{aligned} \text{RAS0} &:= \overline{\text{BINV}} \cdot \overline{\text{RAS0}} \cdot \overline{\text{ISTART}} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS0}} \cdot \overline{\text{DSTART}} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS0}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFACK}} \\ &+ \overline{\text{RAS0}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{IQ3}} \\ &+ \overline{\text{RAS0}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ3}} \\ &+ \overline{\text{RAS0}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{RQ3}} \end{aligned}$$

$$\begin{aligned} \text{RAS} &:= \overline{\text{BINV}} \cdot \overline{\text{RAS}} \cdot \overline{\text{ISTART}} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS}} \cdot \overline{\text{DSTART}} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS}} \cdot \overline{\text{PC1}} \cdot \overline{\text{RFACK}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{IQ3}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ3}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{RFACK}} \cdot \overline{\text{RQ3}} \end{aligned}$$

$$\begin{aligned} \text{PC1} &:= \overline{\text{PC1}} \cdot \overline{\text{IQ3}} \\ &+ \overline{\text{PC1}} \cdot \overline{\text{DQ3}} \\ &+ \overline{\text{PC1}} \cdot \overline{\text{RQ3}} \\ &+ \overline{\text{PC1}} \cdot \overline{\text{PC2}} \end{aligned}$$

$$\text{PC2} := \overline{\text{PC1}}$$

$$\begin{aligned} \text{CAS} &= \overline{\text{RAS}} \cdot \overline{\text{IQ1}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{DQ1}} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{RFRQ0}} \end{aligned}$$

10623C-101

Figure 10-9 PAL20R4-B Byte Write Enable Generator—Single Bank Device U9

CLK $\overline{\text{PC1}}$ $\overline{\text{IQ1}}$ $\overline{\text{DQ1}}$ $\overline{\text{DQ2}}$ $\overline{\text{RAS}}$ $\overline{\text{RFRQ0}}$ OPT1 OPT0 A1 GND
 $\overline{\text{OE}}$ A0 $\overline{\text{WE0}}$ $\overline{\text{WE1}}$ $\overline{\text{RFACK}}$ $\overline{\text{RQ1}}$ $\overline{\text{RQ2}}$ $\overline{\text{RQ3}}$ $\overline{\text{WE2}}$ $\overline{\text{WE3}}$ NC23 VCC

$$\begin{aligned} \text{WE0} &= \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{A1}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{A1}} \cdot \overline{\text{A0}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{WE0}} \end{aligned}$$

$$\begin{aligned} \text{WE1} &= \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{A1}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{A1}} \cdot \overline{\text{A0}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{WE1}} \end{aligned}$$

$$\begin{aligned} \text{WE2} &= \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{A1}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{A1}} \cdot \overline{\text{A0}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{WE2}} \end{aligned}$$

$$\begin{aligned} \text{WE3} &= \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{A1}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} \cdot \overline{\text{A1}} \cdot \overline{\text{A0}} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{DQ2}} \cdot \overline{\text{WE3}} \end{aligned}$$

10623C-102

Figure 10-9 PAL20R4-B Byte Write Enable Generator—Single Bank Device U9 (continued)

$$\text{RFACK} := \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \overline{\text{RFRQ0}} \\ + \text{RFACK} \cdot (\overline{\text{RFREQ0}} \cdot \text{RQ3})$$

$$\text{RQ1} := \overline{\text{RQ1}} \cdot \overline{\text{PC1}} \cdot \text{RFACK} \\ + \text{RQ1} \cdot \overline{\text{RQ3}}$$

$$\text{RQ2} := \text{RQ1} \cdot \overline{\text{RQ3}}$$

$$\text{RQ3} := \text{RQ2} \cdot \overline{\text{RQ3}}$$

RFQ (Refresh Request)

Dynamic memories need to be completely refreshed every 4 μs , which translates into at least one row refreshed every 15.6 μs on average. To keep track of this time, a counter is used. Once a refresh interval has passed, a latch is used to remember that a refresh is requested while the counter continues to count the next interval. Once the refresh has been performed, the latch is cleared.

The counter and refresh request latch is implemented in an AmPAL22V10-25. Nine of the outputs form the counter, which is incremented by the system clock at 20 MHz. This gives up to $512 \times 50 \text{ ns} = 25.6\text{-}\mu\text{s}$ refresh periods. The synchronous preset term for all the registers is programmed to go active on a count value of 389, which will produce a refresh interval of $390 \text{ cycles} \times 40 \text{ ns} = 15.6 \mu\text{s}$. The one remaining output is used to implement the refresh request latch. That latch function (registered output) is also set by the synchronous preset term.

The equations for the counter are shown in Figure 10-4. Below are the preset and refresh latch equations:

$$\text{SYNCHRONOUS PRESET} = \text{RFQ2} \cdot \text{RFQ3} \cdot \text{RFQ4} \cdot \overline{\text{RFQ5}} \cdot \text{RFQ6} \cdot \text{RFQ7} \cdot \overline{\text{RFQ8}} \\ \cdot \overline{\text{RFQ9}} \cdot \text{RFQ10}$$

$$\text{RFRQ0} := \text{RFRQ0} \cdot (\overline{\text{RFACK}} \cdot \text{RQ1})$$

Refresh Sequence Equations

A refresh of the memory requires multiple clocks so the minimum $\overline{\text{RAS}}$ active time of 120 ns can be satisfied. To manage this, the following equations are used.

RFACK

The Refresh Acknowledge (RFACK) signal is used to begin a refresh sequence and to clear the pending refresh request. The RFACK signal goes active when the state machine (DQ token) re-enters the IDLE state as controlled by $\overline{\text{IQ1}}$ and $\overline{\text{DQ1}}$. RFACK is held active until the refresh request is cleared, indicated by $\overline{\text{RFRQ0}} \cdot \text{RQ3}$.

$$\text{RFACK} := \overline{\text{DQ1}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{RFRQ0}} \\ + \text{RFACK} \cdot (\overline{\text{RFREQ0}} \cdot \text{RQ3})$$

RQ1, RQ2, RQ3

The three cycles needed for a refresh are tracked by RQ1, RQ2, and RQ3. RQ1 will not go active until the cycle following the IDLE state. This is controlled by

$\overline{RQ1} \cdot \overline{PC1} \cdot RFACK$, which is only true during IDLE. RQ1 is held active for all three refresh cycles to provide a single signal to identify when a refresh is in progress. RQ2 and RQ3 simply follow RQ1 with RQ3, signaling the last cycle of the refresh sequence.

$$RQ1 := \overline{RQ1} \cdot \overline{PC1} \cdot RFACK \\ + RQ1 \cdot \overline{RQ3}$$

$$RQ2 := RQ1 \cdot \overline{RQ3}$$

$$RQ3 := RQ2 \cdot \overline{RQ3}$$

IME

The use of the Instruction for ME (IME) signal is based on the assumption that other blocks of instruction or data memory may be added later and that there may be valid addresses in address spaces other than instruction/data space.

This means this memory will only respond with \overline{IBACK} or \overline{DRDY} active when this block has been selected by valid addresses in the instruction/data space. This requires that at least some of the more significant address lines above the address range of this memory block be monitored to determine when this memory block is addressed. Also, it means the Instruction Request Type (IREQT), Data Request Type (DREQT0, DREQT1), and Pin 169 lines must be monitored to determine that an address is valid and lies in the instruction/data space.

IME is the indication the address of this memory block is present on the upper address lines, an instruction request is active, Pin 169 is inactive (test hardware has not taken control), and instruction/data address space is indicated. In other words, this memory block is receiving a valid instruction access request. This example design will assume the address of this memory block is equal to $A31 \cdot A30 \cdot A29 \cdot A28 \cdot A27 \cdot A26 \cdot A25 \cdot A24$. The equation for this signal is:

$$IME = IREQ \cdot \overline{IREQT} \cdot \overline{A31} \cdot \overline{A30} \cdot \overline{A29} \cdot \overline{A28} \cdot \overline{A27} \cdot \overline{A26} \cdot \overline{A25} \cdot \overline{A24} \cdot \text{Pin169}$$

Note that IME is not directly implemented as a PAL device output in this design. The terms are used in the generation of the ISTART term.

DME

The Data for ME (DME) signal is the indication the address of this memory block is present on the upper address lines, a data request is active, Pin 169 is inactive, and instruction/data address space is indicated. In other words, this memory block is receiving a valid data access request. This example design will assume the address of this memory block is equal to $A31 \cdot A30 \cdot A29 \cdot A28 \cdot A27 \cdot A26 \cdot A25 \cdot A24$. Note that for this design, both the instruction and data blocks reside in the same address space. This is possible because of the common memory array of the VDRAM accessible to either the instruction serial port or the data I/O port.

The equation for this signal is:

$$DME = DREQ \cdot \overline{DREQT0} \cdot \overline{DREQT1} \cdot \overline{A31} \cdot \overline{A30} \cdot \overline{A29} \cdot \overline{A28} \cdot \overline{A27} \\ \cdot \overline{A26} \cdot \overline{A25} \cdot \overline{A24} \cdot \text{Pin169}$$

As with IME, this term is not directly implemented.

ISTART

The Instruction Start (ISTART) signal causes the transition from IDLE to IRAS and IQ1 states. It is valid only in the IDLE state with no refresh sequence starting, identified by not being in any other state via $\overline{IQ1} \cdot \overline{DQ1} \cdot \overline{RFACK} \cdot \overline{PC1} \cdot \overline{RFRQ0}$. So when in the IDLE state and IME is active, ISTART is active.

$$\text{ISTART} = \overline{IQ1} \cdot \overline{DQ1} \cdot \overline{RFACK} \cdot \overline{PC1} \cdot \overline{RFRQ0} \cdot \text{IME}$$

DSTART

The Data Start (DSTART) signal is the same as ISTART except DME is the qualifier.

$$\text{DSTART} = \overline{IQ1} \cdot \overline{DQ1} \cdot \overline{RFACK} \cdot \overline{PC1} \cdot \overline{RFRQ0} \cdot \text{DME}$$

$\overline{\text{IBACK}}$

The instruction burst acknowledge ($\overline{\text{IBACK}}$) signal is applied to the Am29000 processor and is, in effect, the indication the interface state machine is in an active or suspended instruction access. The equation is:

$$\overline{\text{IBACK}} = \text{IQ2} + \overline{\text{IREQ}} \cdot \overline{\text{IBACK}}$$

The $\overline{\text{IBACK}}$ active state is entered during the IQ2 state. $\overline{\text{IBACK}}$ is delayed until IQ2 in order to hold the instruction address active on the bus until the CAS signal has gone active, thus eliminating the need for address latches or registers.

$\overline{\text{IBACK}}$ remains active until a new instruction access begins. The $\overline{\text{IBACK}}$ signal is combinatorial so it will go inactive in the same cycle $\overline{\text{IREQ}}$ goes active. This is required to hold the address on the bus until a new row transfer sequence can begin. The address must be held because there are no address latches or registers in this design to take the address from the bus. Address latches or registers would be required if $\overline{\text{IBACK}}$ were left active throughout the $\overline{\text{IREQ}}$ cycle.

This places a timing constraint on the $\overline{\text{IBACK}}$ response signal path that is different from earlier memory designs. $\overline{\text{IREQ}}$ is an unstable signal until 16 ns into a cycle. The D-speed PAL device logic implementing the $\overline{\text{IBACK}}$ logic has a propagation delay of 10 ns. The Am29000 processor has a response signal setup time of 15 ns. These delays total 41 ns, which means the logic OR gate used to combine all $\overline{\text{IBACK}}$ response signals in the system must have a worst-case propagation delay of 9 ns. This is not easy to achieve when several $\overline{\text{IBACK}}$ response lines in the system must be logically ORed. Therefore, seven PAL devices must be used.

A solution to this is to move a copy of the VDRAM-block $\overline{\text{IBACK}}$ logic down into the PAL device used to implement the $\overline{\text{IBACK}}$ response signal logical OR gate. That will eliminate one level of PAL device delay. The equation for the response OR-gate function would then become:

$$\begin{aligned}
 \overline{\text{IBACK}} &= \overline{\text{IBACK0}} \cdot \overline{\text{IBREQ.D}} \\
 &+ \overline{\text{IBACK1}} \cdot \overline{\text{IBREQ.D}} \\
 &+ \overline{\text{IBACK2}} \cdot \overline{\text{IBREQ.D}} \\
 &+ \overline{\text{IBACK3}} \cdot \overline{\text{IBREQ.D}} \\
 &+ \overline{\text{IBACK4}} \cdot \overline{\text{IBREQ.D}} \\
 &+ \overline{\text{IBACK5}} \cdot \overline{\text{IBREQ.D}} \\
 &+ \overline{\text{IQ2}} \cdot \overline{\text{IBREQ.D}} \\
 &+ \overline{\text{IREQ}} \cdot \overline{\text{IBACK}}
 \end{aligned}$$

where the numbered $\overline{\text{IBACK}}$ inputs are the $\overline{\text{IBACK}}$ signals from other bus devices and the $\overline{\text{IQ2}} + \overline{\text{IREQ}} \cdot \overline{\text{IBACK}}$ inputs are from the VDRAM control logic.

The $\overline{\text{IBACK}}$ logic defined earlier remains to provide a version of $\overline{\text{IBACK}}$ local to the VDRAM control logic. That version of the $\overline{\text{IBACK}}$ is not as time critical because it will simply be registered. Only $\overline{\text{IBACK.D}}$ is needed by other parts of the VDRAM control logic.

$\overline{\text{IBACK.D}}$

The $\overline{\text{IBACK}}$ Delayed ($\overline{\text{IBACK.D}}$) signal is simply a one-cycle delayed version of $\overline{\text{IBACK}}$. The logic for $\overline{\text{IBACK}}$ is implemented directly in the $\overline{\text{IBACK.D}}$ equation.

$$\begin{aligned}
 \overline{\text{IBACK.D}} &:= \overline{\text{IQ2}} \\
 &+ \overline{\text{IREQ}} \cdot \overline{\text{IBACK}}
 \end{aligned}$$

It is used in the generation of $\overline{\text{IRDY}}$, IOE0 , IOE1 , and CNT .

Instruction Initial Access States

Signals IQ1 , IQ2 , IQ3 , and IQ4 are used to control the state transitions from IQ1 to IACCESS and IRAS through WAIT during the first instruction access. The IQ1 signal goes active during the IQ1 and IRAS states, and remains active for four additional cycles. IQ1 will go active only when there is a valid Istart .

$\overline{\text{BINV}}$ inhibits the transition to IQ1 . $\overline{\text{BINV}}$ is used in this equation instead of in the Istart equation because it only needs a 15-ns setup time for the PAL device. If it were used in the Istart PAL device, an additional 15-ns combinatorial delay would be created, so the $\overline{\text{BINV}}$ signal could not be used correctly any more.

The IQ2 , IQ3 , and IQ4 signals are used to count the five cycles during which IQ1 is active. IQ3 is inactive during the fifth cycle after IQ1 goes active. This is used as a way of identifying the fifth cycle as the condition of $\text{IQ3} \cdot \text{IQ4}$. This eliminates the need for an additional signal to directly indicate the fifth cycle.

$$\begin{aligned}
 \text{IQ1} &:= \overline{\text{BINV}} \cdot \overline{\text{IQ1}} \cdot \text{Istart} \\
 &+ \text{IQ1} \cdot (\overline{\text{IQ3}} \cdot \text{IQ4})
 \end{aligned}$$

$$\text{IQ2} := \text{IQ1} \cdot (\overline{\text{IQ3}} \cdot \text{IQ4})$$

$$\text{IQ2} := \text{IQ1} \cdot (\text{IQ3} \cdot \text{IQ4})$$

$$\text{IQ3} := \text{IQ2} \cdot \overline{\text{IQ4}}$$

$$\text{IQ4} := \text{IQ3}$$

Data Initial Access States

These equations are similar in function to the IQ4–IQ1 signals. They control state transitions during data accesses. DQ1 goes active during the DQ1 state as a result of a valid DSTART signal during the IDLE state. DQ2 through DQ4 simply count off the four DQ states. The reason for using $\overline{\text{BINV}}$ here is the same as for the instruction side.

$$\text{DQ1} := \overline{\text{BINV}} \cdot \overline{\text{DQ1}} \cdot \text{DSTART} \\ + \text{DQ1} \cdot \overline{\text{DQ4}}$$

$$\text{DQ2} := \text{DQ1} \cdot \overline{\text{DQ4}}$$

$$\text{DQ3} := \text{DQ2} \cdot \overline{\text{DQ4}}$$

$$\text{DQ4} := \text{DQ3} \cdot \overline{\text{DQ4}}$$

Precharge States

At the end of any DQ port access, the $\overline{\text{RAS}}$ lines must be made inactive to precharge internal memory buses before another access with a different row address may begin. Three cycles are needed, indicated by the signals PC1 and PC2. The PC1 signal is active during the PC1 state and the PC2 state. The PC2 signal is active during the PC2 state and the first IDLE state that follows the PC2 state. PC1 goes active following the third cycle of any instruction, data, or refresh sequence. In other words, once the minimum $\overline{\text{RAS}}$ pulse width requirement is satisfied, $\overline{\text{RAS}}$ is made inactive to begin precharging for the next access. In the case of a data read where the output data must be held valid after $\overline{\text{RAS}}$ goes inactive, the $\overline{\text{CAS}}$ signal is kept active to hold the data.

$$\text{PC1} := \overline{\text{PC1}} \cdot \text{IQ3} \\ + \overline{\text{PC1}} \cdot \text{DQ3} \\ + \overline{\text{PC1}} \cdot \text{RQ3} \\ + \text{PC1} \cdot \overline{\text{PC2}}$$

$$\text{PC2} := \text{PC1}$$

Transfer Cycle Enable and DQ Port Output Enable

On a VDRAM, there is a dual function signal, called Transfer (TR), which controls when a row transfer cycle is performed and also when the random I/O data port is output enabled. When TR is active during the active edge of $\overline{\text{RAS}}$, a transfer cycle is performed.

The timing of TR is critical when performing this function. It must stay active for a minimum of 90 ns after $\overline{\text{RAS}}$ goes active when the Fujitsu VDRAM (MB81461-12) is used, or 100 ns after $\overline{\text{RAS}}$ goes active when the NEC VDRAM (PD41264-12) is used. The signal must also be inactive before the serial shift clock may go from Low to High, to clock out the first instruction word: 25 ns before for the Fujitsu VDRAM, or 10 ns before for the NEC VDRAM.

To make the above timing constraint fit within the six-cycle initial access time of this memory design, a delay line must be used to precisely set the duration of the TR signal. A separate $\overline{\text{RAS}}$ signal, which is not loaded by the capacitance of either memory bank, is the input to the delay line. The output for a 100-ns delay is TEXT11. More details of this timing are provided in the intra-cycle timing section of this chapter.

TR goes active with $\overline{\text{IREQ}}$, so TR is set up before $\overline{\text{RAS}}$ goes active. TR latches itself active until the appropriate TEXTIT signal goes active. The NEC input is strapped to Low when the NEC memory is used, or to High when the Fujitsu VDRAM is used.

Finally, when DQ2 is active during a non-transfer cycle of a read operation, the active TR signal enables the DQ port output.

$$\begin{aligned} \text{TR} &= \overline{\text{DQ1}} \cdot \overline{\text{IREQ}} && ;\text{Start Transfer for I-Burst} \\ &+ \overline{\text{DQ1}} \cdot \text{TR} \cdot \overline{\text{TEXTIT}} && ;\text{Delay line for Transfer} \\ &+ \text{DQ2} \cdot \overline{\text{WE}} && ;\text{OE for Data read} \end{aligned}$$

Shift Clock

The signal clocking each new instruction out of the serial port is referred to as SAS. This signal must be Low at the time TR goes inactive and it must remain Low for the 25-ns or 10-ns period noted earlier. Once that timing constraint is satisfied, the next rising edge of SAS clocks the serial port output. SAS is held Low while IQ1 is active and IQ4 is inactive. After that time, SAS is controlled by SYSCLK so a new instruction is clocked out every system clock cycle.

There is a special requirement on SAS immediately following system power-on time. The SAS signal must be cycled at least eight times before proper device operation is achieved following a power-on sequence. To ensure this is done, the system reset signal is used to connect the system clock to SAS. This ensures SAS is cycled during the system power-on reset time.

$$\begin{aligned} \overline{\text{SAS}} &= \overline{\text{RESET}} \cdot \overline{\text{SYSCLK}} \\ &+ \overline{\text{RESET}} \cdot \text{IQ1} \cdot \overline{\text{IQ4}} \\ &+ \overline{\text{RESET}} \cdot \text{IQ4} \cdot \overline{\text{IQ3}} \cdot \overline{\text{SYSCLK}} && ;\text{Start term} \\ &+ \overline{\text{RESET}} \cdot \text{IQ1} \cdot \overline{\text{SYSCLK}} \cdot \overline{\text{IBREQ}} && ;\text{Stop term} \end{aligned}$$

$\overline{\text{IRDY}}$

The Instruction Ready ($\overline{\text{IRDY}}$) signal indicates there is valid read data on the instruction bus.

$$\begin{aligned} \overline{\text{IRDY}} &= \text{IQ4} \\ &+ \overline{\text{IQ1}} \cdot \overline{\text{IBREQ}} \cdot \text{D} \end{aligned}$$

This memory design is always ready with data in the IACCESS state indicated by IQ4.

The memory is also ready when $\overline{\text{IBREQ}}$ is active, following the initial instruction word access.

The reason $\overline{\text{IRDY}}$ must be a combinatorial signal is that $\overline{\text{IBREQ}}$ comes very late in the previous cycle and must be registered. There is no $\overline{\text{IBREQ}}$ qualifying time available in the previous cycle before SYSCLK rises. This means the information that $\overline{\text{IBREQ}}$ was active in the last cycle is not available until the cycle in which $\overline{\text{IRDY}}$ should go active for a resumption of a suspended burst access.

$\overline{\text{DRDY}}$

The Data Ready ($\overline{\text{DRDY}}$) signal is the equivalent of $\overline{\text{IRDY}}$, except for data accesses. The difference is that since no burst accesses are supported, $\overline{\text{DRDY}}$ will go active only once in each simple access during the DACCESS state in a read, or during DCAS or WAIT in

a write operation. Due to different data hold times for the Fujitsu and NEC VDRAMs, DRDY must be held until the WAIT state when using the NEC VDRAM.

$$\text{DRDY} = \overline{\text{WE}} \cdot \text{DQ4} + \text{WE} \cdot \text{DQ3} \cdot \overline{\text{DQ4}}$$

Pipeline Enable

During a read operation, the data address is no longer needed on the address bus following the DCAS state. So, to help improve system performance, the Pipeline Enable (PEN) signal response is made active during the DCAS state. This active $\overline{\text{PEN}}$ signal tells the processor the address is no longer needed and allows the processor to place a new address on the bus. In cases where the next address to be issued is for an instruction or data access from a different block of memory, the next access can begin while the current data access finishes.

$$\text{PEN} = \text{DQ2} \cdot \overline{\text{DQ3}}$$

WE

In this design, the VDRAMs are written with the early write protocol. This means WE goes active before or at the same time as the CAS signal. So data is written to the VDRAM at the time when CAS goes active. At this point, data is available on the data bus.

The Write Enable (WE) signal is not allowed to be active during the row transfer sequence that begins each non-sequential instruction access. This is because no write operations are supported for the serial port. During a data access, the read/write line is latched by the DQ2 signal at the end of the DCAS state.

WE shows that a write to the memory section is done, regardless of the half-word or byte address.

$$\text{WE} = \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} + \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \text{DQ2} \cdot \text{WE}$$

To make use of the byte write capability of the Am29000 processor, the following signals are used. Please note that this is true for Big endian notation only.

WE0 = Enable byte write for Bits 31–24

WE1 = Enable byte write for Bits 23–16

WE2 = Enable byte write for Bits 15–8

WE3 = Enable byte write for Bits 7–0

The following signals are not real signals and are used only as macros for the WE3–WE0 equations shown below.

$$\begin{aligned} \text{WEN} &= \overline{\text{OPT1}} \cdot \overline{\text{OPT0}} && ;(32\text{-bit Word Enable}) \\ \text{HEN0} &= \text{OPT1} \cdot \overline{\text{OPT0}} \cdot \overline{\text{A1}} && ;(\text{Half-Word Enable, Bits 31–16}) \\ \text{HEN1} &= \text{OPT1} \cdot \overline{\text{OPT0}} \cdot \text{A1} && ;(\text{Half-Word Enable, Bits 15–0}) \\ \text{BEN0} &= \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \overline{\text{A1}} \cdot \overline{\text{A0}} && ;(\text{Byte Enable, Bits 31–24}) \\ \text{BEN1} &= \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \overline{\text{A1}} \cdot \text{A0} && ;(\text{Byte Enable, Bits 23–16}) \\ \text{BEN2} &= \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \text{A1} \cdot \overline{\text{A0}} && ;(\text{Byte Enable, Bits 15–8}) \\ \text{BEN3} &= \overline{\text{OPT1}} \cdot \text{OPT0} \cdot \text{A1} \cdot \text{A0} && ;(\text{Byte Enable, Bits 7–0}) \end{aligned}$$

The equations for the WE0-WE3 are as follows:

$$\begin{aligned} \text{WE0} &= \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{WEN} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{HEN0} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{BEN0} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \text{DQ2} \cdot \text{WE0} \\ \text{WE1} &= \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{WEN} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{HEN0} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{BEN1} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \text{DQ2} \cdot \text{WE1} \\ \text{WE2} &= \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{WEN} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{HEN1} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{BEN2} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \text{DQ2} \cdot \text{WE2} \\ \text{WE3} &= \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{WEN} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{HEN1} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \overline{\text{DQ2}} \cdot \overline{\text{RW}} \cdot \text{BEN3} \\ &+ \overline{\text{IQ1}} \cdot \text{DQ1} \cdot \text{DQ2} \cdot \text{WE3} \end{aligned}$$

Row Address Strobes

There are three identical Row Address Strobe ($\overline{\text{RAS}}$) lines. One $\overline{\text{RAS}}$ line drives the memories and the other two $\overline{\text{RAS}}$ lines drive the delay line used to switch the address mux at the appropriate time and to control the duration of the transfer signal. Multiple lines are used to split the capacitive and inductive load of the memory array in order to improve signal speed.

$\overline{\text{RAS}}$ is made active by a valid ISTART, DSTART, or refresh condition. $\overline{\text{RAS}}$ is held active for three cycles to satisfy the minimum pulse-width requirement on $\overline{\text{RAS}}$.

$$\begin{aligned} \text{RAS} &:= \overline{\text{BINV}} \cdot \overline{\text{RAS}} \cdot \text{ISTART} \\ &+ \overline{\text{BINV}} \cdot \overline{\text{RAS}} \cdot \text{DSTART} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{PC1}} \cdot \text{RFACK} \\ &+ \overline{\text{RAS}} \cdot \text{IQ1} \cdot \overline{\text{IQ3}} \\ &+ \overline{\text{RAS}} \cdot \text{DQ1} \cdot \overline{\text{DQ3}} \\ &+ \overline{\text{RAS}} \cdot \text{RFACK} \cdot \overline{\text{RQ3}} \end{aligned}$$

Column Address Strobes

$\overline{\text{CAS}}$ goes active in the cycle after $\overline{\text{RAS}}$ during instruction or data accesses. Only in the case of a refresh sequence will $\overline{\text{CAS}}$ be made active prior to $\overline{\text{RAS}}$. This will initiate a CAS-before-RAS refresh cycle in the memories. In this case, $\overline{\text{CAS}}$ is made active during the IDLE state.

$$\begin{aligned} \text{CAS} &:= \text{RAS} \cdot \text{IQ1} \\ &+ \text{RAS} \cdot \text{DQ1} \\ &+ \overline{\text{RAS}} \cdot \overline{\text{IQ1}} \cdot \overline{\text{DQ1}} \cdot \text{RFRQ0} \end{aligned}$$

INTRA-CYCLE TIMING

All of the following description is based on the 20-MHz Am29000 processor system; the cycle time is 50 ns.

This memory architecture has five timing sequences of interest. The first is a cycle used to decode the memory address and control signals from the processor. At the end of this decode cycle, the $\overline{\text{RAS}}$ registers are loaded to begin the initial access of memory if the address selects the memory block.

Following the decode cycle is the Row Address cycle, in which the row address strobe is made active at the beginning of the cycle, and the address multiplexer is later switched between the row address and the column address.

The third timing is a data access, where the $\overline{\text{CAS}}$ signal goes active to begin a read operation or perform a write operation.

The fourth is the critical timing sequence between $\overline{\text{RAS}}$ going active and the first shift clock (SAS) active edge which occurs in the row transfer of the initial access of an instruction burst.


The fifth timing is that of a burst access. This is the timing between SAS going High and a valid instruction being transferred to the processor. This time is designed to fit within two clock cycles.

The combination of a decode cycle followed by the row-address cycle and by a data-read access time defines a five-cycle read of data. Subsequent data-read operations may be six cycles long if the next data address appears during the PC2 precharge state.

For a data write, the access time is made up of a decode cycle followed by a data write, in which $\overline{\text{DRDY}}$ is active in the second or third cycle after decode. The write operation thus takes three to four cycles. Subsequent data-write cycles may take up to six cycles to complete if the next address appears during the data WAIT state (i.e., during the memory-precharge time). A read following a write could take up to eight cycles to complete if it started during the precharge time of the previous access.

The initial access time of an instruction access is made up of a decode cycle, plus a row transfer sequence, plus the first burst access. This totals six cycles. Again, this could be extended up to nine cycles if the instruction address were to appear during the precharge time following a data write operation, or up to seven cycles if it followed a data read.

After the initial access, all burst instruction accesses use a one-clock-cycle timing.

 Figure 10-10 VDRAM Interleaved Bank Memory Decode Cycle

10623C-103

Decode Timing

Within the decode cycle the address timing path is made up of:

- The Am29000 processor clock to address and control valid delay of 16 ns
- Address decode logic PAL device delay of 15 ns
- The setup time of the \overline{RAS} PAL device, 15 ns

Assuming B-speed PAL devices, those times total 46 ns, as shown in Figure 10-10.

Also, within the decode cycle time is the control signal to response signal path. In fact, this timing path is present in every cycle in the sense that the memory response signals must be valid in every clock cycle. This delay path is made up of:

- Clock-to-output time of registers within the control logic state machine PAL device, 12 ns
- Propagation delay of the control logic PAL device, 15 ns
- Propagation delay of a logical OR gate on the response signals from each memory block, 10 ns (D-speed PAL device)
- Control signal set-up time of the processor, 12 ns

Again assuming B-speed PAL devices, these delay path times total 49 ns.


Row Address Timing

Referring to Figure 10-11, within the row-address cycle, the \overline{RAS} line goes Low, which initiates a time delay signal later causing the address multiplexer to change from the row to the column address.

This delay path is made up of:

- Clock-to-output time of \overline{RAS} signal registers within the control-logic state machine PAL device (12 ns), plus an added delay due to capacitive and inductive loading by the memory array of the PAL device outputs. The estimated delay is 2 ns. This is

Figure 10-11 Row Address Timing

 

added to the 12-ns delay of the $\overline{\text{RAS}}$ line (standard 50 pF load) for a worst-case total of 14 ns.

- Mux switch control signal delay path, which runs in parallel with the memory $\overline{\text{RAS}}$ delay just described. This mux signal delay is made up of the clock-to-output delay of a lightly loaded $\overline{\text{RAS}}$ signal (12 ns) plus the delay line time (20 ns).
- Minimum and maximum switching time of the address multiplexer, 4 ns to 9.5 ns, plus added delay for loading (same as calculated above), 2 ns.

Thus the memory $\overline{\text{RAS}}$ signals are stable no later than 14 ns into the cycle, and the address mux output can change no sooner than 36 ns (assuming $\overline{\text{RAS}}$ outputs from the same PAL device will always have similar delays). So, the address hold time after $\overline{\text{RAS}}$ is 22 ns. This works out to satisfy the 15 ns of required address hold time after $\overline{\text{RAS}}$ goes active. Also, the column address is settled by no later than 43.5 ns into the cycle. So the column address is set up prior to the $\overline{\text{CAS}}$ going active in the next cycle.

CAS-to-Data Ready

In a data read operation, the Column Address Strobe ($\overline{\text{CAS}}$) signal-to-end of $\overline{\text{DRDY}}$ cycle is made up of:

- $\overline{\text{CAS}}$ signal clock-to-output time, 12 ns, plus added delay for heavier-than-normal output loading, as determined above, 2 ns.
- Memory access delay from $\overline{\text{CAS}}$, 60 ns.
- Processor set-up time, 8 ns.

This totals 82 ns, which translates into just two cycles. To allow an easy upgrade to higher frequencies, only by changing the RAMs, a three cycle access is assumed here. Therefore, $\overline{\text{DRDY}}$ is not made active until the second cycle following the DCAS state.

In a data-write operation, the data is written by the falling edge of $\overline{\text{CAS}}$. But the data hold time relative to $\overline{\text{RAS}}$ going active may also have to be satisfied before $\overline{\text{DRDY}}$ is made active to free the address and data buses.

For the Fujitsu memory, only the data hold time relative to $\overline{\text{CAS}}$ is required; this is 30 ns after $\overline{\text{CAS}}$ is active. The Am29000 processor will provide a minimum of 4-ns data hold time. The data transceiver will provide an additional minimum of 4-ns hold time beyond the end of the DCAS cycle. As shown in Figure 10-12, these will ensure meeting the hold time if $\overline{\text{DRDY}}$ is active in the DCAS cycle.

For the NEC memory, the hold time relative to $\overline{\text{RAS}}$ is the longer delay path; this is 95 ns from $\overline{\text{RAS}}$ going active. This implies the data must be held 9 ns into the WAIT state after DCAS. So in this case, $\overline{\text{DRDY}}$ must not go active until the WAIT state after DCAS, as shown in Figure 10-13.

Figure 10-12 $\overline{\text{CAS}}$ -to-Data Ready Timing


 


Figure 10-13 NEC Memory Write Data Hold Time

 

RAS-to-Shift Clock Timing

Referring to Figure 10-13, in order to maintain a six-cycle initial instruction access time, only three cycles can be used for the timing of signals between $\overline{\text{RAS}}$ and SAS. In that time, the TR signal must be active for 90 ns to 100 ns after $\overline{\text{RAS}}$, and it must be inactive 25 ns to 10 ns before SAS goes active, depending on the memory used. It is a tight fit. The timing is as follows:

- Clock-to-memory $\overline{\text{RAS}}$ delay, 12 ns, plus the added delay for heavy output loading of 2 ns, for a total of 14 ns.
- In parallel with the memory $\overline{\text{RAS}}$, a separate copy of $\overline{\text{RAS}}$ that is not loaded by the memory array is used to drive the delay line determining the end of the TR signal. Its clock-to-output delay time is 8 ns.
- Delay line time of 100 ns.
- Propagation delay of the PAL device, which generates TR from the output of the delay line, is a minimum of 3 ns and a maximum of 10 ns, plus an output loading delay of 2 ns.
- The SAS output is combinatorial and is dependent on registered input signals (IQ1, IQ3, IQ4). Its minimum delay is the minimum clock-to-output delay plus the minimum propagation delay of a D-speed PAL device, plus the added delay for memory loading (3 ns + 3 ns + 2 ns = 8 ns). Its maximum delay consists of 12 ns of clock-to-output delay, 10 ns of propagation delay, and a loading delay of 2 ns for a total delay of 24 ns.

Assuming minimum delays in the TR and SAS signals and maximum delays in the $\overline{\text{RAS}}$ signals, the hold time for TR will be met for either the NEC or Fujitsu memories. For the Fujitsu memory, the TR setup time before SAS will have a 16 ns margin as shown in Figure 10-14. For the NEC memory, there is 31 ns of margin as shown in Figure 10-15.

The maximum and minimum delays described above rely on the fact that all $\overline{\text{RAS}}$ outputs are implemented in the same PAL device, and TR and SAS outputs reside in the same PAL device. The PAL device outputs for related signals will always track each other with respect to minimum or maximum delay times.

Burst Timing

Within the burst access cycle, the address to data path timing is determined by:

- Propagation delay of SAS PAL device, 10 ns, plus added delay for capacitive and inductive load as was done for the $\overline{\text{RAS}}$ line. The same derating delay of 2 ns will apply.
- Memory access time for serial port, 30 ns
- The processor set-up time, 8 ns


Those delays produce a worst-case total 50 ns as shown in Figure 10-16.

INTER-CYCLE TIMING

Inter-cycle timing for instruction, data-read, and data-write cycles are provided in Figures 10-17 through 10-19. In these timing diagrams, the horizontal time scale is 25-ns per division.

Figure 10-14 Fujitsu Transfer Enable Timing


Fujitsu Memory

 

10623C-107


Figure 10-15 NEC Transfer Enable Timing

NEC Memory

 


10623C-108

Figure 10-16 Burst Access Timing

 


10623C-109

Figure 10-17 VDRAM Instruction Burst Timing

 


10623C-110

Figure 10-18 VDRAM Data Read Timing

 

10623C-111

Figure 10-19 VDRAM Data Write Timing

 

Early write, due to \overline{WE} going active before \overline{CAS} active.
 Also if \overline{WE} is active, DATA is valid.

10623C-112

PARTS LIST

The parts list for the Am29000 Processor Single-Bank VRAM Interface is provided in Table 10-1.

Table 10-1 Single-Bank VRAM Interface Parts List

Item No.	Quantity	Device Description
U1	1	PAL20L8-B
U2	1	AmPAL22V10-25
U3	1	74F175
U4-U5	2	74F157
U6	1	AmPAL22V10-15
U7	1	PAL20L8-D
U8	1	PAL20R8-B
U9	1	PAL20R4-B
U10-U17	8	MB81461-12 or PD41264
U18	1	XTTLDM-100

18 packages

FINAL DISCUSSION

Looking at the design, there may be concerns about the size of the design, whether it is compact or large. For an objective analysis, first look at the design from a theoretical standpoint, without considering the type of processor being used.

To perform single-cycle bursts with VDRAM at clock speeds up to 20 MHz, you can use one bank of VDRAMs. Because of the 32-bit wide architecture, you need a minimum of eight VDRAMs (64K x 4-bit devices).

For DRAMs, the address lines must be multiplexed. This implies the addition of two multiplexers.

A refresh counter must be implemented. This implies the addition of one PAL device.

In any case, you need either a delay line or a high-speed clocked state machine for fast generation of \overline{RAS} and \overline{CAS} signals.

In summary, the raw logic, which does not depend on the type of processor used, requires 12 devices. Only six PAL devices are used for all the rest of the design, including the state machines, the generation of the \overline{RAS} and \overline{CAS} signals, and the interface to the Am29000 processor. By using higher-integrated PAL devices or higher-density logic, this number could be reduced further.



INTEGRATED MEMORY INTERFACE CONTROLLERS

There are several types of integrated memory control devices useful in applications for the 29K Family of microprocessors. These devices often provide a simple, cost-effective implementation of the memory system. Several of these devices are introduced in this chapter.

The V29BMC Burst Mode Memory Controller, manufactured by the V3 Corporation, is a single-chip memory interface controller that works directly with the Am29000 processor and dual interleaved banks of **fast page mode** DRAMs.

The SCORE Peripheral Access Controller, manufactured by the Vista Controls Corporation, is a single-chip interface controller supporting a dual-bank, interleaved instruction memory and a non-burst data memory. In addition, it provides I/O ports for interfacing with DSP, D/A, A/D, and other types of processors, and also provides programmable timers.

The SCORE VME Interface Controller, another product of the Vista Controls Corporation, serves as a single-chip interface between the Am29000 processor and a VME bus. This device makes it easy and economical to build a system integrating the Am29000 processor with VME-bus peripherals.

The VY86C129 29K Memory Controller and the VY86C429 Laser Printer Interface Controller are two ASIC products of VLSI Technology, Inc., which can be used to implement an Am29000 processor-based laser printer controller. The VY86C129 serves as the memory controller while the VY86C429 serves as a laser beam controller and peripheral I/O interface.

V29BMC BURST MODE MEMORY CONTROLLER

One simple, cost-effective solution to memory selection and interfacing is to use a V29BMC Burst Mode Memory Controller device, together with fast page mode DRAMs organized in two interleaved banks. This solution offers a combination of hardware design simplicity, low component count, reasonable memory costs, and high performance.

The key feature of a V29BMC-based memory system is its ability to obtain high performance with relatively low-cost DRAMs. This is accomplished by exploiting the fast page mode of DRAMs, an operating mode allowing high-speed sequential access to data stored in a single row of the DRAM. The result is that column access times of the DRAM (within a single row) are similar to expensive static RAMs; a 100-ns DRAM can behave like a 25-ns SRAM within a given row. To further increase performance, the V29BMC handles two interleaved memory banks without the addition of external logic.

The V29BMC is a single-chip device manufactured by the V3 Corporation. It is designed to simplify the implementation of burst mode access in high-performance systems using the Am29000 processor and page mode DRAMs. The device contains the state machine and all the necessary logic to implement the memory interface, virtually eliminating the need for additional logic devices.


The V29BMC offers the following features:

- Interfaces directly to the Am29000 processor
- Manages page mode dynamic RAM devices ranging from 64 Kbits to 16 Megabits
- Manages both instruction and data memory, using either separate or combined buses
- High-drive output buffers drive memory array directly
- Flexible instruction/data bus buffer management
- Software programmable configuration of memory size, memory location, and operational parameters
- CMOS technology; very low power consumption
- Available in speeds ranging from 16 MHz to 33 MHz
- Available in a 124-pin PGA or 132-pin QFP package

The designer simply connects the V29BMC interface signals directly to those of the Am29000 processor and the memory array. No other external logic is required, except for instruction/data buffers (depending on the implementation).

Figure 11-1 is a block diagram showing the three main components of a V29BMC-based memory system: the V29BMC device, the dual-bank DRAM array, and the instruction/data bus buffers.

Figure 11-1 V29BMC-Based Memory System Block Diagram

 

Design Flexibility

The V29BMC handles both instruction and data accesses, and offers a highly flexible bus buffer management strategy. These features allow the system architect to select the features most appropriate for a given set of system requirements.

Here are some examples of memory system options using the V29BMC:

- Common instruction/data space
- Split instruction/data spaces
- Software-split instruction/data spaces
- Slow memory devices with two-cycle burst write
- Fast memory devices with single-cycle burst write
- Socket-compatible memory devices selected by software configuration
- Selection of buffer devices ranging from the 74F245 to the Am29C983 Bus Interchange Buffer

Interfacing the V29BMC

The V29BMC connects directly to the Am29000 processor address bus and instruction/data bus control signals. The V29BMC-to-Am29000 processor interface handles simple, pipelined, and burst mode accesses for both data and instructions. Because no external logic is required to implement the synchronous channel connection, propagation delays and signal skews that could affect performance are avoided.

A single V29BMC may be used to handle a combined instruction/data memory. To allow overlapped instruction and data accesses, two V29BMC devices can be used to handle separate instruction and data memories. The V29BMC processor-reply output signals are designed so they can simply be wire-ORed together and connected directly to the processor interface.


On the memory side, the V29BMC directly drives an array of DRAM devices supporting page mode accesses. (The majority of current DRAMs offer such support.) Each memory array is organized as two banks of 32 bits each. All the standard memory device sizes from 64 Kbits to 16 Megabits are supported.

Software Configuration

The V29BMC device is configured by software, using the first 32-bit memory read access following de-assertion of the device's reset input. The 32-bit word programs the V29BMC operating mode: the memory block address, the number of burst write cycles (one or two), the number of RAS access cycles (three or four), the byte order (big or little Endian), the bus buffer control mode (four different modes available), and the DRAM device size (64K to 32 Meg). Figure 11-2 shows the bit fields programming the V29BMC.

In memory systems containing two or more V29BMC devices, the V29BMCs can be daisy-chained together, with the reset-out signal from one V29BMC connected to the reset-in signal input to the next one. When one V29BMC is configured, it de-asserts its reset-out signal, allowing the next V29BMC to be configured on the next 32-bit memory read access. Once configured, a V29BMC only responds to addresses within its configured block address range.

Figure 11-2 V29BMC Configuration Word

 

10623C-114

For More Information

For more detailed information on the V29BMC Burst Mode Memory Controller and associated development products, contact the manufacturer directly:

V3 Corporation
 759 Warden Avenue
 Scarborough, Ontario
 Canada M1L 4B5
 Tel: (416) 285-9188
 Fax: (416) 285-9585

SCORE PERIPHERAL ACCESS CONTROLLER

The SCORE Peripheral Access Controller, manufactured by the Vista Controls Corporation, is a 180-pin PGA CMOS gate array allowing rapid design and implementation of instruction memory, data memory, and I/O communication subsystems operating with the Am29000 processor. The major features of the device are listed below.

- Provides logic and counters to support a dual-bank, interleaved instruction memory, using three-cycle initial access and single-cycle burst access; each bank may contain up to 4 Megabytes EPROM, EEPROM, PROM, or SRAM
- Provides logic to support data memory using two-cycle (non-burst) access; up to 1 Megabyte of data memory
- Provides an I/O communication interface using a 128-by-16 dual port RAM; can be used with DSP, D/A, A/D, or other type of processor
- Provides programmable watchdog timer and programmable frame-clock timer
- Provides 16 digital TTL-level inputs and outputs (eight inputs and eight outputs)

SCORE VME INTERFACE CONTROLLER

The SCORE VME Interface Controller, manufactured by the Vista Controls Corporation, is a 180-pin PGA CMOS gate array connecting directly to a VME bus, allowing rapid design and implementation of an Am29000 processor interface to the bus. The device complies with Mil-Std-883C. The major features of the device are listed below.

- Provides VME bus system control functions: system controller determination, system clock generator, system reset generator, and bus arbiter

- Provides CPU support functions: RS-232 serial port, local interrupt handler, local reset generator, local bus timeout generator, and general-purpose programmable timer
- Provides VME bus data transfer functions: bus requester, local CPU bus requester, local CPU bus arbiter, master and slave handshake interfaces (both 16-bit and 24-bit address with 16-bit data), VME location monitors, VME bus timeout generator
- Supports half-word swapping between VME bus and CPU bus
- Performs address decoding and base address mapping during VME slave accesses

For More Information

For detailed information on the SCORE Peripheral Access Controller and/or VME Interface Controller, contact the manufacturer directly:

Vista Controls Corporation
27825 Fremont Court
Valencia, CA 91355
Tel: (805) 257-4430
Fax: (805) 257-4782

VLSI TECHNOLOGY ASIC DEVICES

The VY86C129 29K Memory Controller and the VY86C429 Laser Printer Interface Controller, ASIC products of VLSI Technology, Inc., can be used to implement a Am29000 processor-based laser printer controller. The VY86C129 serves as the memory controller, while the VY86C429 serves as peripheral I/O interface and laser beam controller. These ASICs make it relatively simple to design the complete memory controller and I/O interface for a laser printer system. Figure 11-3 is a high-level block diagram of a laser printer controller using these devices.

VY86C129 29K Family Memory Controller Features

The VY86C129 29K Memory Controller offers the following features:

- Supports 29K Family three-bus processors (Am29000, Am29050, and Am29005 processors) and two-bus processors (Am29030 and Am29035 processors)
- Provides processor bus interface, address mapping, and control logic
- Provides swap and data isolation buffer control signals (DIR and \overline{OE})
- Supports DRAM from 512 Kbytes to 64 Mbytes in one to four banks, with built-in page-mode access logic
- Supports on-board ROM from 512 Kbytes to 16 Mbytes: one-way with four banks, two-way with two banks, or four-way with two banks
- Supports cartridge ROM (up to two HP-type ROM cartridges)
- Supports watchdog timer using bidirectional RES signal line
- Provides 8-bit peripheral expansion bus



**ADVANCED
MICRO
DEVICES, INC.**

901 Thompson Place
P.O. Box 3453
Sunnyvale

California 94088-3453

(408) 732-2400

TWX: 910-339-9280

TELEX: 34-6306

TOLL-FREE

(800) 538-8450

**CORPORATE
APPLICATIONS**

HOTLINE

(800) 222-9323

(408) 749-5703

**29K LITERATURE
ORDERING**

(800) 292-9263

(512) 462-5651

**29K SUPPORT PRODUCTS
ENGINEERING HOTLINE**

USA (800) 2929-AMD

UK 0-800-89-1131

JAPAN 0-031-11-1129

CANADA (800) 531-5202 Ext 55651

GERMANY 49-89-4114-0



**RECYCLED &
RECYCLABLE**

Printed in USA

Cus-9M-3/92

10623C